

CIS 371

Computer Organization and Design


Unit 2: Digital Logic & Hardware Description

Based on slides by Prof. Amir Roth & Prof. Milo Martin

Readings


- Digital logic
 - P&H, Appendix C
- Manufacturing
 - P&H, Section 1.7
- See webpage for Verilog HDL resources

 This Unit: Digital Logic & Hdw Description




- Transistors & fabrication
- Digital logic basics
 - Focus on useful components
- Hardware design methods
 - Introduction to Verilog

Motivation: Implementing an ISA

 


- **Datapath**: performs computation (registers, ALUs, etc.)
 - ISA specific: can implement every insn (single-cycle: in one pass!)
- **Control**: determines which computation is performed
 - Routes data through datapath (which regs, which ALU op)
- **Fetch**: get insn, translate opcode into control
- **Fetch** → **Decode** → **Execute** "cycle"

Two Types of Components

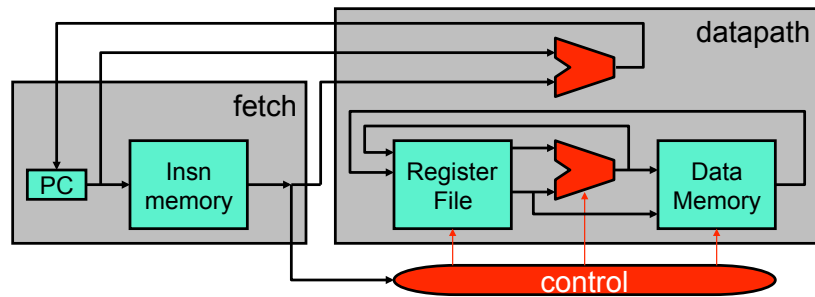


- **Purely combinational:** stateless computation
 - ALUs, muxes, control
 - Arbitrary Boolean functions
- **Combinational/sequential:** storage
 - PC, insn/data memories, register file
 - Internally contain some combinational components

Example Datapath

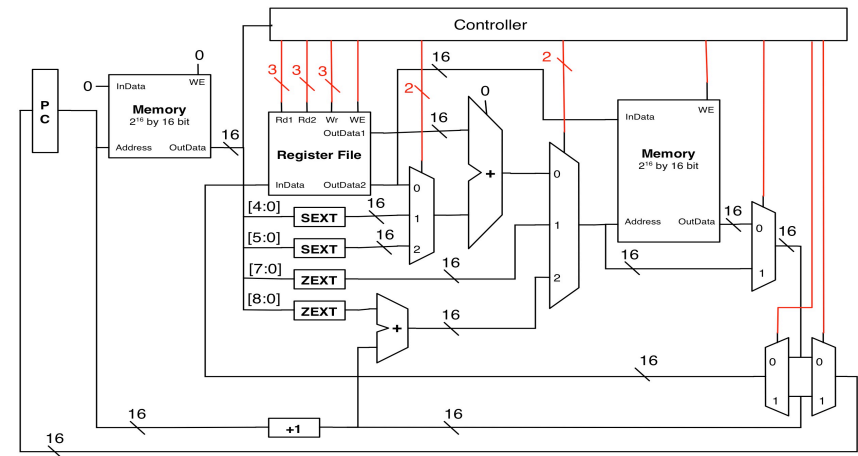


Transistors & Fabrication

 


Intel
Pentium M
Wafer

Semiconductor Technology

 


- Basic technology element: **MOSFET**
 - Solid-state component acts like electrical switch
 - **MOS**: metal-oxide-semiconductor
 - Conductor, insulator, semi-conductor
- **FET**: field-effect transistor
 - Channel conducts source→drain only when voltage applied to gate
- **Channel length**: characteristic parameter (short → fast)
 - Aka "feature size" or "technology"
 - Currently: 0.022 micron (μm), 22 nanometers (nm)
 - Continued miniaturization (scaling) known as "**Moore's Law**"
 - Won't last forever, physical limits approaching (or are they?)

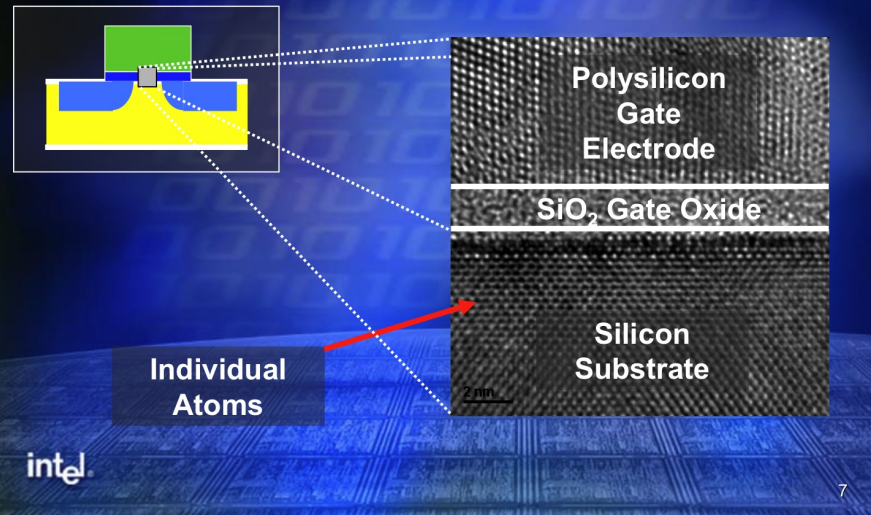
Gate dielectric today is only a few molecular layers thick



Transistors

 


Transistor Geometry: Length & Scaling

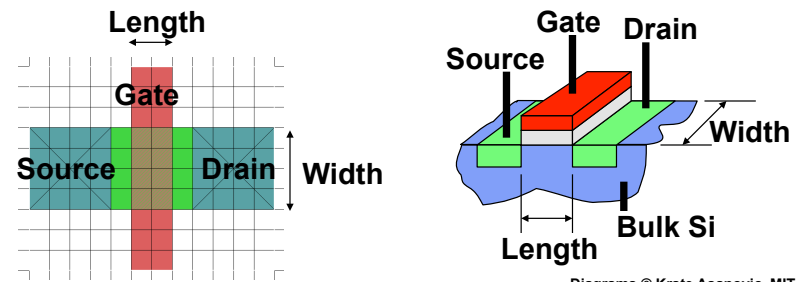

Diagrams © Krste Asanovic, MIT

- **Transistor length**: characteristic of "process generation"
 - "22nm" refers to the transistor gate length
- Each process generation shrinks transistor length by 1.4x
 - "Moore's law" -> roughly 2x improvement transistor density
 - Roughly linear improvement in switching speeds (lower resistance)

Manufacturing Steps

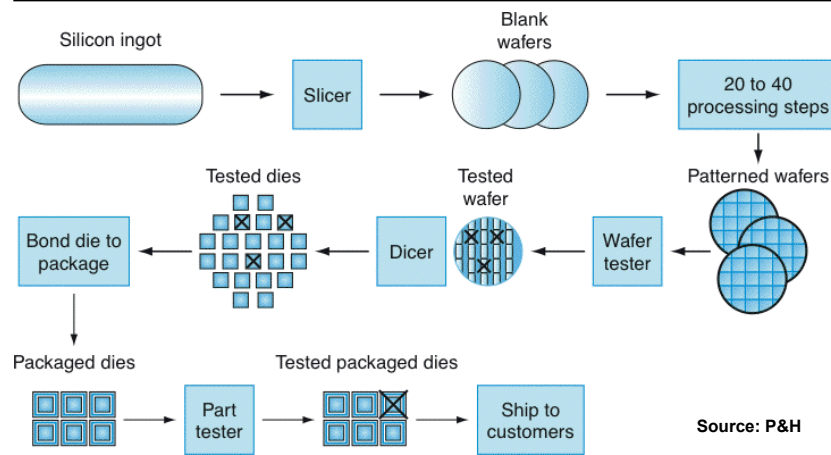


CIS 371 (Martin): Digital Logic & Hardware Description

13

Manufacturing Steps


 
- Multi-step photo-/electro-chemical process
 - More steps, higher unit cost
- + Fixed cost mass production (\$1 million+ for "mask set")



CIS 371 (Martin): Digital Logic & Hardware Description

Integrated Circuit (IC) Costs

- Chips built in multi-step chemical processes on **wafers**
 - Cost / wafer is constant, $f(\text{wafer size, number of steps})$
- Chip (die) cost is related to **area**
 - Larger chips means fewer of them
- Cost is more than linear in area
 - Why? random defects
 - Larger chips means fewer working ones
 - Chip cost \sim chip area $^\alpha$
 - $\alpha = 2$ to 3
- **Wafer yield**: % wafer that is chips
- **Die yield**: % chips that work
- Yield is increasingly non-binary - fast vs slow chips

  


CIS 371 (Martin): Digital Logic & Hardware Description

15

Manufacturing Defects

 
- Defects can arise
 - Under-/over-doping
 - Over-/under-dissolved insulator
 - Mask mis-alignment
 - Particle contaminants
- Try to minimize defects
 - Process margins
 - Design rules
 - Minimal transistor size, separation
- Or, tolerate defects
 - Redundant or "spare" memory cells
 - Can substantially improve yield



CIS 371 (Martin): Digital Logic & Hardware Description


16

Wires

 


- Transistors 1-dimensional for design purposes: **width**
- Wires 4-dimensional: **length, width, height, "pitch"**
 - Longer wires have more resistance (slower)
 - "Thinner" wires have more resistance (slower)
 - Closer wire spacing ("pitch") increases capacitance (slower)

Transistors and Wires

 


Complementary MOS (CMOS)

 - Voltages as values
 - Power (V_{DD}) = "1", Ground = "0"
- Two kinds of MOSFETs
 - **N-transistors**
 - Conduct when gate voltage is 1
 - Good at passing 0s
 - **P-transistors**
 - Conduct when gate voltage is 0
 - Good at passing 1s
- **CMOS**
 - Complementary n-/p- networks form boolean logic (i.e., gates)
 - And some non-gate elements too (important example: RAMs)



Basic CMOS Logic Gate

 
- **Inverter: NOT gate**
 - One p-transistor, one n-transistor
 - Basic operation
 - Input = 0
 - P-transistor closed, n-transistor open
 - Power charges output (1)
 - Input = 1
 - P-transistor open, n-transistor closed
 - Output discharges to ground (0)



Another CMOS Gate Example

- What is this? Look at **truth table**

 
- 0, 0 → 1
- 0, 1 → 1
- 1, 0 → 1
- 1, 1 → 0
- Result: **NAND** (NOT AND)
- NAND is "universal"




CIS 371 (Martin): Digital Logic & Hardware Description

Digital Building Blocks: Logic Gates

 - **Logic gates:** implement Boolean functions
 - Basic gates: NOT, NAND, NOR
 - Underlying CMOS transistors are naturally inverting (○ = NOT)



- NAND, NOR are "Boolean complete"

 

CIS 371 (Martin): Digital Logic & Hardware Description

22


Alternative to Fabrication: FPGA

- We'll use **FPGAs (Field Programmable Gate Array)**
 - Also called Programmable Logic Devices (PLDs)
- An FPGA is a special type of programmable chip
 - Conceptually, contains a grid of gates
 - The wiring connecting them can be reconfigured electrically
 - Using more transistors as switches
 - Once configured, the FPGA can emulate any digital logic design
 - Tool converts **gate-level design** to configuration
- Uses
 - **Hardware prototyping** (what "we" are doing)
 - Low-volume special-purpose hardware
 - New: computational offload

CIS 371 (Martin): Digital Logic & Hardware Description

23

In Our Lab: Digilent XUP-V2P Boards

 

- Program FPGA to run LC4
 - "The project"
- Hook up keyboard And VGA
- Game on!
- Boards have many features
- Use some for debugging
 - LEDs, switches
- Other features
 - Ethernet, flash reader
 - 256MB SDRAM, audio in/out
 - Can boot Linux!

CIS 371 (Martin): Digital Logic & Hardware Description

24

Digital Logic Review

Boolean Functions and Truth Tables

- Any Boolean function can be represented as a truth table
 - Truth table:** point-wise input \rightarrow output mapping
 - Function is disjunction of all rows in which "Out" is 1


A, B, C \rightarrow Out

0, 0, 0 \rightarrow 0
 0, 0, 1 \rightarrow 0
 0, 1, 0 \rightarrow 0
 0, 1, 1 \rightarrow 0
 1, 0, 0 \rightarrow 0
 1, 0, 1 \rightarrow 1
 1, 1, 0 \rightarrow 1
 1, 1, 1 \rightarrow 1

 
- Example above: $Out = AB'C + ABC' + ABC$

Digital Building Blocks: Logic Gates

- Logic gates:** implement Boolean functions
 - Basic gates: NOT, NAND, NOR
 - Underlying CMOS transistors are naturally inverting (\circ = NOT)



- NAND, NOR are "Boolean complete"

 


Truth Tables and PLAs

- Implement Boolean function by implementing its truth table
 - Takes two levels of logic
 - Assumes inputs and inverses of inputs are available (usually are)
 - First level: ANDs (product terms)
 - Second level: ORs (sums of product terms)
- PLA (programmable logic array)**
 - Flexible circuit for doing this

PLA Example

 - PLA with 3 inputs, 2 outputs, and 4 product terms
 - $Out0 = AB'C + ABC' + ABC$



Boolean Algebra

- **Boolean Algebra:** rules for rewriting Boolean functions
 - Useful for simplifying Boolean functions
 - Simplifying = reducing gate count, reducing gate "levels"
 - Rules: similar to logic (0/1 = F/T)
 - **Identity:** $A1 = A$, $A+0 = A$
 - **0/1:** $A0 = 0$, $A+1 = 1$
 - **Inverses:** $(A')' = A$
 - **Idempotency:** $AA = A$, $A+A = A$
 - **Tautology:** $AA' = 0$, $A+A' = 1$
 - **Commutativity:** $AB = BA$, $A+B = B+A$
 - **Associativity:** $A(BC) = (AB)C$, $A+(B+C) = (A+B)+C$
 - **Distributivity:** $A(B+C) = AB+AC$, $A+(BC) = (A+B)(A+C)$
 - **DeMorgan's:** $(AB)' = A'+B'$, $(A+B)' = A'B'$

Logic Minimization

- **Logic minimization**
 - Iterative application of rules to reduce function to simplest form
 - There are tools for automatically doing this

```

Out = AB'C + ABC' + ABC
Out = A(B'C + BC' + BC) // distributivity
Out = A(B'C + (BC' + BC)) // associativity
Out = A(B'C + B(C'+C)) // distributivity (on B)
Out = A(B'C + B1) // tautology
Out = A(B'C + B) // 0/1
Out = A((B'+B)(C+B)) // distributivity (on +B)
Out = A(1(B+C)) // tautology
Out = A(B+C) // 0/1
    
```

Non-Arbitrary Boolean Functions

- PLAs implement Boolean functions point-wise
 - E.g., represent $f(X) = X+5$ as $[0 \rightarrow 5, 1 \rightarrow 6, 2 \rightarrow 7, 3 \rightarrow 8, \dots]$
 - Mainly useful for "arbitrary" functions, no compact representation
- Many useful Boolean functions are not arbitrary
 - Have a compact implementation
 - Examples
 - Multiplexer
 - Adder

Hardware Design Methods


Describing Hardware

- Two general options
 - Schematics
 - Pictures of gates & wires
 - Hardware description languages
 - Use textual descriptions to specify hardware
- Translation process called "synthesis"
 - Textual description -> gates -> full layout
 - Tries to minimize the delay and/or number of gates
 - Much like process of compilation of software

Hardware Design Methodologies

- Fabricating a chip requires a detailed layout
 - All transistors & wires
- How does a hardware designer describe such design?
 - (Bad) Option #1: draw all the masks "by hand"
 - All 1 billion transistors? Umm...
 - Option #2: use computer-aided design (CAD) tools to help
 - Layout done by engineers with CAD tools or automatically
- Design levels – uses **abstraction**
 - **Transistor-level** design – designer specifies transistors (not layout)
 - **Gate-level** design – designer specifies gates, wires (not transistors)
 - **Higher-level** design – designer uses higher-level building blocks
 - Adders, memories, etc.
 - Or logic in terms of and/or/not, and tools translates into gate

Schematics

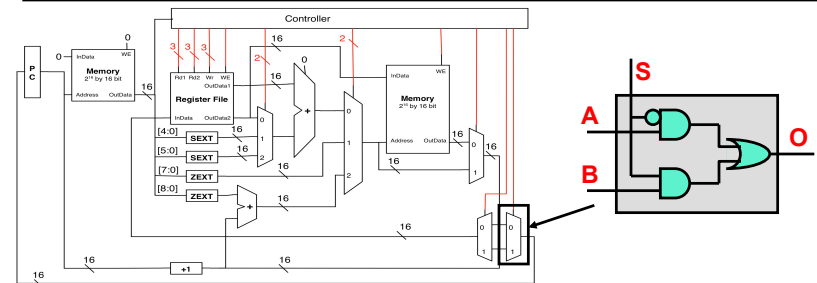

- Draw pictures
 - Use a schematic entry program to draw wires, logic blocks, gates
 - Support hierarchical design (arbitrary nesting)
- + Good match for hardware which is inherently spatial, purty
- Time consuming, "non-scalable" (large designs are unreadable)
- Rarely used in practice ("real-world" designs are big)


Hardware Description Languages (HDLs)

- Write “code” to describe hardware
 - HDL vs. SDL
 - Specify wires, gates, modules (also hierarchical)
 - + Easier to create, edit, modify, scales well
 - Disconnect: must still “think” visually (gets easier with practice)

```


module mux2to1(S, A, B, Out);
  input S, A, B;
  output Out;
  wire S_, AnS_, BnS;

   not (S_, S);
  and (AnS_, A, S_);
  and (BnS, B, S);
  or (Out, AnS_, BnS);
endmodule
    
```



(Hierarchical) HDL Example

 - Build up more complex modules using simpler modules
 - Example: 4-bit wide mux from four 1-bit muxes



```

module mux2to1_4(S, A, B, Out);
  input [3:0] A;
  input [3:0] B;
  input S;
  output [3:0] Out;

  mux2to1 mux0 (S, A[0], B[0], Out[0]);
  mux2to1 mux1 (S, A[1], B[1], Out[1]);
  mux2to1 mux2 (S, A[2], B[2], Out[2]);
  mux2to1 mux3 (S, A[3], B[3], Out[3]);
endmodule
    
```

Verilog HDL

- **Verilog**: HDL we will be using
 - Syntactically similar to C (by design)
 - ± Ease of syntax hides fact that this isn't C (or any SDL)
 - We will use a few lectures to learn Verilog

```

module mux2to1_4(S, A, B, Out);
  input [3:0] A;
  input [3:0] B;
  input S;
  output [3:0] Out;

  mux2to1 mux0 (S, A[0], B[0], Out[0]);
  mux2to1 mux1 (S, A[1], B[1], Out[1]);
  mux2to1 mux2 (S, A[2], B[2], Out[2]);
  mux2to1 mux3 (S, A[3], B[3], Out[3]);
endmodule
    
```

These aren't variables

These aren't function calls

HDLs are not SDLs (PLs)

- Similar in some (intentional) ways ...
 - Syntax
 - Named entities, constants, scoping, etc.
 - Tool chain: synthesis tool analogous to compiler
 - Multiple levels of representation
 - “Optimization”
 - Multiple targets (portability)
 - “Software” engineering
 - Modular structure and parameterization
 - Libraries and code repositories
- ... but different in many others
 - One of the most difficult conceptual leaps of this course

Hardware is not Software

- Just two different beasts (or two parts of the same beast)
 - Things that make sense in hardware, don't in software, vice versa
 - One of the main themes of 371
- **Software is sequential**
 - Hardware is inherently parallel, at multiple levels
 - Have to work to get hardware to *not* do things in parallel
- Software atoms are purely functional ("digital")
 - Hardware atoms have quantitative ("analog") properties too
 - Including correctness properties!
- Software mostly about quality ("functionality")
 - Hardware mostly about quantity: performance, area, power, etc.
- One reason that HDLs are not SDLs

HDL: Behavioral Constructs

- HDLs have **low-level structural** constructs
 - Specify hardware structures directly
 - Transistors, gates (**and**, **not**) and wires, hierarchy via modules
- Also have **mid-level behavioral** constructs
 - Specify operations, not hardware to perform them
 - Low-to-medium-level: **&**, **~**, **+**, *****
- Also **higher-level behavioral** constructs
 - High-level: **if-then-else**, **for** loops
 - Some of these are synthesizable (some are not)
 - Tools try to guess what you want, often highly inefficient
 - Higher-level → more difficult to know what it will synthesize to!
- HDLs are both high- and low-level languages in one!
 - And the boundary is not clear!

HDL: Simulation

- Another use of HDL: simulating & testing a hardware design
 - Cheaper & faster turnaround (no need to fabricate)
 - More visibility into design ("debugger" interface)
- **HDLs have features just for simulation**
 - Higher level data types: integers, FP-numbers, timestamps
 - Higher level control structures: for-loops, conditionals
 - Routines for I/O: error messages, file operations
 - Obviously, **these cannot be synthesized into circuits**
- Also another reason for HDL/SDL confusion
 - HDLs have "SDL" features for simulation

Verilog HDL

HDL History

- 1970s:
 - First HDLs
- Late 1970s: VHDL
 - VHDL = VHSIC HDL = Very High Speed Integrated Circuit HDL
 - VHDL inspired by programming languages of the day (Ada)
- 1980s:
 - Verilog first introduced
 - Verilog inspired by the C programming language
 - VHDL standardized
- 1990s:
 - Verilog standardized (Verilog-1995 standard)
- 2000s:
 - Continued evolution (Verilog-2001 standard)
- Both VHDL and Verilog evolving, still in use today

Verilog HDL

- Verilog is a (surprisingly) big language
 - Structural constructs at both gate and transistor level
 - Facilities for specifying memories
 - Precise timing specification and simulation
 - Lots of “behavioral” constructs
 - C-style procedural variables, including arrays
 - A pre-processor
 - VPI: Verilog programming interface
 - ...

371 Verilog HDL

- **We’re going to learn a focused *subset* of Verilog**
 - Focus on synthesizable constructs
 - Focus on avoiding subtle synthesis errors
 - Use as an educational tool
- For synthesis
 - Structural constructs at gate-level only
 - A few behavioral constructs
- Some testing and debugging features

Rule 1: if you haven’t seen it in lecture, you can’t use it!

Rule 1a: when in doubt, ask!

Basic Verilog Syntax

- Have already seen basic syntax, looks like C
 - C/C++/Java style comments
 - Names are case sensitive, and can use _ (underscore)
 - Avoid: clock, clk, power, pwr, ground, gnd, vdd, vcc, init, reset, rst
 - Some of these are “special” and will silently cause errors


```
/* this is a module */
module mux2to1(S, A, B, Out);
    input S, A, B;
    output Out;
    wire S_, AnS_, BnS;
    // these are gates
    not (S_, S);
    and (AnS_, A, S_);
    and (BnS, B, S);
    or (Out, AnS_, BnS);
endmodule
```

(Gate-Level) Structural Verilog

- Primitive “data type”: **wire**
 - Have to declare it

Structural
 
```
module mux2to1(S, A, B, Out);
input S, A, B;
output Out;
wire S_, AnS_, BnS;
not (S_, S);
and (AnS_, A, S_);
and (BnS, B, S);
or (Out, AnS_, BnS);
endmodule
```




(Gate-Level) Structural Verilog

- Primitive “operators”: gates
 - Specifically: **and, or, xor, nand, nor, xnor, not, buf**
 - Can be multi-input: e.g., **or (C, A, B, D)** (C= A+B+D)
 - “Operator” **buf** just repeats input signal (may amplify it)

Structural
 
```
module mux2to1(S, A, B, Out);
input S, A, B;
output Out;
wire S_, AnS_, BnS;
not (S_, S);
and (AnS_, A, S_);
and (BnS, B, S);
or (Out, AnS_, BnS);
endmodule
```




(Gate-Level) Behavioral Verilog

- Primitive “operators”: boolean operators
 - Specifically: **&, |, ^, ~**
 - Can be combined into expressions
 - Can be mixed with structural Verilog

“Behavioral” (Synthesizable)

```
module mux2to1(S, A, B, Out);
input S, A, B;
output Out;
wire S_, AnS_, BnS;
assign S_ = ~S;
assign AnS_ = A & S_;
assign BnS = B & S;
assign Out = AnS_ | BnS;
endmodule
```

 


Wire Assignment

- **Wire assignment:**
 - Connect combinational logic block or other wire to wire input
 - **Order of statements not important**, executed totally in parallel
 - When right-hand-side changes, it is re-evaluated and re-assigned
 - Designated by the keyword **assign**

“Behavioral” (Synthesizable)

```
module mux2to1(S, A, B, Out);
input S, A, B;
output Out;
wire S_, AnS_, BnS;
assign S_ = ~S;
assign AnS_ = A & S_;
assign BnS = B & S;
assign Out = AnS_ | BnS;
endmodule
```

 


Wire Assignment

- Assignment can be combined with declaration

```
wire c = a | b;
```

“Behavioral” (Synthesizable)

```
module mux2to1(S, A, B, Out);  
  input S, A, B;  
  output Out;  
  
  wire S_ = ~S;  
  wire AnS_ = A & S_  
  wire BnS = B & S;  
  assign Out = AnS_ | BnS;  
endmodule
```

 


(Gate-Level) Behavioral Verilog

- Primitive “operators”: boolean operators
 - Specifically: $\&$, $|$, \wedge , \sim
 - Can be combined into expressions**
 - Can be mixed with structural Verilog

“Behavioral” (Synthesizable)

```
module mux2to1(S, A, B, Out);  
  input S, A, B;  
  output Out;  
  
  assign Out = (~S & A) | (S & B);  
endmodule
```

 


Easiest Way to do a Mux?

- Verilog supports $?:$ conditional assignment operator
 - Much more useful (and common) in Verilog than in C/Java

“Behavioral” (Synthesizable)
 
```
module mux2to1(S, A, B, Out);  
  input S, A, B;  
  output Out;  
  
  assign Out = S ? B : A;  
endmodule
```



Wires Are Not C-like Variables!

- Order of assignment doesn't matter

```
module mux2to1(S, A, B, Out);  
  input S, A, B;  
  output Out;  
  wire S_, AnS_, BnS;  
  assign Out = AnS_ | BnS;  
  assign BnS = B & S;  
  assign AnS_ = A & S_  
  assign S_ = ~S;  
endmodule
```

- Can't “reuse” a wire

```
assign temp = a & b;  
assign temp = a | b;
```

- Actually, you can; but doesn't do what you think it does

Wire Vectors

- Wire vectors: also called “arrays” or “buses”

```
wire [7:0] w1; // 8 bits, w1[7] is most significant bit
wire [0:7] w2; // 8 bits, w2[0] is most significant bit
```

- Example:

```
module 8bit_mux2to1 (S, A, B, Out);
  input S;
  input [7:0] A, B;
  output [7:0] Out;
  assign Out = S ? B : A;
endmodule
```

Unlike C, array range is part of type, not variable!

- Operations

- Bit select: `vec[3]`
- Range select: `vec[3:2]`
- Concatenate: `assign vec = {x, y, z};`

Gate-Level Vector Operators

- Verilog also supports behavioral vector operators

- **Logical bitwise and reduction:** `~, &, |, ^`

```
wire [7:0] vec1, vec2;
wire [7:0] vec3 = vec1 & vec2; // bitwise AND
wire w1 = ~|vec1; // NOR reduction
```

- **Integer arithmetic comparison:** `+, -, *, /, %, ==, !=, <, >`

```
wire [7:0] vec4 = vec1 + vec2; // vec1 + vec2
```

- Important: all arithmetic is unsigned, want signed? “roll your own”
- Good: in signed/unsigned integers: `+`, `-`, `*` produces same output
 - Just a matter of interpretation
- Bad: in signed/unsigned integers: `/`, `%` is not the same
- Ugly: Xilinx will not synthesize `/`, `%` anyway!
 - Our LC4 won’t support DIV and MOD instructions

Repeated Signals

- Concatenation

```
wire vec[2:0] = {x, y, z};
```

- Can also repeat a signal n times

```
wire vec[15:0] = {16{x}}; // 16 copies of x
```

- Example uses (what does this do?):

```
wire [7:0] out;
wire [3:0] A;
assign out = {{4{1'd0}}, A[3:0]};
```

- What about this?

```
assign out = {{4{A[3]}}, A[3:0]};
```

Why Use a High-Level Operator?

- Abstraction

- Why write assembly, when you can write C? (not a great example)

- Take advantage of built-in high level implementation

- Virtex-IIPro FPGAs have integer multipliers on them
- Xilinx will use these rather than synthesizing a multiplier from gates
 - Much faster and more efficient
- How hard is it for Xilinx to figure out you were doing a multiply?
 - If you use “*”: easy
 - If you “roll your own” using gates: nearly impossible

- Why *not* use high-level operators?

- Less certain what they will synthesize to
- Or even if it will synthesize at all: e.g., `/`, `%`

Wire and Wire Vector Constants

```
wire [3:0] w = 4'b0101;
```

- The "4" is the number of bits
- The "b" means "binary" - "h" for hex, "o" for octal, "d" for decimal
- The "0101" are the digits (in binary in this case)

```
wire [3:0] w = 4'd5; // same thing, effectively
```

- Here is a single wire constant

```
wire w = 1'b0;
```

- A useful example of wire-vector constants:

```
module mux4to1(Sel, A, B, C, D, Out);  
  input [1:0] Sel;  
  input A, B, C, D;  
  output Out = (Sel == 2'd0) ? A :  
               (Sel == 2'd1) ? B :  
               (Sel == 2'd2) ? C : D;  
endmodule
```

Hierarchical Design using Modules

- Interface specification

```
module mux2to1(Sel, A, B, Out);  
  input Sel, A, B;  
  output Out;
```

- Can also have `inout`: bidirectional wire (we will not need)

- Alternative: Verilog 2001 interface specification

```
module mux2to1(input Sel, A, B, output Out);
```

- Declarations

- Internal wires, i.e., "locals"
- Wires also known as "nets" or "signals"

```
wire S_, AnS_, BnS;
```

- Implementation: primitive and module instantiations

```
and (AnS_, A, S_);
```

Verilog Module Example

```
module mux2to1(S, A, B, O);
```

```
  input S, A, B;
```

```
  output O;
```

```
  wire S_, AnS_, BnS;
```

```
  not (S_, S);
```


```
  and (AnS_, A, S_);
```

```
  and (BnS_, B, S);
```

```
  or (O, AnS_, BnS);
```

```
endmodule
```

 - Instantiation: `mux2to1 mux0 (cond, in1, in2, out);`
 - Non-primitive module instances must be named (helps debugging)
- Operators and expressions can be used with modules
 - `mux2to1 mux0 (cond1 & cond2, in1, in2, out);`



Hierarchical Verilog Example

- Build up more complex modules using simpler modules
- Example: 4-bit wide mux from four 1-bit muxes
 - Again, just "drawing" boxes and wires

```
module mux2to1_4(Sel, A, B, O);
```

```
  input [3:0] A;
```

```
  input [3:0] B;
```

```
  input Sel;
```

```
  output [3:0] O;
```

```
  mux2to1 mux0 (Sel, A[0], B[0], O[0]);
```

```
  mux2to1 mux1 (Sel, A[1], B[1], O[1]);
```

```
  mux2to1 mux2 (Sel, A[2], B[2], O[2]);
```

```
  mux2to1 mux3 (Sel, A[3], B[3], O[3]);
```

```
endmodule
```

Connections by Name

- Can (should?) specify module connections by name

- Helps keep the bugs away

- Example

```
mux2to1 mux0 (.S(Sel), .A(A[0]), .B(B[0]), .O(O[0]));
```

- Also, then order doesn't matter

```
mux2to1 mux1 (.A(A[1]), .B(B[1]), .O(O[1]), .S(Sel));
```

Per-Instance Module Parameters

- Module parameters: useful for defines varying bus widths
 - But for widths, not "types" (in HDL "width" == "type")

```
module Nbit_mux2to1 (Sel, A, B, Out);  
    parameter N = 1;  
    input [N-1:0] A, B;  
    input Sel;  
    output [N-1:0] Out;  
    assign Out = Sel ? B : A;  
endmodule
```

- Two ways to instantiate: implicit

```
Nbit_mux2to1 #(4) mux1 (S, in1, in2, out);
```

- And explicit

```
Nbit_mux2to1 mux1 (S, in1, in2, out);
```

```
defparam mux1.N = 4;
```

- Multiple parameters per module allowed

Verilog Pre-Processor

- Like the C pre-processor

- But uses ` (back-tick) instead of #

- Constants: ``define`

- No parameterized macros

- Use ` before expanding constant macro

```
`define letter_A 8'h41
```

```
wire w[7:0] = `letter_A;
```

- Conditional compilation: ``ifdef`, ``endif`

- File inclusion: ``include`

- Parameter vs ``define`

- Parameter only for "per instance" constants


- ``define` for "global" constants

Sequential Logic

Two Types of Digital Circuits


- **Combinational Logic**
 - Logic **without state** variables
 - Examples: adders, multiplexers, decoders, encoders
 - **No clock involved**
- **Sequential Logic**
 - Logic **with state** variables
 - State variables: latches, flip-flops, registers, memories
 - **Clocked**
 - State machines, multi-cycle arithmetic, processors
- **Sequential Logic in Verilog**
 - Special idioms using behavioral constructs that synthesize into latches, memories

Sequential Logic & Synchronous Systems

 

- Processors are complex fine state machines (FSMs)
 - Combinational (compute) blocks separated by storage elements
 - State storage: memories, registers, etc.
- **Synchronous systems**
 - **Clock**: global signal acts as write enable for all storage elements
 - Typically marked as triangle
 - All state elements write together, values move forward in lock-step
 - + Simplifies design: design combinational blocks independently
- **Aside: asynchronous systems**
 - Same thing, but ... no clock
 - Values move forward using explicit handshaking
 - ± May have some advantages, but difficult to design


Datapath Storage Elements

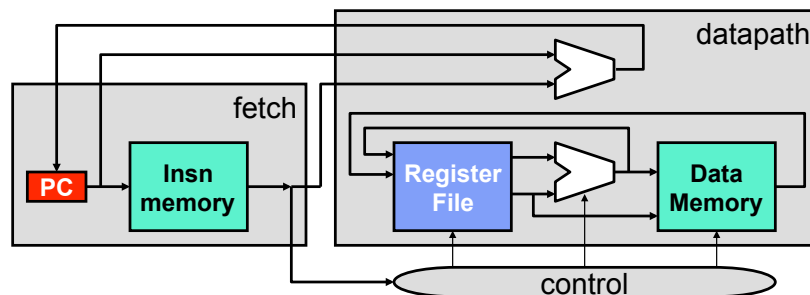

- Three main types of storage elements
 - **Singleton registers**: PC
 - **Register files**: ISA registers
 - **Memories**: insn/data memory

Cross-Coupled Inverters (CCIs)

 - **Cross-coupled inverters (CCIs)**
 - **Primitive "storage element" for storing state**
 - Most storage arrays (regfile, caches) implemented this way
 - Where is the input and where is the output?




S-R Latch

- **S-R (set-reset) latch**

- Cross-coupled NOR gates
- Distinct inputs/outputs

S, R	Q
0, 0	old Q
0, 1	0
1, 0	1
1, 1	0

 

- S=0, R=0? circuit degenerates to cross-coupled INVs
- S=1, R=1? not very useful
- Not really used ... except as component in something else

D Latch


- **D latch:** S-R latch + ...

- control that makes S=R=1 impossible

E, D	Q
0, 0	old Q
0, 1	old Q
1, 0	0
1, 1	1


- In other words

0, D	old Q
1, D	D
- In words
 - When E is 1, Q gets D
 - When E is 0, Q retains old value

 


Timing Diagrams

 - Voltage {0,1} diagrams for different nodes in system
 - "Digitally stylized": changes are vertical lines (instantaneous?)
 - Reality is analog, changes are continuous and smooth
- Timing diagram for a D latch



Triggering: Level vs. Edge


 


- The D-latch is **level-triggered**
 - The latch is open for writing as long as E is 1
 - If D changes continuously, so does Q
 - May not be the functionality we want
- Often easier to reason about an **edge-triggered** latch
 - The latch is open for writing only on E transition (0 → 1 or 1 → 0)
 - + Don't need to worry about fluctuations in value of D

D Flip-Flop

D Flip-Flop:

  - Sequential D-latches
- Enabled by inverse signals
- First latch open when $E = 0$
- Second latch open when $E = 1$
- Overall effect?
 - D flipflop latches D on $0 \rightarrow 1$ transition
- E is the "clock" signal input




CIS 371 (Martin): Digital Logic & Hardware Description

81

FF_{WE} : FF with Separate Write Enable

FF_{WE} : FF with separate write enable

 - FF D(ata) input is MUX of D and Q, WE selects




- Bad idea: why not just AND the CLK and WE?
 - + Fewer gates
 - Creates timing problems
 - Do not try to do logic on CLK in Verilog
 - No, really. Never do this.

CIS 371 (Martin): Digital Logic & Hardware Description

82

N-bit Register

 

- **Register**: one n -bit storage word
 - Non-multiplexed input/output: data buses write/read same word
- Implementation: FF_{WE} array with shared write-enable (WE)
 - FFs written on CLK edge if WE is 1 (or if there is no WE)

CIS 371 (Martin): Digital Logic & Hardware Description

83


Sequential Logic in Verilog

CIS 371 (Martin): Digital Logic & Hardware Description

84

Designing Sequential Logic

 - CIS371 design rule: separate combinational logic from sequential state elements
 - Not enforced by Verilog, but a very good idea
 - Possible exceptions: counters, shift registers
- We'll give you a flip-flop module (see next slide)
 - Edge-triggered, not a transparent latch
 - Parameterized to create a n -bit register
- Example use: state machine




CIS 371 (Martin): Digital Logic & Hardware Description

85

Sequential Logic In Verilog

- How are state-holding variables specified in Verilog?
 - First instinct: structurally
 - After all, real latches and flip-flops are made from gates...

```
module latch(out, in, we);
    output out; input in, we;
    wire not_out = ~(out | (we & ~in));
    assign out = ~(not_out | (we & in));
endmodule
```

 

- This should work, right? RIGHT?

- Logically, yes... in practice, no
 - Storage elements are highly analog
 - FPGAs have dedicated storage

CIS 371 (Martin): Digital Logic & Hardware Description

86

Verilog Flipflop (Behavioral Magic)

- How do we specify state-holding constructs in Verilog?

```
module dff (out, in, wen, rst, clk);
```

```
    output out;
    input in;
    input wen, rst, clk;
```

```
    wen = write enable
    rst = reset
    clk = clock
```

```
    reg out;
    always @(posedge clk)
    begin
        if (rst)
            out = 0;
        else if (wen)
            out = in;
    end
```

- **reg**: interface-less storage bit
- **always @ ()**: synthesizable behavioral sequential Verilog
 - Tricky: hard to know exactly what it will synthesize to
 - **We will give this to you, don't write your own**
 - "Creativity is a poor substitute for knowing what you're doing"

```
endmodule
```

CIS 371 (Martin): Digital Logic & Hardware Description

87

Verilog Register (Behavioral Magic)

- How do we specify state-holding constructs in Verilog?

```
module register (out, in, wen, rst, clk);
```

```
    parameter n = 1;
    output [n-1:0] out;
    input [n-1:0] in;
    input wen, rst, clk;
```

```
    wen = write enable
    rst = reset
    clk = clock
```

```
    reg [n-1:0] out;
    always @(posedge clk)
    begin
        if (rst)
            out = 0;
        else if (wen)
            out = in;
    end
```

- **reg**: interface-less storage bit
- **always @ ()**: synthesizable behavioral sequential Verilog
 - Tricky: hard to know exactly what it will synthesize to
 - **We will give this to you, don't write your own**
 - "Creativity is a poor substitute for knowing what you're doing"

```
endmodule
```

CIS 371 (Martin): Digital Logic & Hardware Description


88

Clocks Signals

- Clocks & reset signals are **not** normal signals
- Travel on dedicated “clock” wires
 - Reach all parts of the chip
 - Special “low-skew” routing
- Ramifications:
 - Never do logic operations on the clocks
 - If you want to add a “write enable” to a flip-flop:
 - Use a mux to route the old value back into it
 - (or use the flip-flop with write enable we give you!)
 - Do not just “and” the write-enable signal with the clock!
- Messing with the clock can cause a errors
 - Often can only be found using detail low-level simulation

Simulation

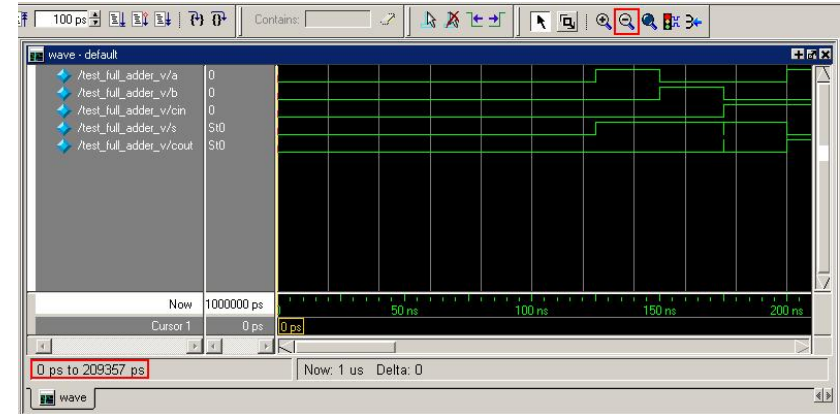- One way to test and debug designs
- Graphical output via waveforms



Testbenches

- A more effective way to test & debug designs
- In C/Java?
 - Write test code in C/Java to test C/Java
 - “Test harness”, “unit testing”
- For Verilog/VHDL?
 - Write test code in Verilog to test Verilog
 - Verilog has advanced “behavioral” commands to facilitate this:
 - Delay for n units of time
 - Full high-level constructs: if, while, sequential assignment, ints
 - Input/output: file I/O, output to display, etc.


Common Errors

- Tools are from a less gentle time
 - More like C, less like Java
 - Assume that you mean what you say
- Common errors:
 - Not assigning a wire a value
 - Assigning a wire a value more than once
 - Implicit wire declarations (default to type “wire” 1-bit wide)
- Avoid names such as:
 - clock, clk, power, pwr, ground, gnd, vdd, vcc, init, reset, rst
 - Some of these are “special” and will silently cause errors

Additional Verilog Resources

- Elements of Logic Design Style by Shing Kong, 2001
 - Dos, do-nots, tips
 - <http://www.cis.upenn.edu/~milom/elements-of-logic-design-style/>
- Verilog HDL Synthesis: A Practical Primer
 - By J. Bhasker, 1998
 - To the point (<200 pages)
- Advanced Digital Design with the Verilog HDL
 - By Michael D. Ciletti, 2003
 - Verilog plus lots of digital logic design (~1000 pages)
- Verilog tutorial from textbook (posted on course web page)

Summary

 

- Transistors & fabrication
- Digital logic basics
 - Focus on useful components
- Hardware design methods
 - Introduction to Verilog
- Next unit: single-cycle datapath