

CIS 371 Computer Organization and Design


Unit 3: Arithmetic

Based on slides by Prof. Amir Roth & Prof. Milo Martin

Readings

- P&H
 - Chapter 3
 - You can skim Section 3.5 (Floating point)

This Unit: Arithmetic

 

- A little review
 - Binary + 2s complement
 - Ripple-carry addition (RCA)
- Fast integer addition
 - Carry-select (CSeA)
- Shifters
- Integer multiplication and division
- Floating point arithmetic

Pre-Class Exercise

Add:


$$\begin{array}{r} 43 = 00101011 \\ + 29 = 00011101 \\ \hline \end{array}$$

$$\begin{array}{r} 19 = 010011 \\ * 12 = 001100 \\ \hline \end{array}$$

Divide:

$$3 \overline{)29} = 0011 \overline{)011101}$$

The Importance of Fast Arithmetic

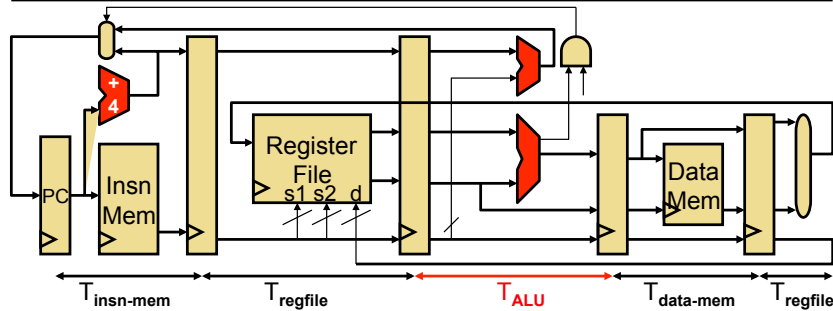

- Addition of two numbers is most common operation
 - Programs use addition frequently
 - Loads and stores use addition for address calculation
 - Branches use addition to test conditions and calculate targets
 - All insns use addition to calculate default next PC
- Fast addition critical to high performance

Review: Binary Integers

- Computers represent integers in binary (base2)
 - 3 = 11, 4 = 100, 5 = 101, 30 = 11110
 - + Natural since only two values are represented
 - Addition, etc. take place as usual (carry the 1, etc.)

$$\begin{array}{r} 17 = 10001 \\ +5 = 101 \\ \hline 22 = 10110 \end{array}$$

- Some old machines use decimal (base10) with only 0/1
 - 30 = 011 000
 - Unnatural for digital logic, implementation complicated & slow

Fixed Width

- On pencil and paper, integers have infinite width
- In hardware, integers have **fixed width**
 - N bits: 16, 32 or 64
 - LSB is 2^0 , MSB is 2^{N-1}
 - **Range:** 0 to 2^N-1
 - Numbers $>2^N$ represented using multiple fixed-width integers
 - In software

What About Negative Integers?

- **Sign/magnitude**
 - Unsigned plus one bit for sign
 - 10 = 00001010, -10 = 10001010
 - + Matches our intuition from "by hand" decimal arithmetic
 - Both 0 and -0
 - Addition is difficult
 - Range: $-(2^{N-1}-1)$ to $2^{N-1}-1$
- Option II: **two's complement (2C)**
 - Leading 0s mean positive number, leading 1s negative
 - 10 = 00001010, -10 = 11110110
 - + One representation for 0
 - + Easy addition
 - Range: $-(2^{N-1})$ to $2^{N-1}-1$

The Tao of 2C

- How did 2C come about?
 - "Let's design a representation that makes addition easy"
 - Think of subtracting 10 from 0 by hand
 - Have to "borrow" 1s from some imaginary leading 1

$$\begin{array}{r} 0 = 100000000 \\ -10 = \underline{00001010} \\ -10 = 011110110 \end{array}$$

- Now, add the conventional way...

$$\begin{array}{r} -10 = 11110110 \\ +10 = \underline{00001010} \\ 0 = 100000000 \end{array}$$

Addition

Still More On 2C

- What is the interpretation of 2C?
 - Same as binary, except **MSB represents -2^{N-1}** , not 2^{N-1}
 - $-10 = 11110110 = -2^7 + 2^6 + 2^5 + 2^4 + 2^2 + 2^1$
 - + Extends to any width
 - $-10 = 110110 = -2^5 + 2^4 + 2^2 + 2^1$
 - Why? $2^N = 2 * 2^{N-1}$
 - $-2^5 + 2^4 + 2^2 + 2^1 = (-2^6 + 2 * 2^5) - 2^5 + 2^4 + 2^2 + 2^1 = -2^6 + 2^5 + 2^4 + 2^2 + 2^1$
- Trick to negating a number quickly: **$-B = B' + 1$**
 - $-(1) = (0001)' + 1 = 1110 + 1 = 1111 = -1$
 - $-(-1) = (1111)' + 1 = 0000 + 1 = 0001 = 1$
 - $-(0) = (0000)' + 1 = 1111 + 1 = 0000 = 0$
 - Think about why this works

1st Grade: Decimal Addition

$$\begin{array}{r} 1 \\ 43 \\ +29 \\ \hline 72 \end{array}$$

- Repeat N times
 - Add least significant digits and any overflow from previous add
 - Carry "overflow" to next addition
 - **Overflow**: any digit other than least significant of sum
 - Shift two addends and sum one digit to the right
- Sum of two N-digit numbers can yield an N+1 digit number

Binary Addition: Works the Same Way

```

  1   111111
 43 = 00101011
+29 = 00011101
-----
 72 = 01001000
  
```


- Repeat N times
 - Add least significant bits and any overflow from previous add
 - Carry the overflow to next addition
 - Shift two addends and sum one bit to the right
- Sum of two N-bit numbers can yield an N+1 bit number
- More steps (smaller base)
- Each one is simpler (adding just 1 and 0)
 - So simple we can do it in hardware

The Half Adder

- How to add two binary integers in hardware?
- Start with adding two bits
 - When all else fails ... look at truth table

A	B	CO	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 
- $S = A \oplus B$
- $CO \text{ (carry out)} = AB$
- This is called a **half adder**



The Other Half

- We could chain half adders together, but to do that...
 - Need to incorporate a carry out from previous adder


C	A	B	CO	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

- $S = C'A'B + C'AB' + CA'B' + CAB = C \oplus A \oplus B$
- $CO = C'AB + CA'B + CAB' + CAB = CA + CB + AB$
- This is called a **full adder**

Ripple-Carry Adder

 - N-bit **ripple-carry** adder
 - N 1-bit full adders "chained" together
 - $CO_0 = CI_1, CO_1 = CI_2, \text{ etc.}$
 - $CI_0 = 0$
 - CO_{N-1} is carry-out of entire adder
 - $CO_{N-1} = 1 \rightarrow \text{"overflow"}$
- Example: 16-bit ripple carry adder
 - How fast is this?
 - How fast is an N-bit ripple-carry adder?




Quantifying Adder Delay

- Combinational logic dominated by gate (transistor) delays
 - Array storage dominated by wire delays
 - Longest delay or “critical path” is what matters
- Can implement any combinational function in “2” logic levels
 - 1 level of AND + 1 level of OR (PLA)
 - NOTs are “free”: push to input (DeMorgan’s) or read from latch
 - Example: delay(FullAdder) = 2
 - $d(\text{CarryOut}) = \text{delay}(AB + AC + BC)$
 - $d(\text{Sum}) = d(A \wedge B \wedge C) = d(AB'C' + A'BC' + ABC' + ABC) = 2$
 - Note '^' means Xor (just like in C & Java)
- Caveat: “2” assumes gates have few (<8 ?) inputs

Fast Addition

Ripple-Carry Adder Delay

 - Longest path is to CO_{15} (or S_{15})
 - $d(CO_{15}) = 2 + \text{MAX}(d(A_{15}), d(B_{15}), d(CI_{15}))$
 - $d(A_{15}) = d(B_{15}) = 0, d(CI_{15}) = d(CO_{14})$
 - $d(CO_{15}) = 2 + d(CO_{14}) = 2 + 2 + d(CO_{13}) \dots$
 - **$d(CO_{15}) = 32$**
- **$D(CO_{N-1}) = 2N$**
 - **Too slow!**
 - **Linear in number of bits**
- Number of gates is also linear



Bad idea: a PLA-based Adder?


- If any function can be expressed as two-level logic...
 - ...why not use a PLA for an entire 8-bit adder?
- Not small
 - Approx. 2^{15} AND gates, each with 2^{16} inputs
 - Then, 2^{16} OR gates, each with 2^{16} inputs
 - Number of gates **exponential in bit width!**
- Not that fast, either
 - An AND gate with 65 thousand inputs != 2-input AND gate
 - Many-input gates made a tree of, say, 4-input gates
 - 16-input gates would have at least 8 logic levels
 - So, at least 16 levels of logic for a 16-bit PLA
 - Even so, delay is still **logarithmic in number of bits**
- There are better (faster, smaller) ways

Theme: Hardware != Software

- Hardware can do things that software fundamentally can't
 - And vice versa (of course)
- In hardware, it's easier to trade **resources** for **latency**
- One example of this: **speculation**
 - Slow computation is waiting for some slow input?
 - Input one of two things?
 - **Compute with both (slow), choose right one later (fast)**
- Does this make sense in software? Not on a uni-processor
- Difference? hardware is parallel, software is sequential


Carry-Select Adder

 - **Carry-select adder**
 - Do $A_{15-8} + B_{15-8}$ twice, once assuming C_8 (CO_7) = 0, once = 1
 - Choose the correct one when CO_7 finally becomes available
 - + Effectively cuts carry chain in half (break critical path)
 - But adds mux
 - Delay?



Multi-Segment Carry-Select Adder

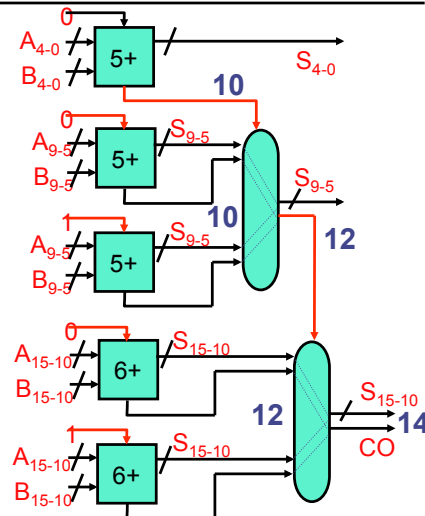- Multiple segments
 - Example: 5, 5, 6 bit = 16 bit
- Hardware cost
 - Still mostly linear ($\sim 2x$)
 - Compute each segment with 0 and 1 carry-in
 - Serial mux chain
- Delay
 - 5-bit adder (10) + Two muxes (4) = 14



Carry-Select Adder Delay


- What is carry-select adder delay (two segment)?
 - $d(CO_{15}) = \text{MAX}(d(CO_{15-8}), d(CO_{7-0})) + 2$
 - $d(CO_{15}) = \text{MAX}(2*8, 2*8) + 2 = \mathbf{18}$
 - In general: $\mathbf{2*(N/2) + 2 = N+2}$ (vs $\mathbf{2N}$ for RCA)
- What if we cut adder into 4 equal pieces?
 - Would it be $2*(N/4) + 2 = 10$? Not quite
 - $d(CO_{15}) = \text{MAX}(d(CO_{15-12}), d(CO_{11-0})) + 2$
 - $d(CO_{15}) = \text{MAX}(2*4, \text{MAX}(d(CO_{11-8}), d(CO_{7-0}))) + 2 + 2$
 - $d(CO_{15}) = \text{MAX}(2*4, \text{MAX}(2*4, \text{MAX}(d(CO_{7-4}), d(CO_{3-0}))) + 2) + 2 + 2$
 - $d(CO_{15}) = \text{MAX}(2*4, \text{MAX}(2*4, \text{MAX}(2*4, 2*4) + 2) + 2) + 2$
 - $d(CO_{15}) = 2*4 + 3*2 = \mathbf{14}$
- N-bit adder in M equal pieces: $\mathbf{2*(N/M) + (M-1)*2}$
 - 16-bit adder in 8 parts: $2*(16/8) + 7*2 = \mathbf{18}$

Another Option: Carry Lookahead

- Is carry-select adder as fast as we can go?
 - Nope
- Another approach to using additional resources
 - Instead of redundantly computing sums assuming different carries
 - Use redundancy to compute carries more quickly
 - This approach is called **carry lookahead (CLA)**

Carry Lookahead Adder (CLA)

 - Calculate "propagate" and "generate" based on A, B
 - Not based on carry in
- Combine with tree structure
- Prior years: CLA covered in great detail
 - Dozen slides or so
 - Not this year
- Take aways
 - **Tree gives logarithmic delay**
 - Reasonable area



Adders In Real Processors

- Real processors super-optimize their adders
 - Ten or so different versions of CLA
 - Highly optimized versions of carry-select
 - Other gate techniques: carry-skip, conditional-sum
 - Sub-gate (transistor) techniques: Manchester carry chain
 - Combinations of different techniques
 - Alpha 21264 used CLA+CSeA+RippleCA
 - Used a different levels
- Even more optimizations for incrementers
 - Why?


 


FIG 10.47 Area vs. delay of synthesized adders

Subtraction: Addition's Tricky Pal

 - Sign/magnitude subtraction is mental reverse addition
 - 2C subtraction **is** addition
- How to subtract using an adder?
 - `sub A B = add A -B`
 - Negate B before adding (fast negation trick: $-B = B' + 1$)
- Isn't a subtraction then **a negation and two additions**?
 - + No, an adder can implement $A+B+1$ by setting the carry-in to 1



Shifts & Rotates

Shift and Rotation Instructions




- Left/right shifts are useful...
 - Fast multiplication/division by small constants (next)
 - Bit manipulation: extracting and setting individual bits in words
- Right shifts
 - Can be **logical** (shift in 0s) or **arithmetic** (shift in copies of MSB)
 - `srl 110011, 2 = 001100`
 - `sra 110011, 2 = 111100`
 - Caveat: `sra` is not equal to division by 2 of negative numbers
- Rotations are less useful...
 - But almost "free" if shifter is there
 - MIPS and LC4 have only shifts, x86 has shifts and rotations

Compiler Opt: Strength Reduction

- **Strength reduction**: compilers will do this (sort of)
 - $A * 4 = A \ll 2$
 - $A * 5 = (A \ll 2) + A$
 - $A / 8 = A \gg 3$ (only if A is unsigned)
- Useful for address calculation: all basic data types are 2^M in size
 - `int A[100];`
 - $\&A[N] = A + (N * \text{sizeof}(\text{int})) = A + N * 4 = A + N \ll 2$

A Simple Shifter

  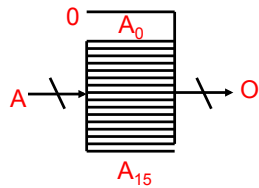
- The simplest 16-bit shifter: can only shift left by 1
 - Implement using wires (no logic!)**
- Slightly more complicated: can shift left by 1 or 0
 - Implement using wires and a multiplexor (mux16_2to1)



Multiplication

Barrel Shifter

 - What about shifting left by any amount 0–15?
 - 16 consecutive “left-shift-by-1-or-0” blocks?
 - Would take too long (how long?)
 - Barrel shifter:** 4 “shift-left-by-X-or-0” blocks (X = 1,2,4,8)
 - What is the delay?



- Similar barrel designs for right shifts and rotations

3rd Grade: Decimal Multiplication

$$\begin{array}{r}
 19 \quad // \text{ multiplicand} \\
 * 12 \quad // \text{ multiplier} \\
 \hline
 38 \\
 + 190 \\
 \hline
 228 \quad // \text{ product}
 \end{array}$$

- Start with product 0, repeat steps until no multiplier digits
 - Multiply multiplicand by least significant multiplier digit
 - Add to product
 - Shift multiplicand one digit to the left (multiply by 10)
 - Shift multiplier one digit to the right (divide by 10)
- Product of N-digit, M-digit numbers may have N+M digits

Binary Multiplication: Same Refrain

```

19 =      010011 // multiplicand
* 12 =     001100 // multiplier
-----
0 = 000000000000
0 = 000000000000
76 = 000001001100
152 = 000010011000
0 = 000000000000
+ 0 = 000000000000
-----
228 = 000011100100 // product
    
```

± Smaller base → more steps, each is simpler

- Multiply multiplicand by **least significant multiplier digit**
+ 0 or 1 → no actual multiplication, add multiplicand or not
- Add to total: we know how to do that
- Shift multiplicand left, multiplier right by one digit


Software Multiplication

- Can implement this algorithm in software
- Inputs: `md` (multiplicand) and `mr` (multiplier)

```


int pd = 0; // product
int i = 0;
for (i = 0; i < 16 && mr != 0; i++) {
    if (mr & 1) {
        pd = pd + md;
    }
    md = md << 1; // shift left
    mr = mr >> 1; // shift right
}
    
```

Hardware Multiply: Iterative

 


- **Control:** repeat 16 times
 - If least significant bit of multiplier is 1...
 - Then add multiplicand to product
 - Shift multiplicand left by 1
 - Shift multiplier right by 1

Hardware Multiply: Multiple Adders

 


- Multiply by N bits at a time using N adders
 - Example: $N=5$, terms (P =product, C =multiplicand, M =multiplier)
 - $P = (M[0] ? (C) : 0) + (M[1] ? (C<<1) : 0) + (M[2] ? (C<<2) : 0) + (M[3] ? (C<<3) : 0) + \dots$
 - Arrange like a tree to reduce gate delay critical path
- Delay? N^2 vs $N \cdot \log N$? Not that simple, depends on adder
 - Approx " $2N$ " versus " $N + \log N$ ", with optimization: $O(\log N)$

Consecutive Addition: Carry Save Adder

 

 - 2 N-bit RC adders
+ 2 + d(add) gate delays
- M N-bit RC adders delay
 - Naïve: $O(M*N)$
 - Actual: $O(M+N)$



- M N-bit Carry Select?
 - Delay calculation tricky
- Carry Save Adder (CSA)
 - 3-to-2 CSA tree + adder
 - Delay: $O(\log M + \log N)$

Hardware != Software: Part Deux

- Recall: hardware is parallel, software is sequential
- Exploit: evaluate independent sub-expressions in parallel
- Example I: $S = A + B + C + D$
 - Software? 3 steps: (1) $S1 = A+B$, (2) $S2 = S1+C$, (3) $S = S2+D$
 - + Hardware? 2 steps: (1) $S1 = A+B$, $S2=C+D$, (2) $S = S1+S2$
- Example II: $S = A + B + C$
 - Software? 2 steps: (1) $S1 = A+B$, (2) $S = S1+C$
 - Hardware? 2 steps: (1) $S1 = A+B$ (2) $S = S1+C$
 - + Actually hardware can do this in 1.2 steps! (CSA adder)

Division

4th Grade: Decimal Division

$$\begin{array}{r}
 \underline{9} \\
 3 \overline{) 29} \\
 \underline{-27} \\
 2
 \end{array}$$

// quotient
// divisor | dividend
// remainder

- Shift divisor left (multiply by 10) until MSB lines up with dividend's
- Repeat until remaining dividend (remainder) < divisor
 - Find largest single digit q such that $(q*\text{divisor}) < \text{dividend}$
 - Set LSB of quotient to q
 - Subtract $(q*\text{divisor})$ from dividend
 - Shift quotient left by one digit (multiply by 10)
 - Shift divisor right by one digit (divide by 10)

Binary Division

$$\begin{array}{r}
 \underline{} \\
 3 \overline{)29} = 0011 \overline{)011101} = 9 \\
 \underline{-24} = - 011000 \\
 5 = 000101 \\
 \underline{-3} = - 000011 \\
 2 = 000010
 \end{array}$$

Binary Division Hardware

- Same as decimal division, except (again)
 - More individual steps (base is smaller)
 - + Each step is simpler
- Find largest bit q such that $(q * \text{divisor}) < \text{dividend}$
 - $q = 0$ or 1
- Subtract $(q * \text{divisor})$ from dividend
 - $q = 0$ or $1 \rightarrow$ no actual multiplication, subtract divisor or not
- Complication: **largest** q such that $(q * \text{divisor}) < \text{dividend}$
 - How do you know if $(1 * \text{divisor}) < \text{dividend}$?
 - Human can “eyeball” this
 - Computer does not have eyeballs
 - Subtract and see if result is negative

Software Divide Algorithm

- Can implement this algorithm in software
- Inputs: dividend and divisor

```

for (int i = 0; i < 32; i++) {
    remainder = (remainder << 1) | (dividend >> 31);
    if (remainder >= divisor) {
        quotient = (quotient << 1) | 1;
        remainder = remainder - divisor;
    } else {
        quotient = (quotient << 1) | 0;
    }
    dividend = dividend << 1;
}

```


Divide Example

- Input: Divisor = 00011 , Dividend = 11101

Step	Remainder	Quotient	Remainder	Dividend
0	00000	00000	00000	11101
1	00001	00000	00001	11010
2	00011	00001	00000	10100
3	00001	00010	00001	01000
4	00010	00100	00001	10000
5	00101	01001	00010	00000

- Result: Quotient: 1001, Remainder: 10

Divider Circuit

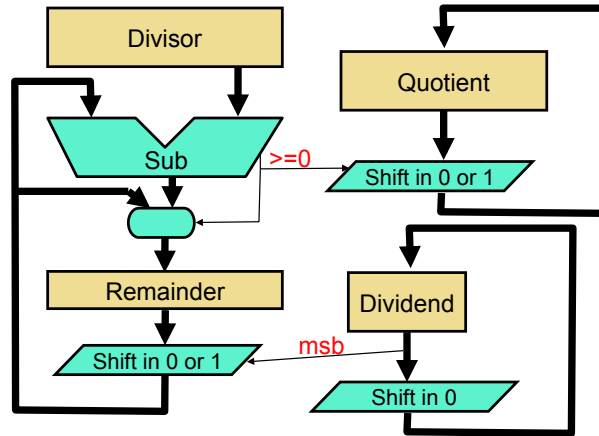

- N cycles for n-bit divide

Floating Point

Floating Point (FP) Numbers

- **Floating point numbers:** numbers in scientific notation
 - Two uses
- Use I: real numbers (numbers with non-zero fractions)
 - 3.1415926...
 - 2.1878...
 - $6.62 * 10^{-34}$
- Use II: really big numbers
 - $3.0 * 10^8$
 - $6.02 * 10^{23}$
- Aside: best not used for currency values

Scientific Notation

- **Scientific notation:**
 - Number $[S,F,E] = S * F * 2^E$
 - S: **sign**
 - F: **significand** (fraction)
 - E: **exponent**
 - **"Floating point"**: binary (decimal) point has different magnitude
- + "Sliding window" of precision using notion of **significant digits**
 - Small numbers very precise, many places after decimal point
 - Big numbers are much less so, not all integers representable
 - But for those instances you don't really care anyway
- Caveat: all representations are just approximations
 - Sometimes wierdos like 0.9999999 or 1.0000001 come up
 - + But good enough for most purposes

IEEE 754 Standard Precision/Range

- **Single precision:** `float` in C
 - 32-bit: 1-bit sign + 8-bit exponent + 23-bit significand
 - Range: $2.0 * 10^{-38} < N < 2.0 * 10^{38}$
 - Precision: ~7 significant (decimal) digits
 - Used when exact precision is less important (e.g., 3D games)
- **Double precision:** `double` in C
 - 64-bit: 1-bit sign + 11-bit exponent + 52-bit significand
 - Range: $2.0 * 10^{-308} < N < 2.0 * 10^{308}$
 - Precision: ~15 significant (decimal) digits
 - Used for scientific computations
- Numbers $> 10^{308}$ don't come up in many calculations
 - 10^{80} ~ number of atoms in universe

Floating Point is Inexact

- Accuracy problems sometimes get bad
 - FP arithmetic not associative: $(A+B)+C$ not same as $A+(B+C)$
 - Addition of big and small numbers (summing many small numbers)
 - Subtraction of two big numbers
- Example, what's $(1*10^{30} + 1*10^0) - 1*10^{30}$?
 - Intuitively: $1*10^0 = 1$
 - But: $(1*10^{30} + 1*10^0) - 1*10^{30} = (1*10^{30} - 1*10^{30}) = 0$
- Reciprocal math: "x/y" versus "x*(1/y)"
 - Reciprocal & multiply is faster than divide, but less precise
- Compilers are generally conservative by default
 - GCC flag: `-ffast-math` (allows assoc. opts, reciprocal math)
- **Numerical analysis:** field formed around this problem
 - Re-formulating algorithms in a way that bounds numerical error
- In your code: never test for equality between FP numbers
 - Use something like: `if (abs(a-b) < 0.00001) then ...`

Pentium FDIV Bug

- Pentium shipped in August 1994
- Intel actually knew about the bug in July
 - But calculated that delaying the project a month would cost ~\$1M
 - And that in reality only a dozen or so people would encounter it
 - They were right... but one of them took the story to EE times
- By November 1994, firestorm was full on
 - IBM said that typical Excel user would encounter bug every month
 - Assumed 5K divisions per second around the clock
 - People believed the story
 - IBM stopped shipping Pentium PCs
- By December 1994, Intel promises full recall
 - Total cost: ~\$550M
- Recent example: Intel's chipset (January 2011)


Arithmetic Latencies

- Latency in cycles of common arithmetic operations
- Source: *Software Optimization Guide for AMD Family 10h Processors, Dec 2007*
 - Intel "Core 2" chips similar

	Int 32	Int 64	Fp 32	Fp 64
Add/Subtract	1	1	4	4
Multiply	3	5	4	4
Divide	14 to 40	23 to 87	16	20

- Divide is **variable latency** based on the size of the dividend
 - Detect number of leading zeros, then divide
- Floating point divide faster than integer divide? Why?

Summary

 

- Integer addition
 - Most timing-critical operation in datapath
 - Hardware != software
 - Exploit sub-addition parallelism
- Fast addition
 - Carry-select: parallelism in sum
- Multiplication
 - Chains and trees of additions
- Division
- Floating point

- Next: single-cycle datapath