

Chapter 3

Digital Logic Structures

Based on slides © McGraw-Hill
Additional material © 2004/2005/2006 Lewis/Martin

Transistor: Building Block of Computers

Microprocessors contain millions of transistors

- Intel Pentium 4 (2000): 48 million
- IBM PowerPC 750FX (2002): 38 million
- IBM PowerPC G5 (2003): 58 million
- Intel Core Duo 2 (2006): 291 million (192+ million in cache alone)

Logically, each transistor acts as a switch

Combined to implement logic functions

- AND, OR, NOT

Combined to build higher-level structures


- Adder, multiplexer, decoder, register, ...

Combined to build processor

- LC-3

CSE 240

3-2

 


How do we represent data in a computer?

At the lowest level, a computer has electronic “plumbing”

- Operates by controlling the flow of electrons

Easy to recognize two conditions:

 1. Presence of a voltage – we’ll call this state “1”
2. Absence of a voltage – we’ll call this state “0”



Computer use transistors as switches to manipulate bits

- Before transistors: tubes, electro-mechanical relays (pre 1950s)
- Mechanical adders (punch cards, gears) as far back as mid-1600s

Before describing transistors, we present an analogy...

CSE 240

3-4


A Transistor Analogy: Computing with Air

Use air pressure to encode values

- High pressure represents a "1" (blow)
- Low pressure represents a "0" (suck)

Valve can allow or disallow the flow of air


- Two types of valves

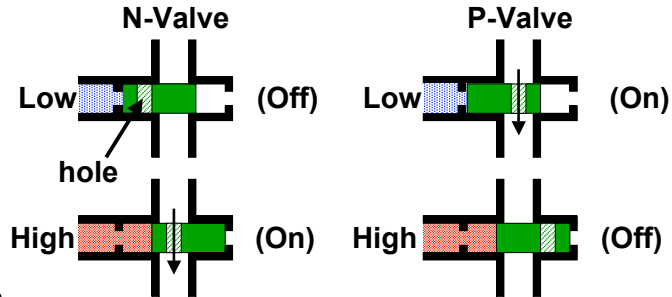

CSE 240

3-5


Pressure Inverter

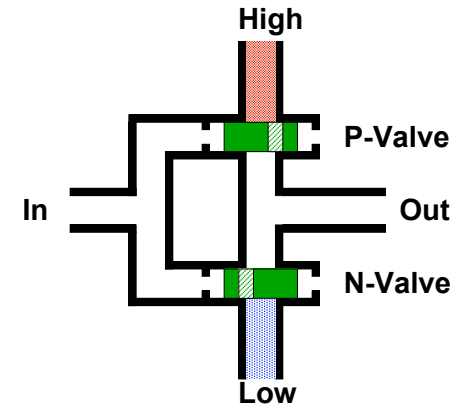

CSE 240

3-6


Pressure Inverter (Low to High)

 

CSE 240

3-7


Pressure Inverter

 

CSE 240

3-8

Pressure Inverter (High to Low)

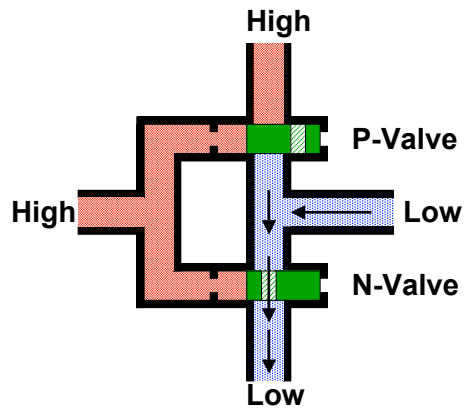

CSE 240

3-9

Analogy Explained

Pressure differential → electrical potential (voltage)

- Air molecules → electrons
- High pressure → high voltage
- Low pressure → low voltage

Air flow → electrical current

- Pipes → wires
- Air only flows from high to low pressure
- Electrons only flow from high to low voltage
- Flow only occurs when changing from 1 to 0 or 0 to 1

Valve → transistor

- The transistor: one of the century's most important inventions

CSE 240

3-10


Transistors as Switches

Two types

- N-type
- P-type

Properties


- Solid state (no moving parts)
- Reliable (low failure rate)
- Small (90nm channel length)
- Fast (<0.1ns switch latency)

 

CSE 240

3-11

MOS + FET

 

MOS: three materials needed to make a transistor

- **Metal** (Al, W, Cu): conductor
- **Oxide** (SiO₂): insulator
- **Semiconductor** (doped Si): conducts under certain conditions

FET: field effect (the mechanism) transistor

- Voltage on gate: current flows source to drain (transistor on)
- No voltage on gate: no current (transistor off)


Recall, two types of MOSFET: n and p

CSE 240

3-12

N-type MOS Transistor

- When Gate has **positive** voltage, short circuit between #1 and #2 (switch **closed**)
- When Gate has **zero** voltage, open circuit between #1 and #2 (switch **open**)

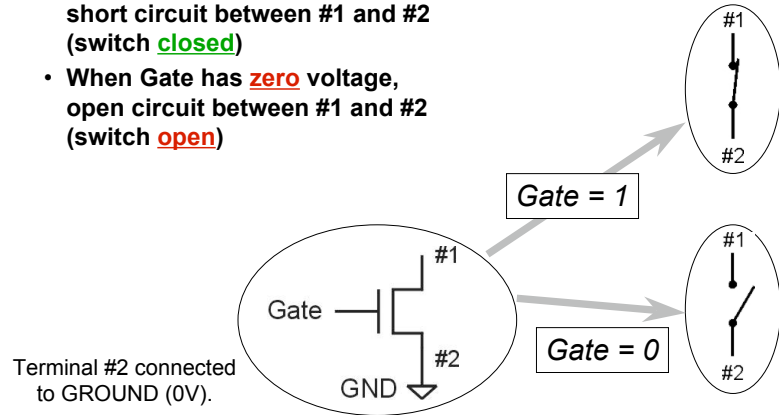


CSE 240

3-13

P-type MOS Transistor

P-type is complementary to n-type


- When Gate has **positive** voltage, open circuit between #1 and #2 (switch **open**)
- When Gate has **zero** voltage, short circuit between #1 and #2 (switch **closed**)

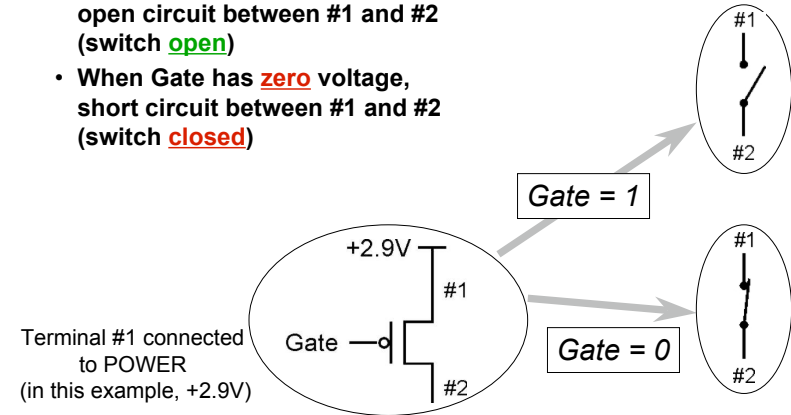

CSE 240

3-14

Inverter (NOT Gate)

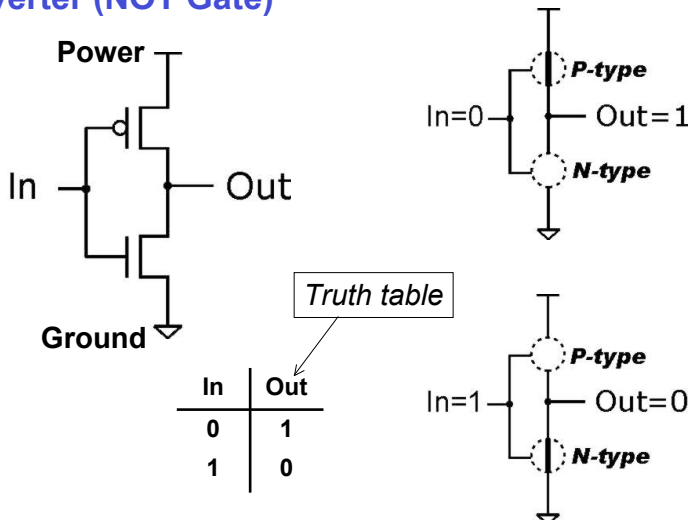

CSE 240

3-15

CMOS Circuit

Inverter is an example of **Complementary MOS (CMOS)**

Uses both **n-type** and **p-type** MOS transistors



- p-type
 - Attached to **POWER** (high voltage)
 - Pulls output voltage **UP** when input is zero
- n-type
 - Attached to **GROUND** (low voltage)
 - Pulls output voltage **DOWN** when input is one

For all inputs, make sure that output is either connected to **GROUND** or to **POWER**, but not both! (why?)

CSE 240

3-16

NAND Gate (NOT-AND)

  


A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

CSE 240 Note: Parallel structure on top, serial on bottom.

3-17

AND Gate


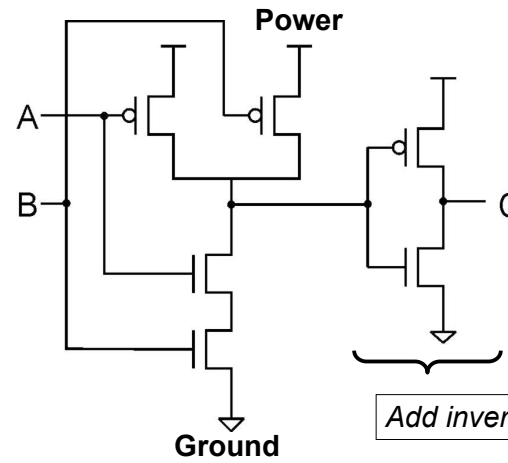


A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

CSE 240

3-18

NOR Gate (NOT-OR)

  


A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

CSE 240 Note: Serial structure on top, parallel on bottom.

3-19

OR Gate

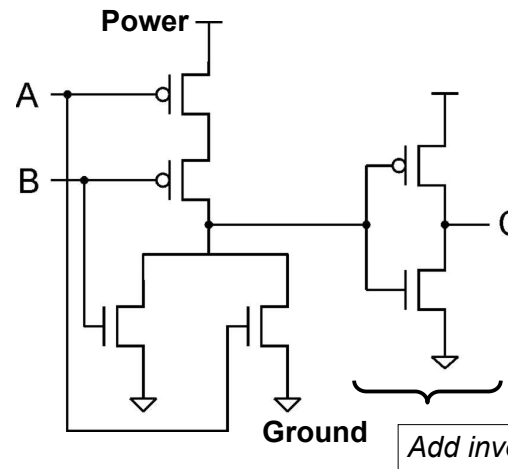

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

CSE 240

3-20


Basic Gates

From Now On... Gates

- Covered transistors mostly so that you know they exist
- Note: "Logic Gate" not related to "Gate" of transistors

Will study implementation in terms of gates

 - Circuits that implement Boolean functions



More complicated gates from transistors possible

- XOR, Multiple-input AND-OR-Invert (AOI) gates

CSE 240

3-21


More than 2 Inputs?

AND/OR can take any number of inputs

- AND = 1 if all inputs are 1
- OR = 1 if any input is 1
- Similar for NAND/NOR

Implementation

- Multiple two-input gates or single CMOS circuit

 


CSE 240

3-22

Visual Shorthand for Multi-bit Gates

Use a cross-hatch mark to group wires

- Example: calculate the AND of a pair of 4-bit numbers
- A_3 is "high-order" or "most-significant" bit
- If "A" is 1000, then $A_3 = 1, A_2 = 0, A_1 = 0, A_0 = 0$

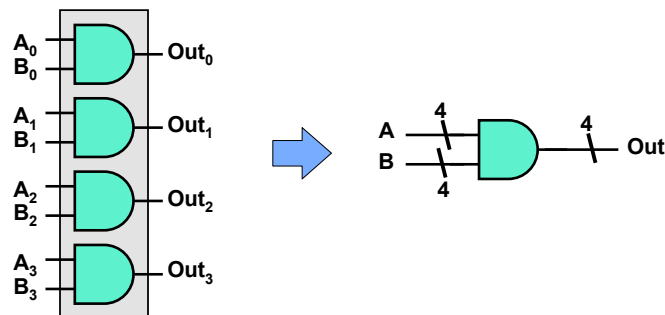


CSE 240

3-23

Shorthand for Inverting Signals

Invert a signal by adding either

- A \circ before/after a gate
- A "bar" over letter

 


CSE 240

3-24

Logical Completeness

AND, OR, NOT can implement ANY truth table

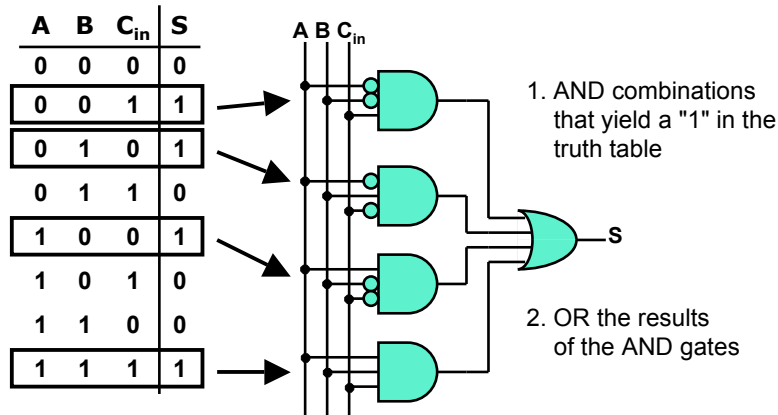

CSE 240

3-25

Logical Completeness via PLAs

Any truth table as a Programmable Logic Array (PLA)

- Traditionally a grid of AND and OR gates
- Configurable by removing wires

Single-output custom PLA (as on previous slide):

- One AND gate per row with "1" in output in truth table
- Maximum number of AND gates: 2^n for n inputs
- One OR gate

Multiple-output custom PLA:

- Build multiple single-output PLAs
- Share AND gates "in common"
- One OR gate per output column in truth table

CSE 240

3-26

DeMorgan's Law

Converting AND to OR (with some help from NOT)



Consider the following gate:

To convert AND to OR
(or vice versa),
invert inputs and output.

$$\overline{\overline{A} \text{ AND } \overline{B}} = A \text{ OR } B$$



A	B	\overline{A}	\overline{B}	A AND B	$\overline{\overline{A} \text{ AND } \overline{B}}$
0	0	1	1	0	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	1	1

  

Why might this be useful?

CSE 240

3-27

Summary

MOS transistors: switches to implement logic functions

- n-type: connect to GROUND, turn on (with 1) to pull down to 0
- p-type: connect to POWER, turn on (with 0) to pull up to 1

Basic gates: NOT, NOR, NAND

- Logic functions are usually expressed with AND, OR, and NOT
- Universal: any truth table to simple gates (via a PLA)

DeMorgan's Law

- Convert AND to OR (and vice versa) by inverting inputs/output

Ok, we now have simple logic gates

- Next up: how do we combine them into something useful?

CSE 240

3-28

Chapter 3


Digital Logic Structures

Based on slides © McGraw-Hill
Additional material © 2004/2005/2006 Lewis/Martin

Incrementer

Let's create an incrementer

 - Input: **A** (as a 16-bit 2's complement integer)
- Output: **A+1** (also as a 16-bit 2's complement integer)



Approach #1 (impractical):

- Use PLA-like techniques to implement circuit
- Problem: 2^{16} or 65536 rows, 16 output columns
- In theory, possible; in practice, intractable

Approach #2 (pragmatic):

- Create a 1-bit incrementer circuit
- Replicate it 16 times

AND, OR, NOT Gates: What Good Are They?

Last time:

- Transistors and gates
- Can implement any logical function using gates (using PLAs)

Today:




- We'll use gates to create some building blocks of a processor
- One goal: automate binary arithmetic from Chapter 2
- Continuing on our bottom-up journey

Next time:

- Storing bits (memory)
- Circuits with "state"




One-bit Incrementer

   Implement a single-column of an incrementer



Aside: XOR

A_n	C_{in}	S_n	C_{out}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

   


CSE 240

3-33

N-bit Incrementer

Chain N 1-bit incrementers together


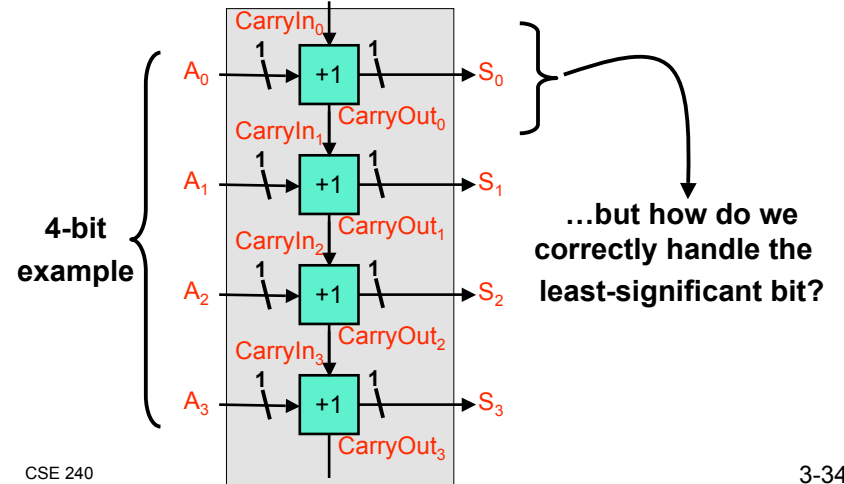


CSE 240

3-34

N-bit Incrementer, continued

How do we handle the least-significant bit?

  



CSE 240

3-35

Adder

Conceptually similar to an incrementer

- Build a one-bit slice, replicate n times

  


CSE 240

3-36

One-bit Adder

Add two bits and carry-in
produce one-bit sum and carry-out


A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

CSE 240


3-37

N-bit Adder

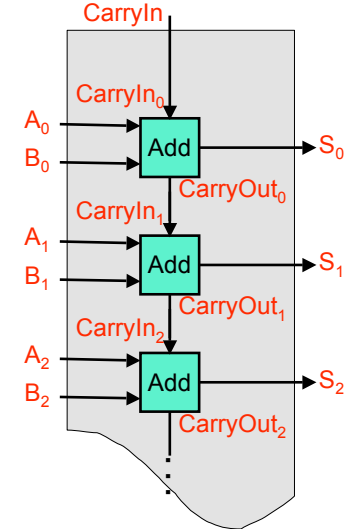

CSE 240

3-38

 

CarryOut: useful for detecting overflow

CarryIn: assumed to be zero if not present

Aside: Efficient Adders

Full disclosure:

- Our adder: Ripple-carry adder
- **No one (sane) actually uses ripple-carry adders**
- Why? way too slow
- Latency proportional to n

We can do better

- Many ways to create adders with latency proportional to $\log_2(n)$
- In theory: constant latency (build a big PLA)
- In practice: too much hardware, too many high-degree gates
- “Constant factor” matters, too
- More on this topic in CSE371


CSE 240

3-39

Subtractor

Build a subtractor from an adder

 - Calculate $A - B = A + -B$
- Negate B
- Recall $-B = \text{NOT}(B) + 1$



Now, let's create an adder/subtractor


CSE 240

3-40

...But First, The Multiplexer (MUX)

Selector/Chooser of signals

- Multi-way switch

 

CSE 240

3-41


The Multiplexer (MUX)

In general

- N select bits chooses from 2^N inputs
- An incredibly useful building block

Multi-bit muxes


- Can switch an entire "bus" or group of signals
- Switch n-bits with n muxes with the same select bits

 

CSE 240

3-42


Adder/Subtractor - Approach #1

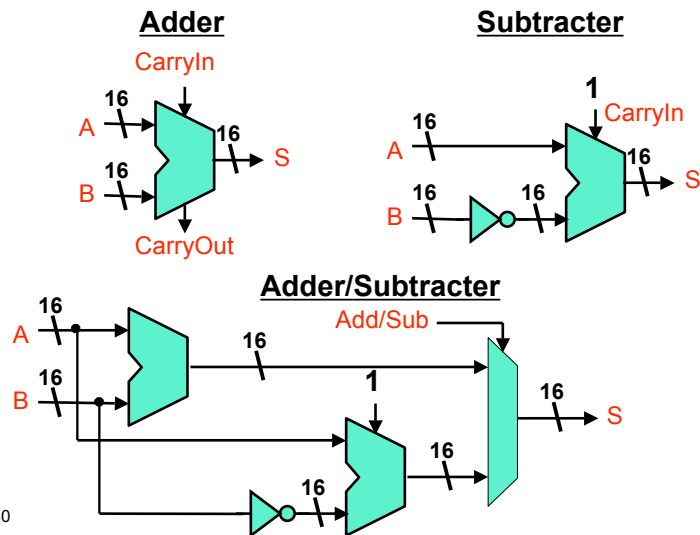

CSE 240

3-43

Adder/Subtractor - Approach #2

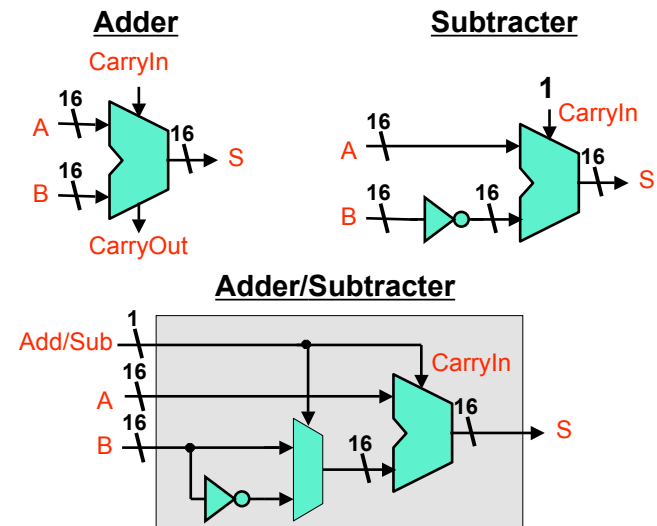

CSE 240

3-44

Ok, So We Can Add and Subtract

Other arithmetic operations similar

- Even floating point operations

We can calculate; but we can't remember

- Next time: **storage and memory**
- After that: simple “state machines”
- After that: a simple processor

Remember: readings, quizzes, and homework

- Homework 2 due Friday

Chapter 3 Digital Logic Structures

Based on slides © McGraw-Hill
Additional material © 2004/2005/2006 Lewis/Martin

CSE 240

3-45

Combinational vs. Sequential Logic

Combinational Circuit

- Always gives the same output for a given set of inputs
 - For example, adder always generates sum and carry, regardless of previous inputs

Sequential Circuit

- Stores information
- Output depends on stored information (state) plus input
 - Given input might produce different outputs, depending on stored information
- *Example:* ticket counter
 - Advances when you push the button
 - Output depends on previous state
- Useful for building “memory” elements and “state machines”

CSE 240

3-47

Storage - Cross-Coupled Inverters

Cross-coupled inverters (INV) gates

- Holds value Q and Q' (Q' is the same as \bar{Q})



- **Read:** get value from either Q or Q'

Maintains its “state”, but how do we change the state?

- **Write:** Option #1: put opposite values on Q and Q' simultaneously
 - Requires “analog” overdriving of Q and Q'


CSE 240

3-48


Storage - NANDs

Option #2: "Digital" alternative for changing state

Write: change Q to one

 

Write: change Q to zero

 

CSE 240

3-49

Storage - Cross-Coupled NANDs (R-S Latch)

Write either a zero or one

- When $S=1$ and $R=1$, "quiescent" state; maintains value



- When $S=0$ and $R=1$, state changes to one ("set")
- When $S=1$ and $R=0$, state changes to zero ("reset" or "clear")




CSE 240

3-50

Storage - Cross-Coupled NANDs (R-S Latch)

What happens with $S=0$ and $R=0$?

 - Short answer: bad things
- Long answer: value stored will depend on timing on circuit



- Does S or R go to one first?
 - If they change at the same time?
 - Oscillation or meta-stability can result
- Let's make sure this can never happen...

CSE 240

3-51


Gated D-Latch

Add logic to an R-S latch

- Create a better interface

Two inputs: D (data) and WE (write enable)

- When $WE = 1$, latch is set to **value of D**
 - $S = \text{NOT}(D)$, $R = D$
- When $WE = 0$, latch continues to hold **previous value**
 - $S = R = 1$
- Does not allow $S=0$, $R=0$ case to occur

 


CSE 240

3-52

Register

A register stores a multi-bit value

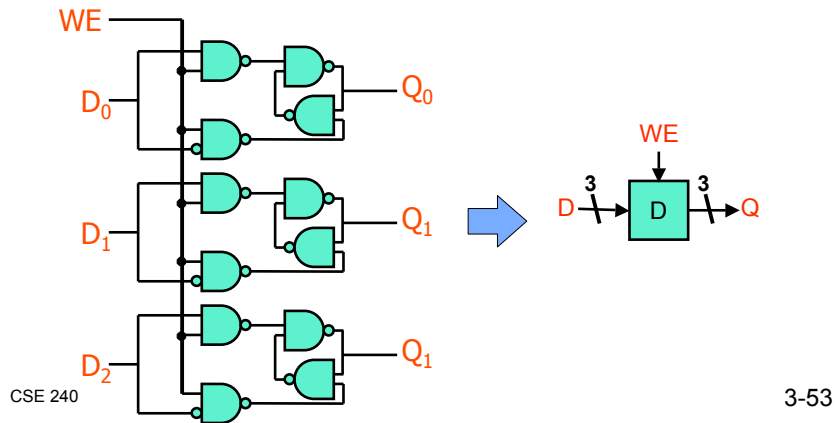- A collection of D-latches, controlled by a common WE
- When WE=1, n-bit value D is written to register




Aside: More on Representing Multi-bit Values

Number bits from right (0) to left (n-1)

- Just a convention -- could be left to right, but must be *consistent*

Use brackets to denote range:

 
D[l:r] denotes bit l to bit r, from *left to right*




May also see A<14:9>

- Especially in hardware block diagrams.

CSE 240

 

Let's Try to Build a Counter

 

How quickly will this count?

- Timing dependent

Will it even work?

- Probably not
- D-latches are "transparent"
 - Allows next input to immediately flow to output
 - Outputs will never be "stable"


CSE 240

3-55

What's Missing? The Clock

A **clock** controls when registers are "updated"

 - Oscillating global signal with fixed period
- Typical clock frequencies today: a couple of gigahertz




- Corresponds to <1 nanosecond between one rise and the next
- Generated on-chip by special circuitry (for example, oscillating ring of inverters)

CSE 240

3-56

Let's Try Again: a Counter

 

Solves half the problem

- Controls the rate of updates

Remaining problem

- When clock=1, same problem
- D-latches are still transparent


CSE 240

3-57



Example of Incorrect Operation

Initial state: 010_2

 


CSE 240

3-58



Example of Incorrect Operation

Set WE (Write Enable) to 1

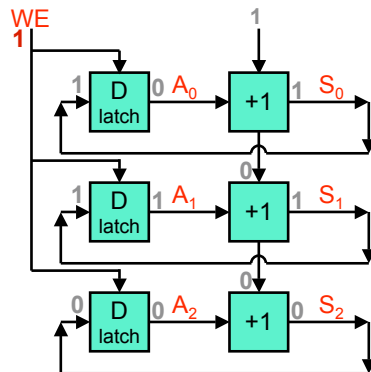

CSE 240


3-59



Example of Incorrect Operation

D latches write new value: 011_2

Goal: 100_2

 


CSE 240

3-60




Example of Incorrect Operation

Incrementer calculates 1st bit

 

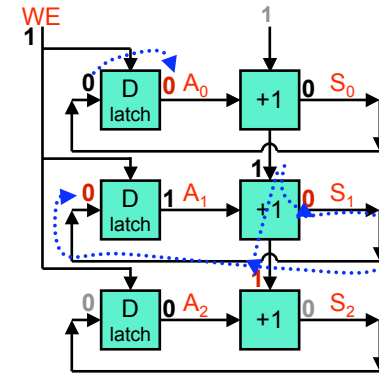
Example of Incorrect Operation

Incrementer calculates 2nd bit, 1st bit latched



 
Example of Incorrect Operation

Incrementer calculates 3rd bit, 2nd bit latched,
1st bit re-calculated



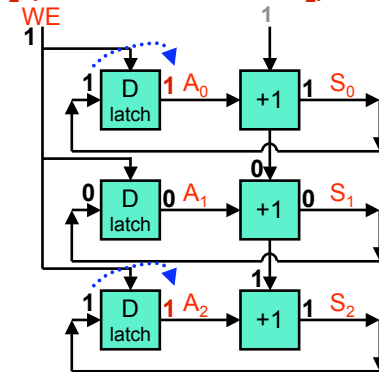
Example of Incorrect Operation

1st and 3rd bits latched
value is: 101_2 (not the desired 100_2)



Correct Operation

Additional D-latches, WE is NOT(Clock) and Clock
Initial state: 010_2

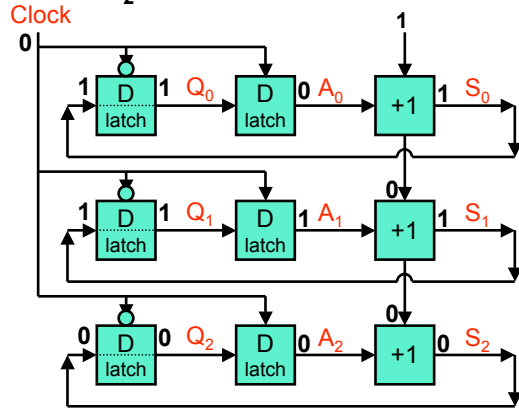


CSE 240

3-65

Correct Operation

Clock switches to 1, 2nd latch WE = 1

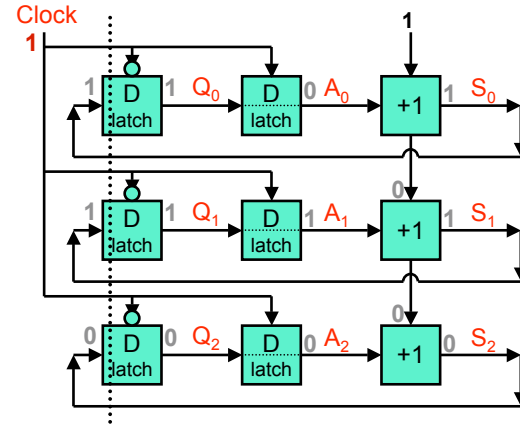


CSE 240

3-66

Correct Operation

D latches write new value: 011_2
Goal: 100_2

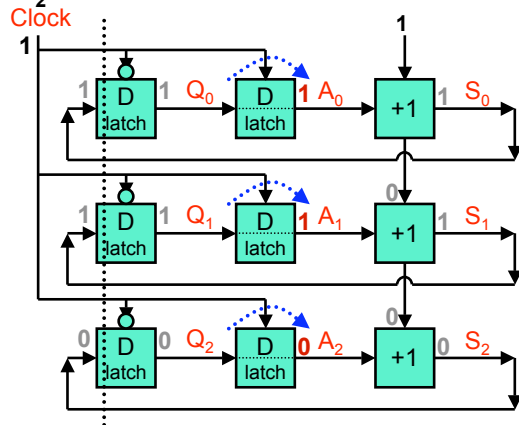


CSE 240

3-67

Correct Operation

Incrementer begins calculation

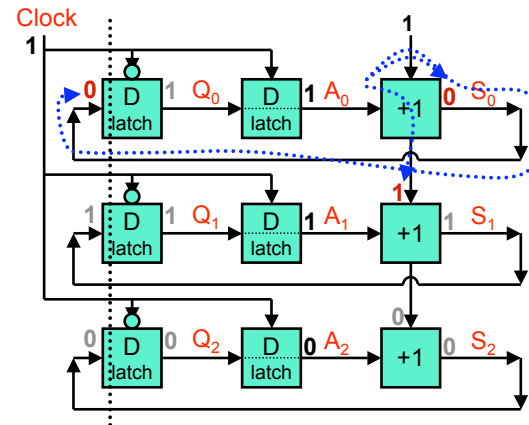


CSE 240

3-68




Correct Operation

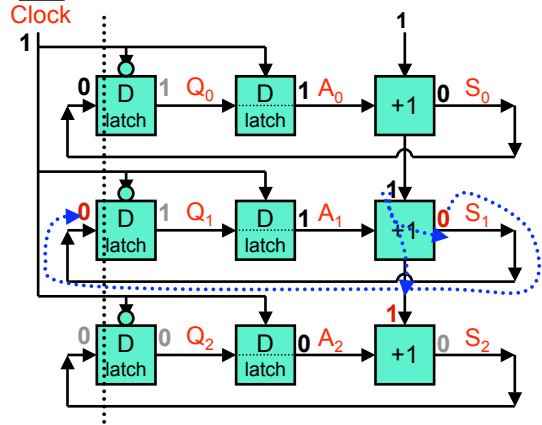Incrementer calculates 2nd bit,
First bit not written to latch




Correct Operation

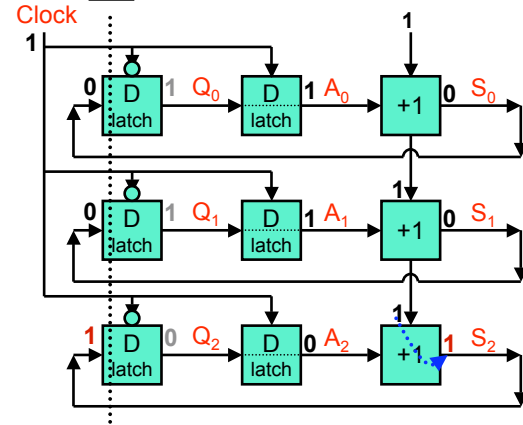Incrementer calculates 3rd bit,
1st, 2nd bits not written to latch




Correct Operation

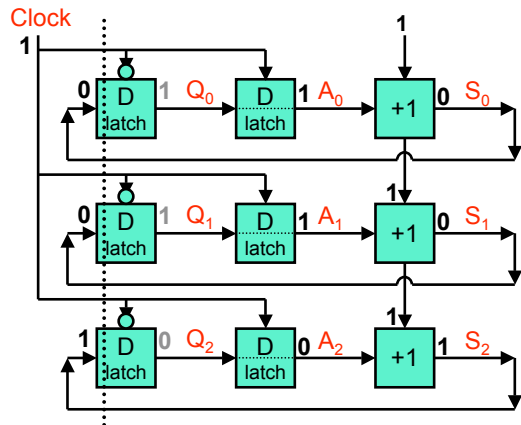
Correct value ready to latch (100_2), circuit **quiescent**





Correct Operation

Clock changes to 0

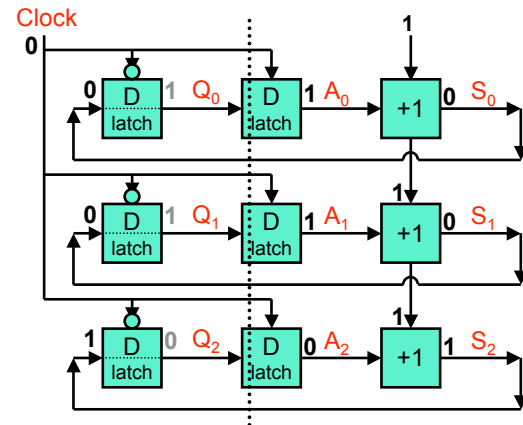


 

 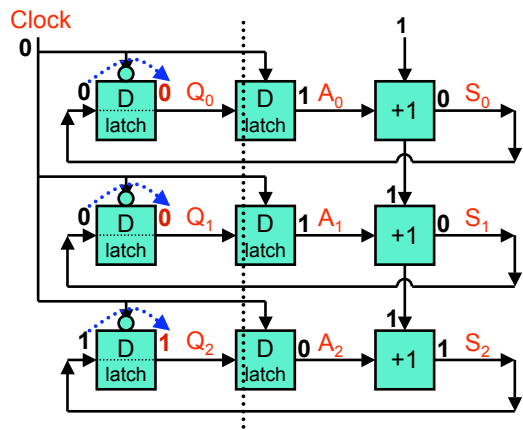2nd set of latches write correct value, circuit **quiescent**



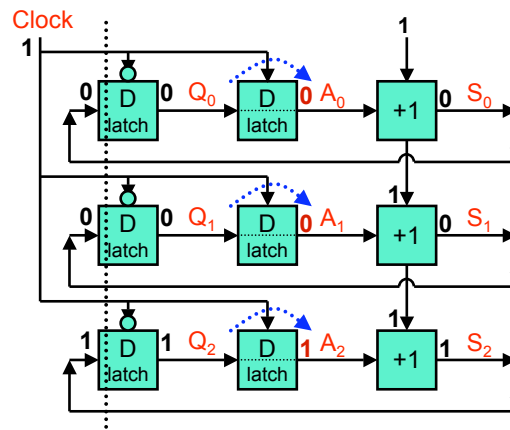
Clock changes back to 1, next increment begins



D Flip-Flop (or master-slave flip-flop)


D Flip-Flop is a pair of D latches

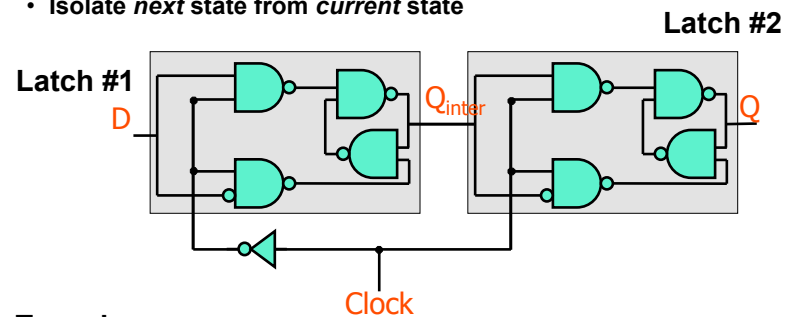- Stupid name, but it stuck
- Isolate *next* state from *current* state




Two phases:

- Clock = 1, Clock = 0

 

Phase 1

- Clock = 1
- Latch 1: writing disabled (output is stable Q_{inter})
- Latch 2: writing enabled ($Q = Q_{inter}$)

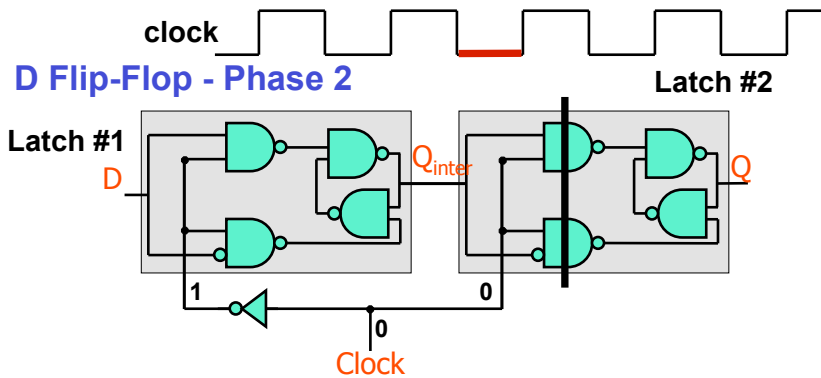

Phase 2

- Clock = 0
- Latch 1: writing enabled ($Q_{inter} = D$)
- Latch 2: writing disabled (output is stable Q)

Back to Phase 1

- Q becomes Q_{inter}

Latches & Flip-Flops

Latches

- “level triggered” (high or low)
- “transparent”

Flip-Flops


- “edge triggered” (rising/positive edge or falling/negative edge)
- “non-transparent” or “opaque” or just “latch” (!!!)

Flip-Flops have WE (write enable) signals, too

- Uses a gate to suppress the rising (or falling) edge of clock
- Once internalized in FF, no need to manipulate clock with logic
- Otherwise manipulating clock with logic usually a bad idea™


Working Counter

 Use a clocked register (made of D flip-flops)



More simply

- If WE = 1 assumed if WE is not present

 


Use WE input for conditional counter (stop watch)

Memory

Now that we know how to store bits, we can build a memory – a logical k by m array of stored bits

Address Space:
number of locations
(usually a power of 2)


$k = 2^n$
locations

 

Addressability:
number of bits per location
(e.g., byte-addressable)

m bits

Memory Interface

 


CSE 240

3-81

2² by 3-bit memory

Read operation

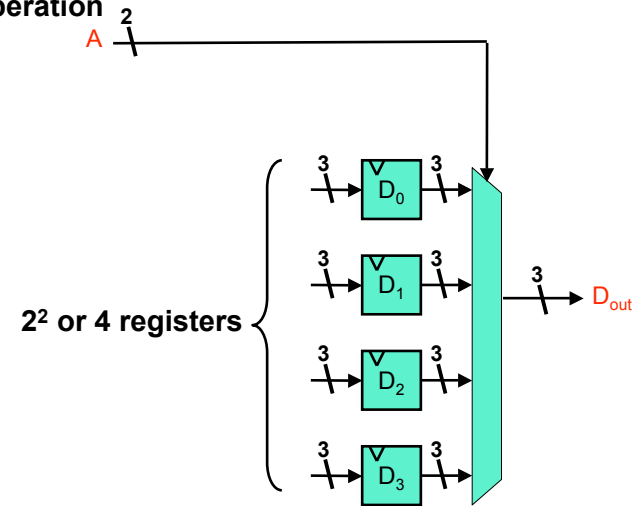


CSE 240

3-82

The Decoder

n inputs, 2^n outputs

- Exactly one output is 1 for each possible input pattern

 


CSE 240

3-83

2² by 3-bit memory

Write operation

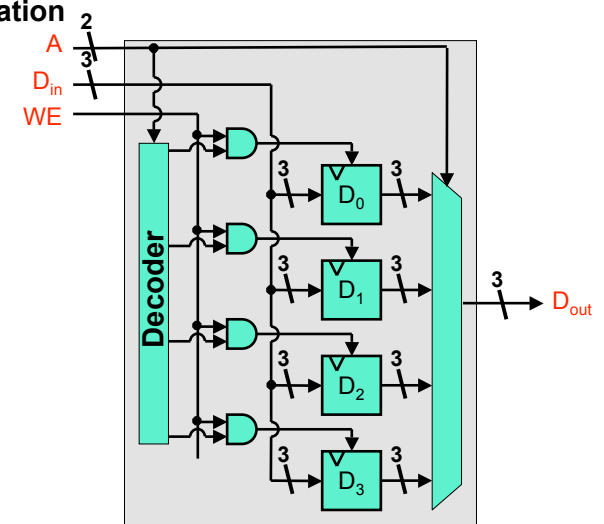


CSE 240

3-84

2² by 3-bit memory - Multiple "Ports"


Independent Read/Write

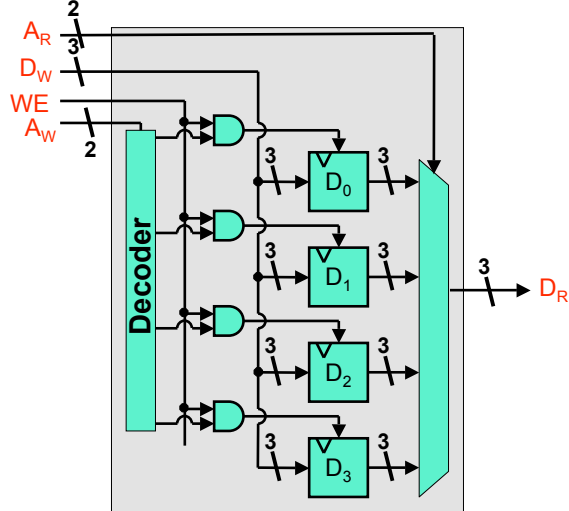

CSE 240

3-85


2² by 3-bit memory - Multiple Read Ports

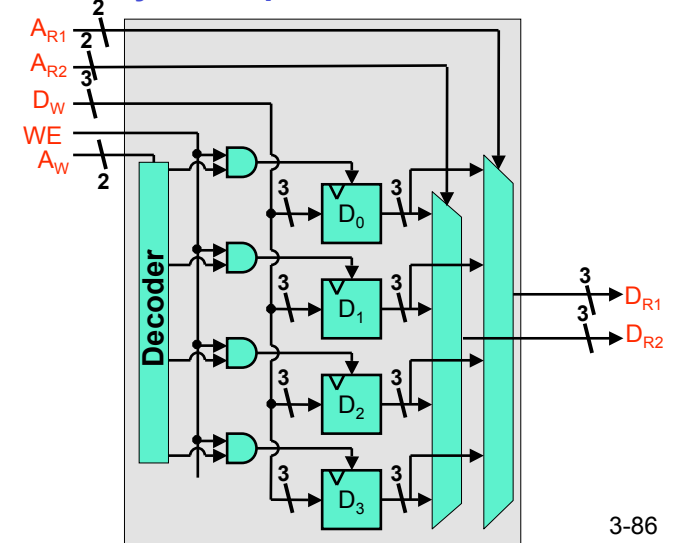

CSE 240

3-86

An Efficient 2² by 3-bit Memory - Single Port

 

CSE 240

3-87

More Memory Details

This is still not the way actual memory is implemented

- Real memory: fewer transistors, denser, relies on analog properties

But the logical structure is similar

- Address decoder
- Word select line, word write enable
- Bit line

Two basic kinds of RAM (Random Access Memory)

Static RAM (SRAM) - 6 transistors per bit

- Fast, maintains data as long as power applied

Dynamic RAM (DRAM) - 1 transistor per bit

- Denser but slower, destructive read, bit storage decays – must be periodically refreshed (like a leaky balloon)

CSE 240


Also, non-volatile memories: ROM, PROM, flash, ...

3-88

State Machine

Another type of sequential circuit

- Combines combinational logic with storage
- “Remembers” state, and changes output (and state) based on **inputs** and **current state**

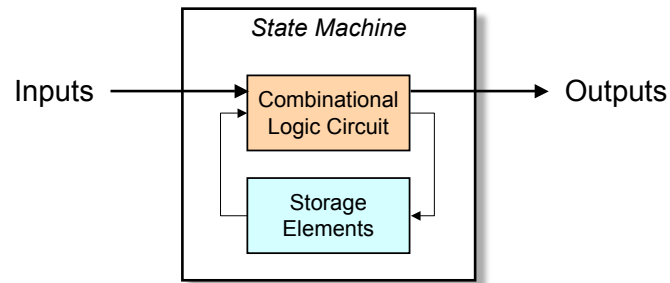


CSE 240

3-89


Combinational vs. Sequential

Two types of “combination” locks

 

Combinational

 Success depends only on the **values**, not the order in which they are set.



Sequential

Success depends on the **sequence** of values (e.g, R-13, L-22, R-3).

CSE 240

3-90

State

The **state** of system is **snapshot** of **all relevant elements** of system at moment snapshot is taken

Examples

- The state of a basketball game can be represented by the scoreboard
 - Number of points, time remaining, possession, etc.
- The state of a tic-tac-toe game can be represented by the placement of X's and O's on the board (and turn)

CSE 240

3-91

State of Sequential Lock

Our lock example has four different states, labeled A-D:


- A:** The lock is **not open**, and no relevant operations have been performed
- B:** The lock is **not open**, and the user has completed the **R-13** operation
- C:** The lock is **not open**, and the user has completed **R-13**, followed by **L-22**
- D:** The lock is **open**

CSE 240

3-92

Sequential Lock State Diagram

Shows **states** and **actions** that cause a **transition** between states

 

CSE 240

3-93

Finite State Machine

A description of a system with the following components:

1. A finite number of **states**
2. A finite number of external **inputs**
3. A finite number of external **outputs**
4. An explicit specification of all **state transitions**
5. An explicit specification of what determines each external **output value**

Often described by a state diagram

- Inputs trigger state transitions
- Outputs are associated with each state (or with each transition)

CSE 240

3-94


Implementing a Finite State Machine

Combinational logic

- Determine outputs and next state.

Storage elements

- Maintain state representation.

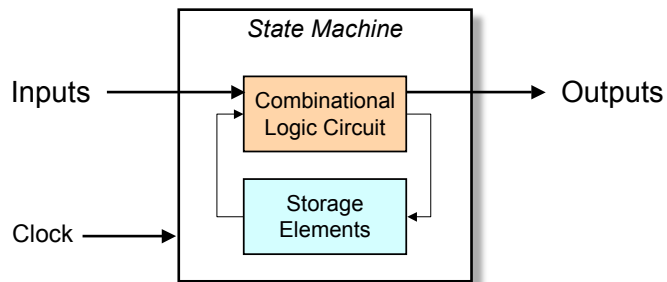

CSE 240

3-95

Storage

Master-slave flip-flop stores one state bit

Number of storage elements (flip-flops)

- Determined by number of states (and representation of states)

Examples

- Sequential lock
 - Four states – two bits
- Basketball scoreboard
 - 8 bits for each score, 5 bits for minutes, 6 bits for seconds, 1 bit for possession arrow, 1 bit for half, ...


CSE 240

3-96

Complete Example

A blinking traffic sign


- No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)

 

CSE 240

3-97

Traffic Sign State Diagram

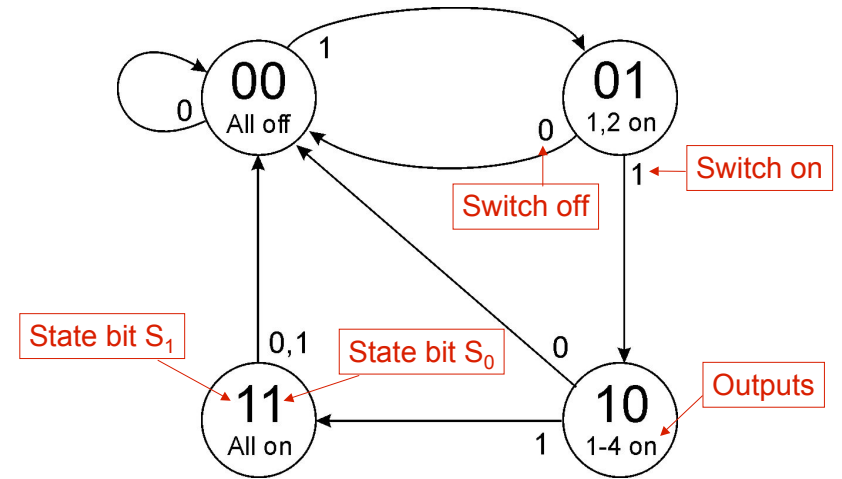


CSE 240

Transition on each clock cycle.

3-98

Traffic Sign State Diagram: State 00

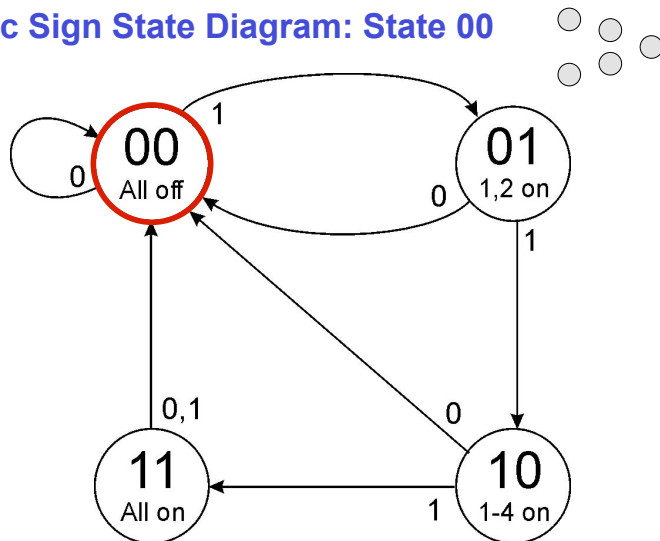


CSE 240

Transition on each clock cycle.

3-99

Traffic Sign State Diagram: State 01

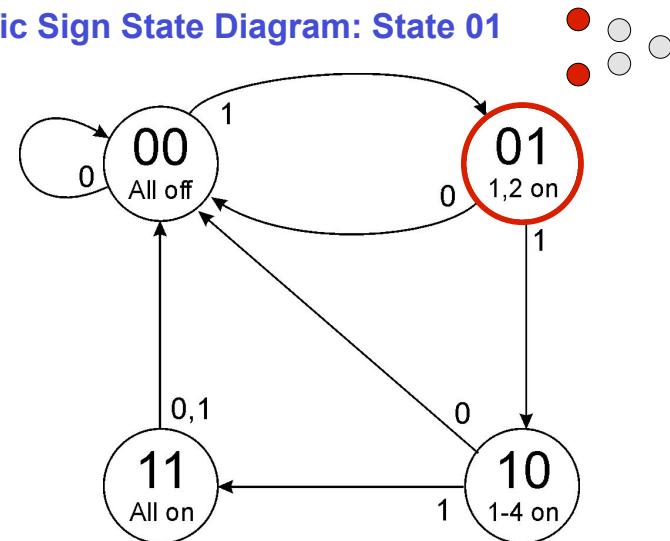


CSE 240

Transition on each clock cycle.

3-100


Traffic Sign State Diagram: State 10

 

CSE 240 Transition on each clock cycle.

3-101


Traffic Sign State Diagram: State 11

 

CSE 240 Transition on each clock cycle.

3-102

Traffic Sign State Diagram: State 00

 

CSE 240 Transition on each clock cycle.

3-103

Traffic Sign Truth Tables

Outputs
(depend only on state: S_1S_0)

S_1	S_0	Z	Y	X
0	0	0	0	0
0	1	1	0	0
1	0	1	1	0
1	1	1	1	1

Next State: $S_1'S_0'$
(depend on state and input)


In	S_1	S_0	S_1'	S_0'
0	X	X	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

Whenever In=0, next state is 00.

CSE 240

3-104

Traffic Sign Logic

 


CSE 240

3-105

Programmable State Machines

What if we want to change the pattern of the sign?

 - An alternative state machine implementation
- Use a memory indexed by state number



In/S ₁ /S ₀	S
000	00
001	00
010	00
011	00
100	01
101	10
110	11
111	00

S	X/Y/Z
00	000
01	100
10	110
11	111


CSE 240

3-106

Programmable State Machines

Change to a two-state pattern:

 - All off
 - All on
- State: 00 State: 10 State: 00



In/S ₁ /S ₀	S
000	00
001	--
010	00
011	--
100	10
101	--
110	00
111	--

S	Z/Y/Z
00	000
01	--
10	111
11	--

CSE 240

3-107

From Logic to Data Path

The data path of a computer is all the logic used to process information.

- See the data path of the LC-3 on next slide

Combinational Logic

- Decoders -- convert instructions into control signals
- Multiplexers -- select inputs and outputs
- ALU (Arithmetic and Logic Unit) -- operations on data

Sequential Logic

- State machine -- coordinate control signals and data movement
- Registers and latches -- storage elements

CSE 240


3-108

LC-3 Data Path

Combinational Logic

Storage

State Machine

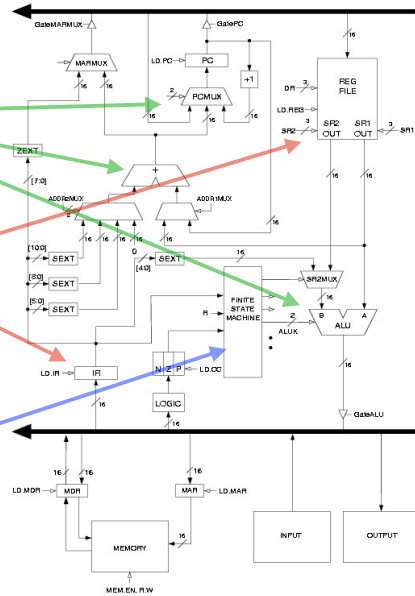

CSE 240

3-109

Looking Forward...

We've touched on basic digital logic

- Transistors
- Gates
- Storage (latches, flip-flops, memory)
- State machines

Built some simple circuits

- Incrementer, adder, subtracter, adder/subtracter
- Counter (consisting of register and incrementer)
- Hard-coded traffic sign state machine
- Programmable traffic sign state machine

Up next: a computer as a (simple?) state machine

CSE 240

3-110

Next Time

Topic

- The von Neumann Model

Readings

- Chapter 4.0 - 4.2

Online quiz

- You know the drill!

CSE 240

3-111