

CIS 371

Computer Organization and Design

Unit 2: Single-Cycle Datapath and Control

CIS371 (Roth/Martin): Datapath and Control

1


Readings

- Digital logic
 - P&H, Appendix C (on CD)
- Basic datapath
 - P&H, Chapter 4.1 – 4.4 (well-written, relates to lecture well)

CIS371 (Roth/Martin): Datapath and Control

3

This Unit: Single-Cycle Datapaths

 

- Digital logic basics
 - Focus on useful components
- Mapping an ISA to a datapath
 - MIPS example
- Single-cycle control

CIS371 (Roth/Martin): Datapath and Control

2


So You Have an ISA...

- ... not useful without a piece of hardware to execute it

CIS371 (Roth/Martin): Datapath and Control


4

Implementing an ISA

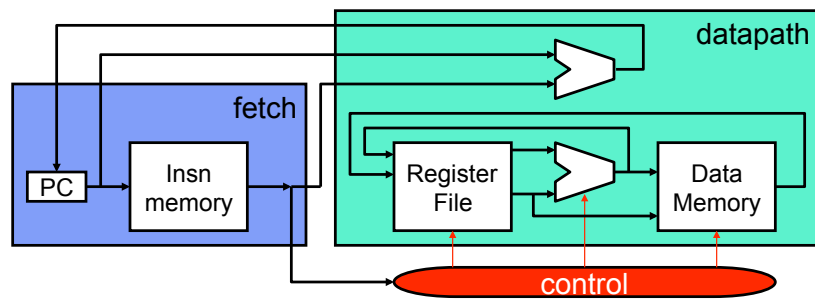

- **Datapath**: performs computation (registers, ALUs, etc.)
 - ISA specific: can implement every insn (single-cycle: in one pass!)
- **Control**: determines which computation is performed
 - Routes data through datapath (which regs, which ALU op)
- **Fetch**: get insn, translate opcode into control
- **Fetch** → **Decode** → **Execute** "cycle"

Two Types of Components

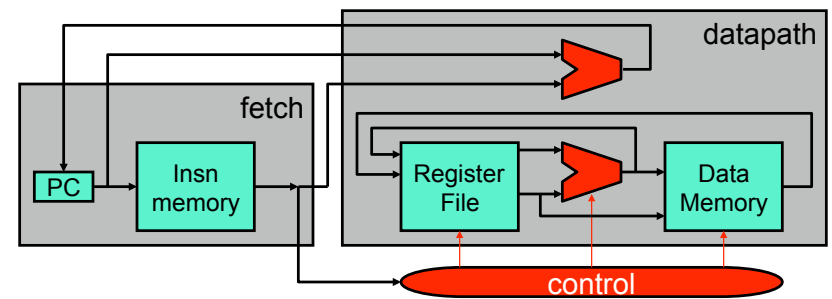


- **Purely combinational**: stateless computation
 - ALUs, muxes, control
 - Arbitrary Boolean functions
- **Combinational/sequential**: storage
 - PC, insn/data memories, register file
 - Internally contain some combinational components


Digital Logic Review

Building Blocks: Logic Gates

 - **Logic gates**: implement Boolean functions
 - Basic gates: NOT, NAND, NOR
 - Underlying CMOS transistors are naturally inverting (● = NOT)



- NAND, NOR are "Boolean complete"

 

Boolean Functions and Truth Tables

- Any Boolean function can be represented as a truth table
 - Truth table:** point-wise input \rightarrow output mapping
 - Function is disjunction of all rows in which "Out" is 1

A, B, C \rightarrow Out

0, 0, 0 \rightarrow 0
 0, 0, 1 \rightarrow 0
 0, 1, 0 \rightarrow 0
 0, 1, 1 \rightarrow 0
 1, 0, 0 \rightarrow 0
 1, 0, 1 \rightarrow 1
 1, 1, 0 \rightarrow 1
 1, 1, 1 \rightarrow 1


- Example above: $Out = AB'C + ABC' + ABC$

Truth Tables and PLAs

- Implement Boolean function by implementing its truth table
 - Takes two levels of logic
 - Assumes inputs and inverses of inputs are available (usually are)
 - First level: ANDs (product terms)
 - Second level: ORs (sums of product terms)
- PLA (programmable logic array)**
 - Flexible circuit for doing this

PLA Example

 - PLA with 3 inputs, 2 outputs, and 4 product terms
 - $Out0 = AB'C + ABC' + ABC$



Boolean Algebra

- Boolean Algebra:** rules for rewriting Boolean functions
 - Useful for simplifying Boolean functions
 - Simplifying = reducing gate count, reducing gate "levels"
 - Rules: similar to logic (0/1 = F/T)
 - Identity:** $A1 = A, A+0 = A$
 - 0/1:** $A0 = 0, A+1 = 1$
 - Inverses:** $(A')' = A$
 - Idempotency:** $AA = A, A+A = A$
 - Tautology:** $AA' = 0, A+A' = 1$
 - Commutativity:** $AB = BA, A+B = B+A$
 - Associativity:** $A(BC) = (AB)C, A+(B+C) = (A+B)+C$
 - Distributivity:** $A(B+C) = AB+AC, A+(BC) = (A+B)(A+C)$
 - DeMorgan's:** $(AB)' = A'+B', (A+B)' = A'B'$

Logic Minimization

- **Logic minimization**
 - Iterative application of rules to reduce function to simplest form
 - There are tools for automatically doing this
 - Example below: function from slide #8

```


Out = AB'C + ABC' + ABC
Out = A(B'C + BC' + BC) // distributivity
Out = A(B'C + (BC' + BC)) // associativity
Out = A(B'C + B(C'+C)) // distributivity (on B)
Out = A(B'C + B1) // tautology
Out = A(B'C + B) // 0/1
Out = A((B'+B)(C+B)) // distributivity (on +B)
Out = A(1(B+C)) // tautology
Out = A(B+C) // 0/1
    
```

Non-Arbitrary Boolean Functions

- PLAs implement Boolean functions point-wise
 - E.g., represent $f(X) = X+5$ as $[0 \rightarrow 5, 1 \rightarrow 6, 2 \rightarrow 7, 3 \rightarrow 8, \dots]$
 - Mainly useful for "arbitrary" functions, no compact representation
- Many useful Boolean functions are not arbitrary
 - Have a compact representation
 - E.g., represent $f(X) = X+5$ as $X+5$
 - Examples
 - Decoder
 - Multiplexer
 - Adder: e.g., $X+5$ (or more generally, $X+Y$)


Decoder

 - **Decoder**: converts binary integer to 1-hot representation
 - Binary representation of $0 \dots 2^N - 1$: N bits
 - 1 hot representation of $0 \dots 2^N - 1$: 2^N bits
 - J represented as J^{th} bit 1, all other bits zero
 - Example below: 2-to-4 decoder



Multiplexer (Mux)

 - **Multiplexer (mux)**: selects output from N inputs
 - Example: 1-bit 4-to-1 mux
 - Not shown: N -bit 4-to-1 mux = N 1-bit 4-to-1 muxes + 1 decoder



Adder


- **Adder:** adds/subtracts two 2C binary integers
 - **Half adder:** adds two 1-bit "integers", no carry-in
 - **Full adder:** adds three 1-bit "integers", includes carry-in
 - **Ripple-carry adder:** N chained full adders add 2 N-bit integers
 - **To subtract:** negate B input, set bit 0 carry-in to 1

Full Adder

- What is the logic for a full adder?


- Look at truth table

CI	A	B	→	CO	S
0	0	0	→	0	0
0	0	1	→	0	1
0	1	0	→	0	1
0	1	1	→	1	0
1	0	0	→	0	1
1	0	1	→	1	0
1	1	0	→	1	0
1	1	1	→	1	1

 


- $S = C'A'B + C'AB' + CA'B' + CAB = C \wedge A \wedge B$
- $CO = C'AB + CA'B + CAB' + CAB = CA + CB + AB$

N-bit Adder/Subtractor

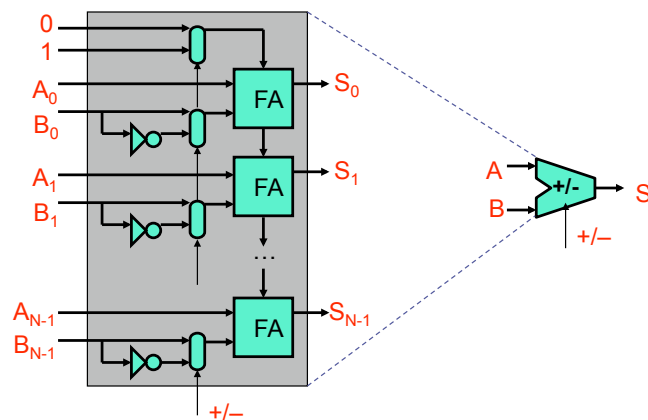


- More later when we cover arithmetic

Sequential Logic & Synchronous Systems

 

- Processors are complex finite state machines (FSMs)
 - Combinational (compute) blocks separated by storage elements
 - State storage: memories, registers, etc.
- **Synchronous systems**
 - **Clock:** global signal acts as write enable for all storage elements
 - Typically marked as triangle
 - All state elements write together, values move forward in lock-step
 - + Simplifies design: design combinational blocks independently
- Aside: asynchronous systems
 - Same thing, but ... no clock
 - Values move forward using explicit handshaking
 - ± May have some advantages, but difficult to design


Datapath Storage Elements

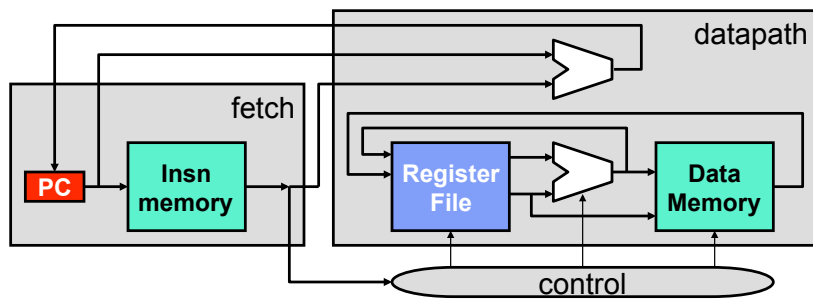

- Three main types of storage elements
 - **Singleton registers:** PC
 - **Register files:** ISA registers
 - **Memories:** insn/data memory

Cross-Coupled Inverters (CCIs)

 - **Cross-coupled inverters (CCIs)**
 - **Primitive "storage element" for storing state**
 - Most storage arrays (regfile, caches) implemented this way
 - Where is the input and where is the output?




S-R Latch

• S-R (set-reset) latch

- Cross-coupled NOR gates
- Distinct inputs/outputs

S, R	Q
0, 0	o1dQ
0, 1	0
1, 0	1
1, 1	0

 

- S=0, R=0? circuit degenerates to cross-coupled INVs
- S=1, R=1? not very useful
- Not really used ... except as component in something else


D Latch

• D latch: S-R latch + ...

- control that makes S=R=1 impossible


E, D	Q
0, 0	o1dQ
0, 1	o1dQ
1, 0	0
1, 1	1

 - In other words
 - 0, D → o1dQ
 - 1, D → D
- In words
 - When E is 1, Q gets D
 - When E is 0, Q retains old value




Timing Diagrams

 - Voltage {0,1} diagrams for different nodes in system
 - "Digitally stylized": changes are vertical lines (instantaneous?)
 - Reality is analog, changes are continuous and smooth
- Timing diagram for a D latch





Triggering: Level vs. Edge

 

- The D-latch is **level-triggered**
 - The latch is open for writing as long as E is 1
 - If D changes continuously, so does Q
 - May not be the functionality we want
- Often easier to reason about an **edge-triggered** latch
 - The latch is open for writing only on E transition (0 → 1 or 1 → 0)
 - + Don't need to worry about fluctuations in value of D


D Flip-Flop

  - **D Flip-Flop**: also called master-slave flip-flop
 - Sequential D-latches
 - Enabled by inverse signals
 - First latch open when E = 0
 - Second latch open when E = 1
 - Overall effect?
 - D FF latches D on 0→1 transition
 - E is the "clock" signal input




FF_{WE}: FF with Separate Write Enable

 - **FF_{WE}**: FF with separate write enable
 - FF D(ata) input is MUX of D and Q, WE selects




- Alternative: FF E(nable) input is AND of CLK and WE
 - + Fewer gates
 - Creates timing problems
 - Do not try to do logic on CLK in Verilog
 - No, really.

Singleton Register

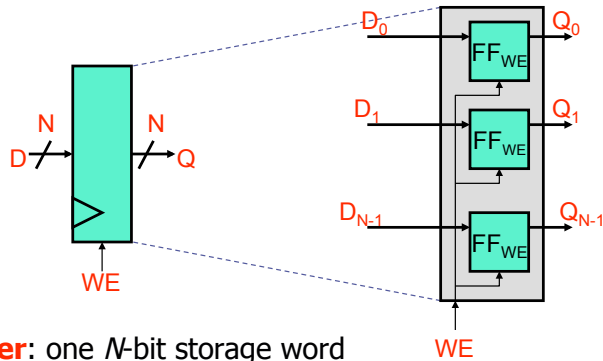


- **Register:** one N -bit storage word
 - Non-multiplexed input/output: data buses write/read same word
- **Implementation:** FF_{WE} array with shared write-enable (WE)
 - FFs written on CLK edge if WE is 1 (or if there is no WE)

Register File

 


- **Register file:** M N -bit storage words
 - Multiplexed input/output: data buses write/read "random" word
- **"Port":** set of buses for accessing a random word in array
 - Data bus (N -bits) + address bus ($\log_2 M$ -bits) + optional WE bit
 - P ports = P parallel and independent accesses
- MIPS integer register file
 - 32 32-bit words, two read ports + one write port (why?)

Register File (Port) Implementation

 


- Register file with four registers

Add a Read Port

 


- Output of each register into 4to1 mux ($RSrc1Val$)
 - $RS1$ is select input of $RSrc1Val$ mux

Add Another Read Port

 


- Output of each register into another 4to1 mux (RSrc2Val)
 - RS2 is select input of RSrc2Val mux

Add a Write Port

 

- Input RegDestVal into each register
 - Enable only one register's WE: (Decoded RD) & (WE)
- What if we needed two write ports?


Another Useful Component: Memory

 

- Register file: M N-bit storage words
 - Few words (< 256), many ports, dedicated read and write ports
 - Synchronous
- **Memory**: M N-bit storage words, yet not a register file
 - Many words (> 1024), few ports (1, 2), shared read/write ports
- Leads to different implementation choices
 - Lots of circuit tricks and such

MIPS Datapath & Control

Unified vs Split Memory Architecture

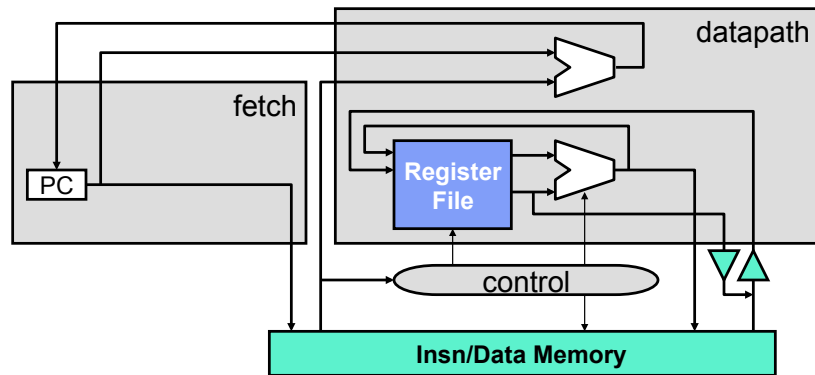


- **Unified architecture:** unified insn/data memory
 - LC3, MIPS, every other ISA
- **Harvard architecture:** split insn/data memories
 - LC4

Datapath for MIPS ISA

- Registers in MIPS are \$0, \$2... \$31
- Consider only the following instructions


add \$1,\$2,\$3	\$1 = \$2 + \$3	(add)
addi \$1,2,\$3	\$1 = 2 + \$3	(add immed)
lw \$1,4(\$3)	\$1 = Memory[4+\$3]	(load)
sw \$1,4(\$3)	Memory[4+\$3] = \$1	(store)
beq \$1,\$2,PC_relative_target	(branch equal)	
j absolute_target	(unconditional jump)	
- Why only these?
 - Most other instructions are the same from datapath viewpoint
 - The one's that aren't are left for you to figure out

Start With Fetch

 


- PC and instruction memory (Harvard architecture, for now)
- A +4 incremter computes default next instruction PC

First Instruction: add

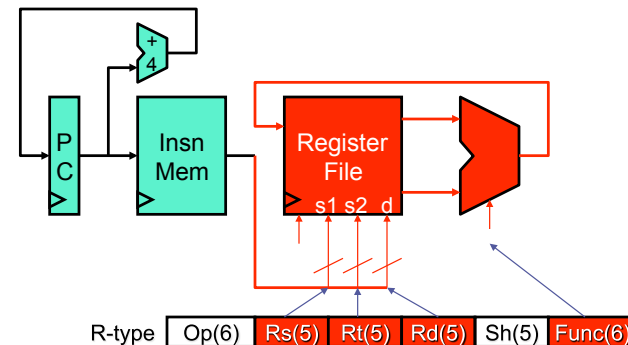


- Add register file and ALU

Second Instruction: **addi**

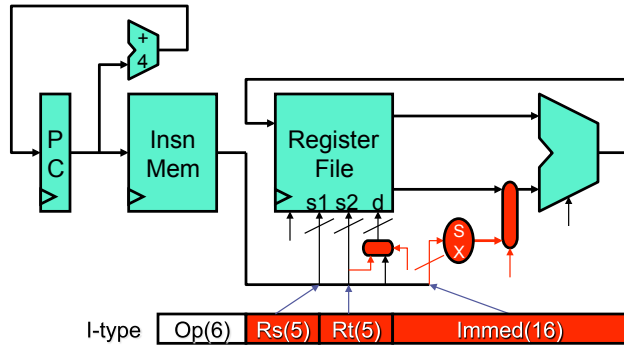


- Destination register can now be either Rd or Rt
- Add sign extension unit and mux into second ALU input

Third Instruction: **lw**

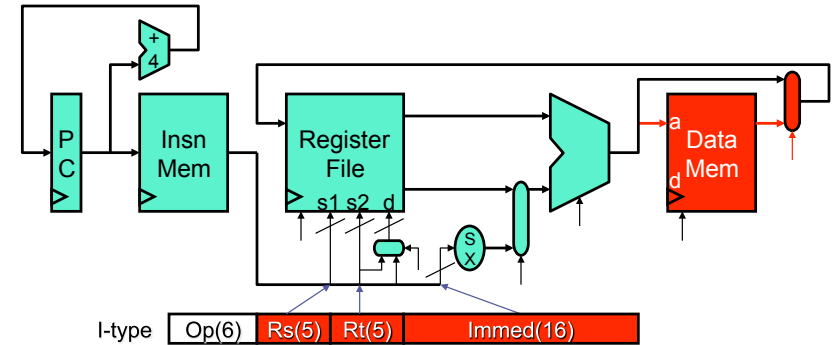


- Add data memory, address is ALU output
- Add register write data mux to select memory output or ALU output

Fourth Instruction: **sw**

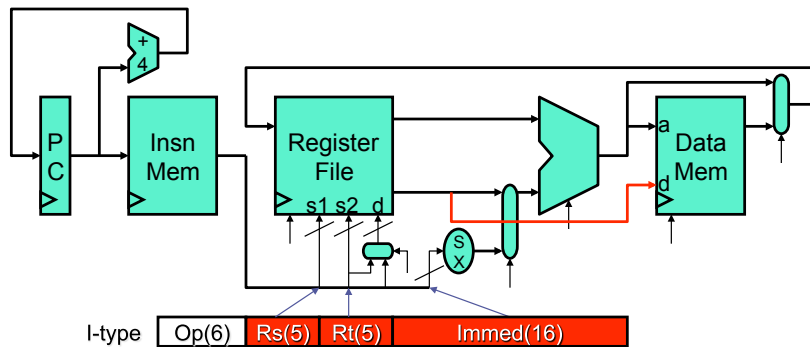


- Add path from second input register to data memory data input

Fifth Instruction: **beq**

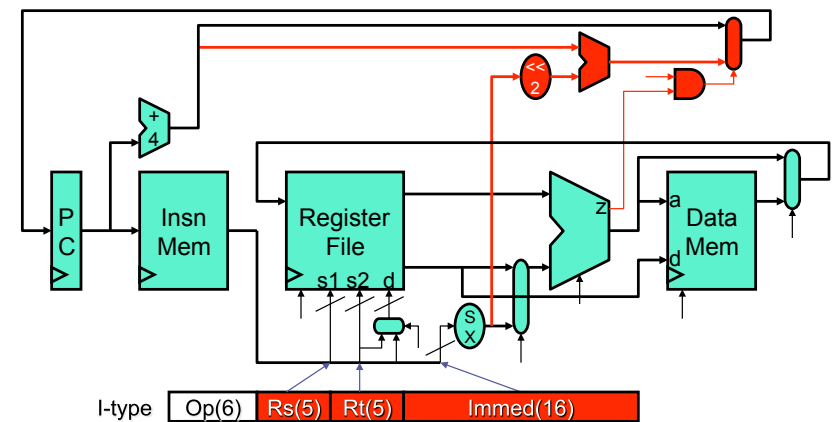

- Add left shift unit and adder to compute PC-relative branch target
- Add PC input mux to select PC+4 or branch target


Sixth Instruction: **j**

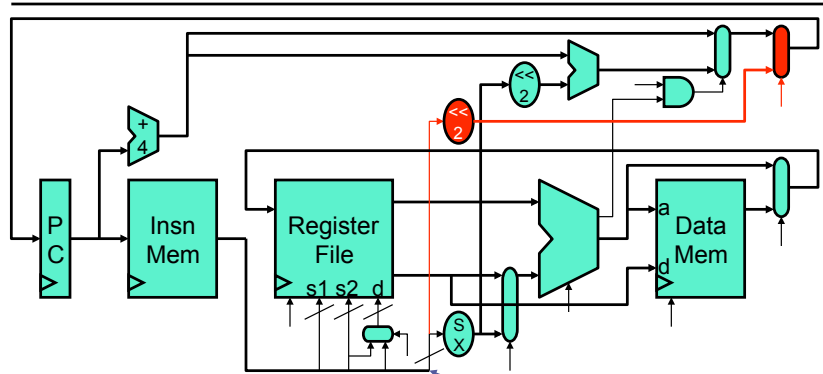

J-type Op(6) Immed(26)


- Add shifter to compute left shift of 26-bit immediate
- Add additional PC input mux for jump target

"Continuous Read" Datapath Timing

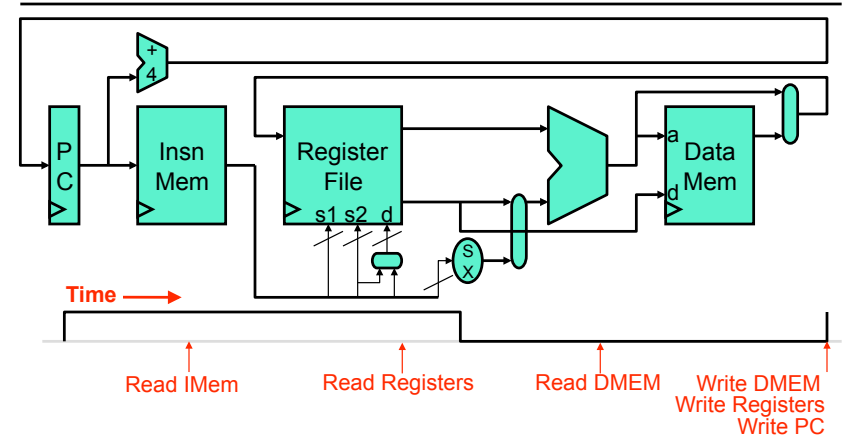


- Works because writes (PC, RegFile, DMem) are independent
- And because no read logically follows any write

What Is Control?

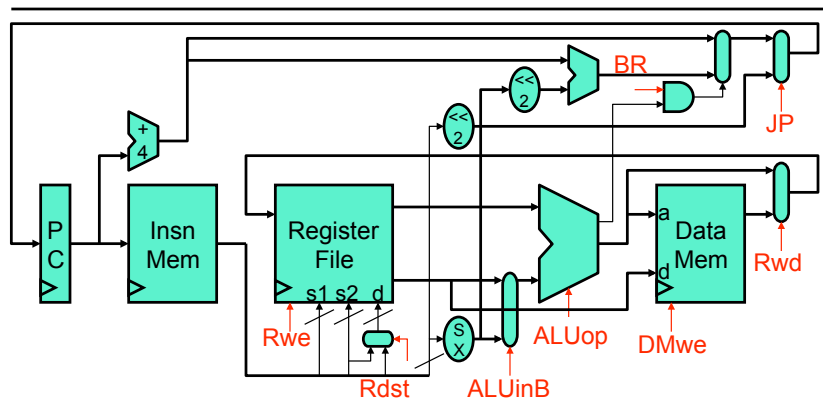


- 9 signals control flow of data through this datapath
 - MUX selectors, or register/memory write enable signals
 - A real datapath has 300-500 control signals

Example: Control for **add**

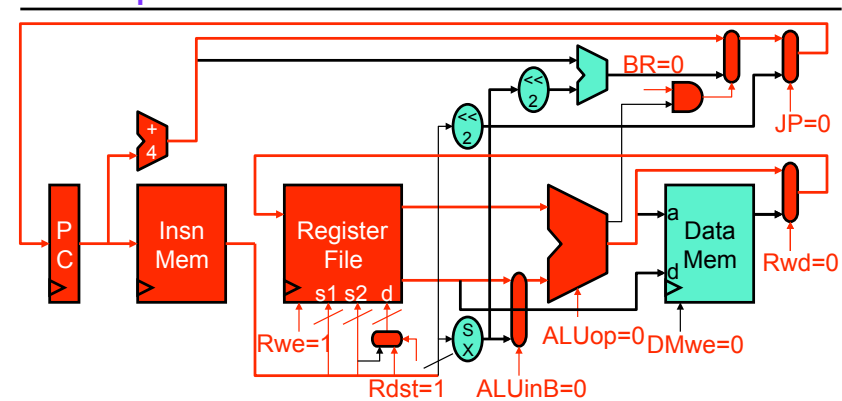


Example: Control for **sw**

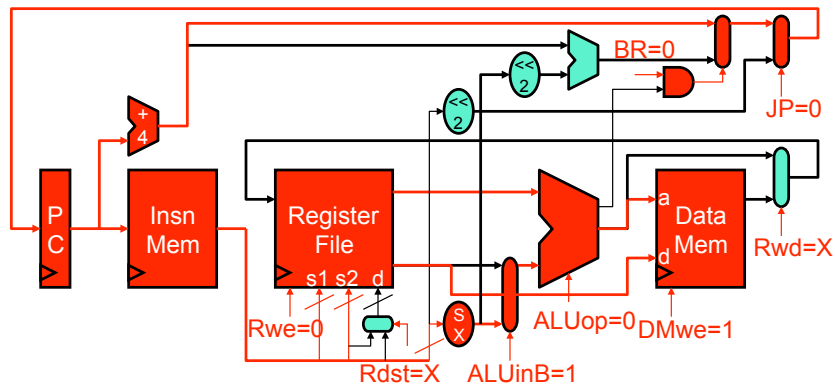


- Difference between **sw** and **add** is 5 signals
 - 3 if you don't count the X (don't care) signals

Example: Control for **beq**

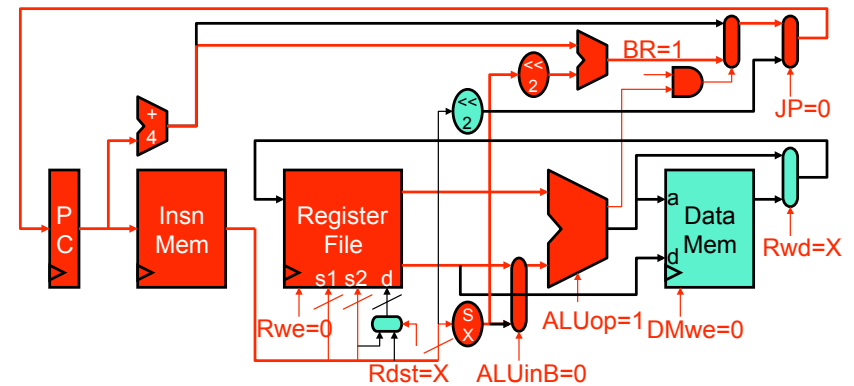

- Difference between **sw** and **beq** is only 4 signals

How Is Control Implemented?

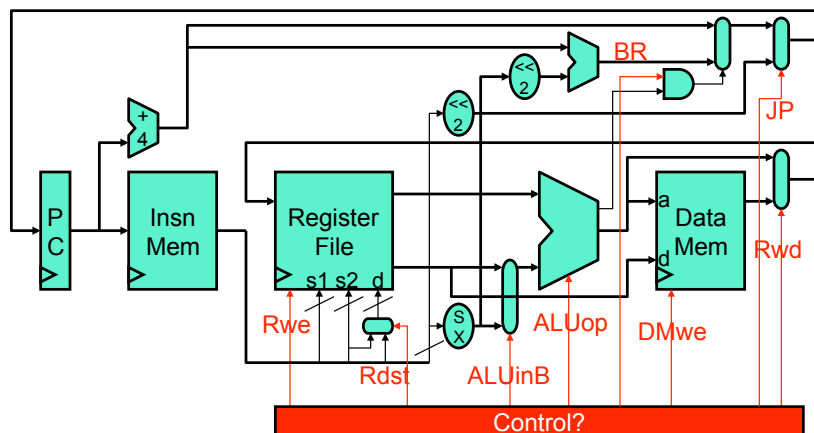


Implementing Control

- Each instruction has a unique set of control signals
 - Most are function of opcode
 - Some may be encoded in the instruction itself
 - E.g., the ALUOp signal is some portion of the MIPS Func field
 - Simplifies controller implementation
 - Requires careful ISA design

Control Implementation: ROM

 - **ROM (read only memory)**: like a RAM but unwritable
 - Bits in data words are control signals
 - Lines indexed by opcode
 - Example: ROM control for 6-insn MIPS datapath
 - X is "don't care"




CIS371 (Roth/Martin): Datapath and Control

53

Control Implementation: Logic

 
- Real machines have 100+ insns 300+ control signals
 - 30,000+ control bits (~4KB)
 - Not huge, but hard to make faster than datapath (important!)
- Alternative: **logic gates** or "random logic" (unstructured)
 - Exploits the observation: many signals have few 1s or few 0s
 - Example: random logic control for 6-insn MIPS datapath



CIS371 (Roth/Martin): Datapath and Control

54


Datapath and Control Timing

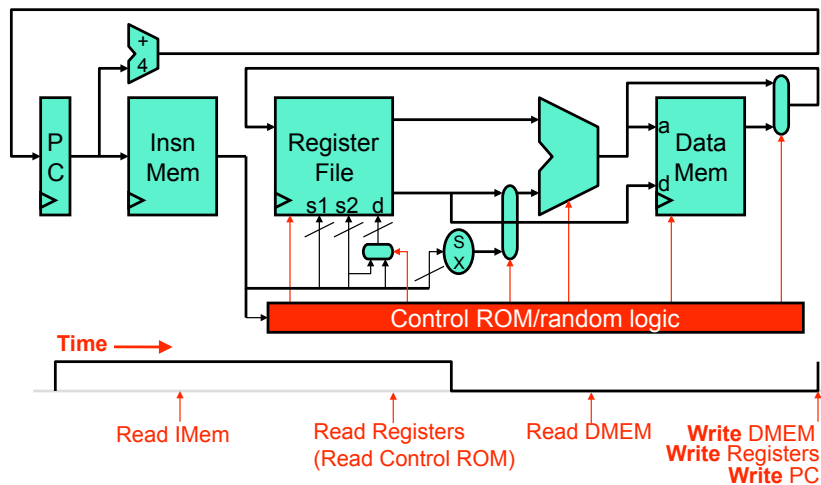

CIS371 (Roth/Martin): Datapath and Control

55

Single-Cycle Datapath Performance

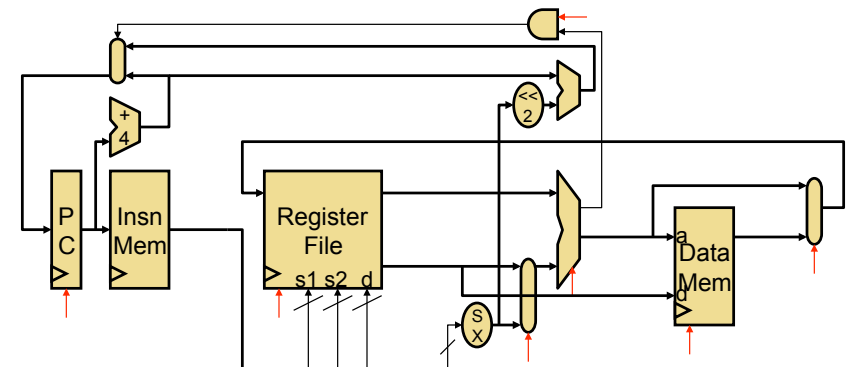


- One instruction per cycle (1 IPC or 1 CPI)
- Clock cycle time proportional to worst-case logic delay
 - In this datapath: insn fetch, decode, register read, ALU, data memory access, write register
 - Can we do better?

CIS371 (Roth/Martin): Datapath and Control


56

Foreshadowing: Pipelined Datapath

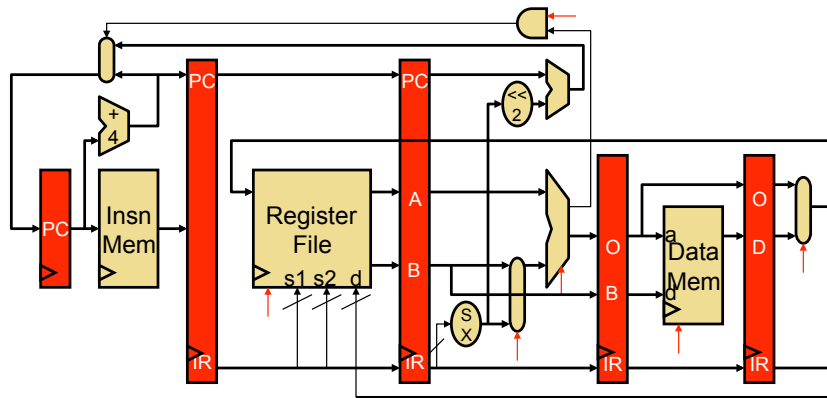

- Split datapath into multiple stages
 - Assembly line analogy
 - 5 stages results in up to 5x clock & performance improvement

Summary

 

- Digital logic review
- Single-cycle datapath and control
- Next up:
 - Arithmetic
 - Performance & metrics