

Basic Components

Based on slides © McGraw-Hill
Additional material © 2004/2005 Lewis/Martin
Modified by Diana Palsetia

Components of a Computer

Combinational Structures/Circuits

- Always gives the same output for a given set of inputs
- Do not store any information
- Examples: adder, subtracter, multiplexer (mux), decoder

Sequential Structures/Circuits

- Combination of Combinational Structure and Memory Elements
- Store Information
- Example: memory, and state machine


CIT 593

2/21

Adder

Adder

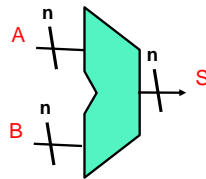- A and B are operands
- S is the result of the addition
- Write now we are not interested in how it works (CIT 595 goes in detail)



Black box view of the Adder


CIT 593

3/21

Subtractor

Build a subtracter from an adder

- Calculate $A - B = A + -B$
- Recall 2's complement!!
- Negate B
- Recall $-B = \text{NOT}(B) + 1$

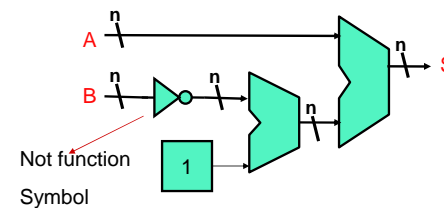


CIT 593

4/21

Multiplexer (MUX)

Selector/Chooser of value (electrical voltages)

- Multi-way switch

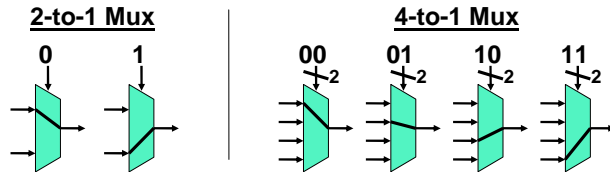

In general

- N select bits chooses from 2^N inputs
- An incredibly useful building block

CIT 593

5/21

More on Representing Multi-bit Values

Number bits from right (0) to left (n-1)

- Just a convention -- could be left to right, but must be consistent

Use brackets to denote range:

- $D[l:r]$ denotes bit l to bit r, from *left to right*


$A = \overset{14}{0} \overset{12}{1} \overset{8}{0} \overset{4}{0} \overset{0}{1} 0101$

$A[14:9] = 101001$

$A[2:0] = 101$

May also see $A\langle 14:9 \rangle$

- Especially in hardware block diagrams

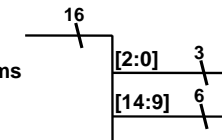

CIT 593

6/21


Decoder

Decodes information

- Undoing the encoding so that the original information can be retrieved

n -bit inputs, 2^n outputs

- Exactly one output is **1** or **ON** or **TRUE** for each possible input pattern
- Example: 2 to 4 decoder

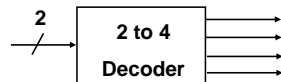

CIT 593

7/21

Overview of Sequential Structure/Circuit

Sequential Structure/Circuit

- Stores information – contains storage element
- **Output** depends on stored information (**state**) plus **input**
 - Given **input** might produce different outputs, depending on stored information
 - **State** = snapshot of all relevant elements of system at moment snapshot is taken
- Example:
 - **state** = Score board of basketball game (number of points, time remaining, possession)
 - **input** = which team scored the point
 - **output** = point increase for the team that just scored

Useful for building memory (ROM/RAM/Registers) and state machines (E.g. Vending Machine)


CIT 593

8/21

Storage Unit

Storage Unit a.k.a a flip-flop

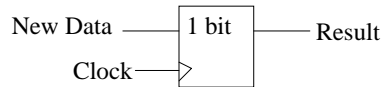- Stores 1 bit of Information
- Data is changed on an event (a.k.a a clock*)
 - Do not want to change data abruptly
 - Event provides consistency



*clock is a pulse that generated using electronic circuitry
if clock = '1' then new data stored else stored value remains


CIT 593

9/21

Sequential: Memory

Memory (logical view)

- Holds information (e.g. phone directory contains phone numbers)
- a logical k by m array of stored bits

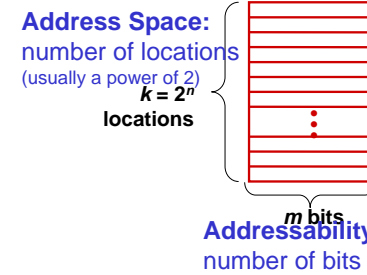

CIT 593

10/21

Memory Size

Terminology First

- Decimal system short form for large denominations
 - 1000 = 1K(thousand), 1,000,000 = 1M (million)
- Binary Systems sort notation for large denominations
 - 1 Byte = $2^3 = 8$ bits
 - 1 Kilo Byte (KB) = 1024 bytes = 2^{10} Bytes = $2^{10} \times 2^3 = 2^{13} = 8192$ bits
 - 1 Mega Byte (MB) = 1024 KB = 2^{20} Bytes = $2^{20} \times 2^3 = 2^{23} = 8388608$ bits
 - 1Giga Byte (GB) = 1024 MB = 2^{30} Bytes = $2^{30} \times 2^3 = 2^{33} = 8589934592$ bits

Example: 16 MB memory = $2^4 \times 2^{20} = 2^{24}$ bytes

- $2^{24} = 16777216$ (~ 16 million) unique locations, each holds a 8-bit value


Addressability can vary

- We can also have manufacture memory such that each memory location hold 16-bit or 32-bit
- Example: LC3 has $2^{16} \times 16 (= 2^4)$ memory = $2^{17} \times 2^3 = 2^{17}$ bytes

CIT 593

11/21


Sequential: Memory as a black box

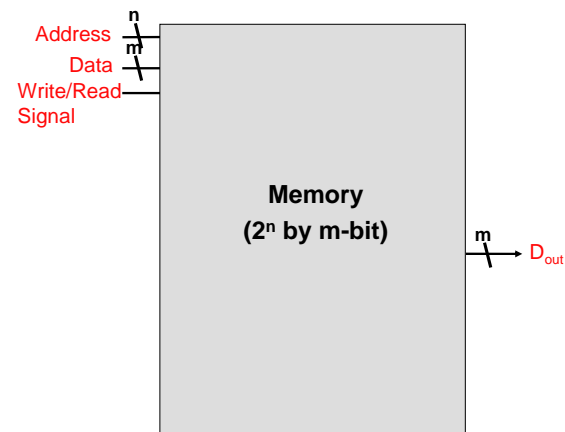

CIT 593

12/21


Memory (1 layer down)

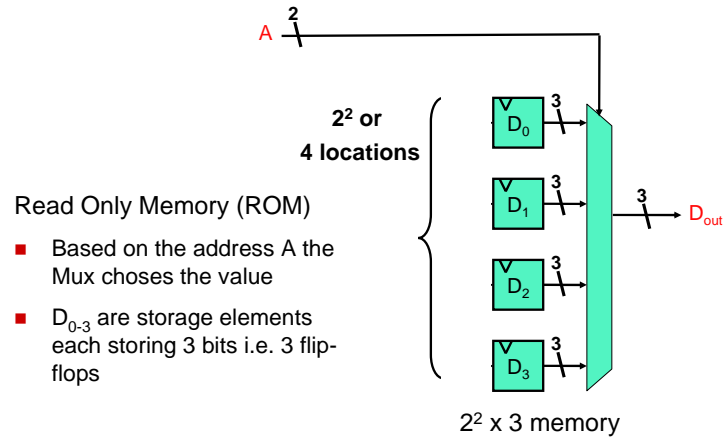

CIT 593

13/21

Memory – Read and Write

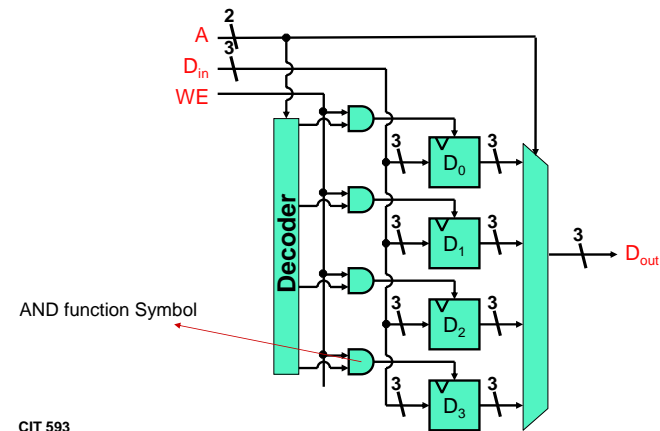

CIT 593

14/21

Sequential: Register File

Small fast memory

- Small – only 8-32 locations. E.g. LC3 has only 8 registers
- Fast – For faster access compared to 256 MB memory
 - This all driven by technology and cost

Used for temporary storage

- To avoid going back and forth to the memory
- For intermediate calculations
 - E.g. (A+B)*C

Analogy: we use our desk to keep a few books (immediate need), and use a bookshelf to store the other books.


CIT 593

15/21

Sequential: State Machine

Another type of sequential structure

- Combines combinational structure with storage (memory element)
- “Remembers” state (past information), and changes output (and state) based on **inputs** and **current state**

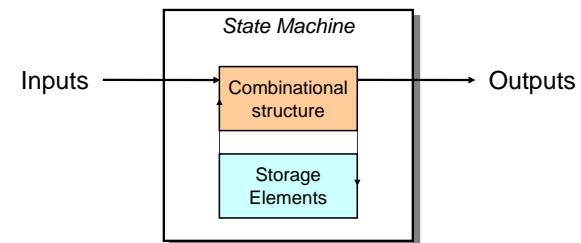


CIT 593

16/21


Combinational vs. Sequential Example

Two types of “combination” locks

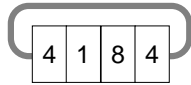

Combinational

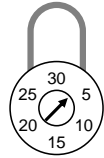Success depends only on the **values**, not the order in which they are set.



Sequential


Success depends on the **sequence** of values (e.g, R-13, L-22, R-3).

CIT 593

17/21

Sequential Lock State Diagram

Shows **states** and **actions** that cause a **transition** between states

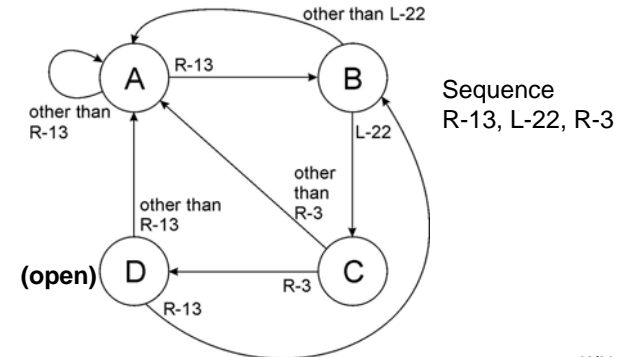

CIT 593

18/21

State of Sequential Lock

Our lock example has four different states, labeled A-D:

- A:** The lock is **not open**, and no relevant operations have been performed
- B:** The lock is **not open**, and the user has completed the **R-13** operation
- C:** The lock is **not open**, and the user has completed **R-13**, followed by **L-22**
- D:** The lock is **open**

CIT 593

19/21

Storage elements for sequential circuits

Recall that flip-flop/storage unit stores one bit

- State can be 0 or 1

Number of storage elements (flip-flops)

- Determined by number of states (and representation of states)

Examples

- Sequential lock
 - Four states – two bits



- Basketball scoreboard
 - 8 bits for each score, 6 bits for playtime minutes and seconds, 1 bit for possession arrow,

CIT 593

20/21

Next

Put all the components together and we have a working computer

- **Combinational Elements:** Adder, Decoder
 - Forms the Arithmetic & Logic Unit a.k.a ALU which does all the processing

- **Sequential Elements:**
 - Memory: Registers (temp storage), Memory (storage while power is on)
 - Control a.k.a brain of the computer : Co-ordinate control signals and data movement to and from memory and I/O