

# CIS 371 Computer Organization and Design

## Unit 3: Arithmetic

Based on slides by Prof. Amir Roth & Prof. Milo Martin

CIS 371 (Martin): Arithmetic

1


## Readings

- P&H
  - Chapter 3
  - You can skim Section 3.5 (Floating point)

CIS 371 (Martin): Arithmetic

3

## This Unit: Arithmetic

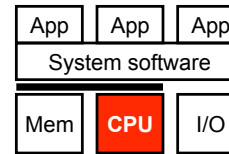

- A little review
  - Binary + 2s complement
  - Ripple-carry addition (RCA)
- Fast integer addition
  - Carry-select (CSeA)
- Shifters
- Integer Multiplication and division
- Floating point arithmetic

CIS 371 (Martin): Arithmetic

2

## Pre Class Exercise

$$\begin{array}{r} 43 = 00101011 \\ + 29 = 00011101 \\ \hline \end{array}$$


$$3 \overline{)29} = 0011 \overline{)011101}$$

$$\begin{array}{r} 19 = 010011 \\ * 12 = 001100 \\ \hline \end{array}$$

CIS 371 (Martin): Arithmetic

4

## The Importance of Fast Arithmetic

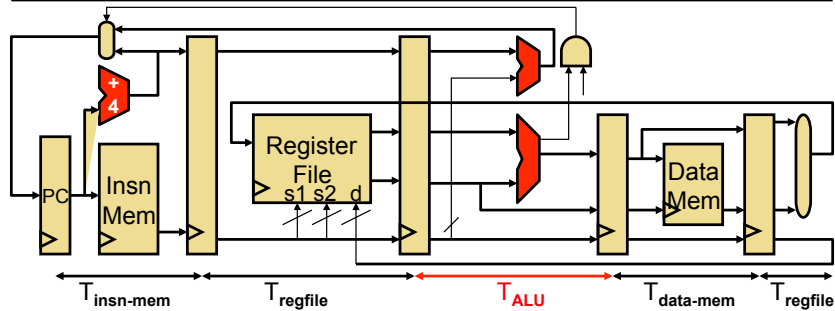

- Addition of two numbers is most common operation
  - Programs use addition frequently
  - Loads and stores use addition for address calculation
  - Branches use addition to test conditions and calculate targets
  - All insns use addition to calculate default next PC
- Fast addition critical to high performance

## Fixed Width

- On pencil and paper, integers have infinite width
- In hardware, integers have **fixed width**
  - N bits: 16, 32 or 64
  - LSB is  $2^0$ , MSB is  $2^{N-1}$
  - **Range:** 0 to  $2^N-1$
- Numbers  $>2^N$  represented using multiple fixed-width integers
  - In software

## Review: Binary Integers

- Computers represent integers in binary (base2)
  - $3 = 11$ ,  $4 = 100$ ,  $5 = 101$ ,  $30 = 11110$
  - + Natural since only two values are represented
  - Addition, etc. take place as usual (carry the 1, etc.)

$$\begin{array}{r} 17 = 10001 \\ +5 = 101 \\ \hline 22 = 10110 \end{array}$$

- Some old machines use decimal (base10) with only 0/1
  - $30 = 011\ 000$
  - Unnatural for digital logic, implementation complicated & slow

## What About Negative Integers?

- **Sign/magnitude**
  - Unsigned plus one bit for sign
  - $10 = 00001010$ ,  $-10 = 10001010$
  - + Matches our intuition from "by hand" decimal arithmetic
  - Both 0 and  $-0$
  - Addition is difficult
  - Range:  $-(2^{N-1}-1)$  to  $2^{N-1}-1$
- Option II: **two's complement (2C)**
  - Leading 0s mean positive number, leading 1s negative
  - $10 = 00001010$ ,  $-10 = 11110110$
  - + One representation for 0
  - + Easy addition
  - Range:  $-(2^{N-1})$  to  $2^{N-1}-1$

## The Tao of 2C

---

- How did 2C come about?
  - "Let's design a representation that makes addition easy"
  - Think of subtracting 10 from 0 by hand
  - Have to "borrow" 1s from some imaginary leading 1

$$\begin{array}{r} 0 = 100000000 \\ -10 = \underline{00001010} \\ -10 = 011110110 \end{array}$$

- Now, add the conventional way...

$$\begin{array}{r} -10 = 11110110 \\ +10 = \underline{00001010} \\ 0 = 100000000 \end{array}$$

## Addition

## Still More On 2C

---

- What is the interpretation of 2C?
  - Same as binary, except **MSB represents  $-2^{N-1}$** , not  $2^{N-1}$ 
    - $-10 = 11110110 = -2^7 + 2^6 + 2^5 + 2^4 + 2^2 + 2^1$
  - + Extends to any width
    - $-10 = 110110 = -2^5 + 2^4 + 2^2 + 2^1$
    - Why?  $2^N = 2 * 2^{N-1}$
    - $-2^5 + 2^4 + 2^2 + 2^1 = (-2^6 + 2 * 2^5) - 2^5 + 2^4 + 2^2 + 2^1 = -2^6 + 2^5 + 2^4 + 2^2 + 2^1$
- Trick to negating a number quickly:  **$-B = B' + 1$** 
  - $-(1) = (0001)' + 1 = 1110 + 1 = 1111 = -1$
  - $-(-1) = (1111)' + 1 = 0000 + 1 = 0001 = 1$
  - $-(0) = (0000)' + 1 = 1111 + 1 = 0000 = 0$
  - Think about why this works

## 1st Grade: Decimal Addition

---

$$\begin{array}{r} 1 \\ 43 \\ +29 \\ \hline 72 \end{array}$$

- Repeat N times
  - Add least significant digits and any overflow from previous add
  - Carry "overflow" to next addition
    - **Overflow**: any digit other than least significant of sum
  - Shift two addends and sum one digit to the right
- Sum of two N-digit numbers can yield an N+1 digit number

## Binary Addition: Works the Same Way

```

  1   111111
 43 = 00101011
+29 = 00011101
-----
 72 = 01001000
  
```


- Repeat N times
  - Add least significant bits and any overflow from previous add
  - Carry the overflow to next addition
  - Shift two addends and sum one bit to the right
- Sum of two N-bit numbers can yield an N+1 bit number
- More steps (smaller base)
- + Each one is simpler (adding just 1 and 0)
  - So simple we can do it in hardware

## The Half Adder

- How to add two binary integers in hardware?
- Start with adding two bits
  - When all else fails ... look at truth table

A	B	CO	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 
- $S = A \oplus B$
- $CO \text{ (carry out)} = AB$
- This is called a **half adder**



## The Other Half

- We could chain half adders together, but to do that...
  - Need to incorporate a carry out from previous adder


C	A	B	CO	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

- $S = C'A'B + C'AB' + CA'B' + CAB = C \oplus A \oplus B$
- $CO = C'AB + CA'B + CAB' + CAB = CA + CB + AB$
- This is called a **full adder**
 
## Ripple-Carry Adder

- N-bit **ripple-carry** adder
  - N 1-bit full adders "chained" together
    - $CO_0 = CI_1, CO_1 = CI_2$ , etc.
    - $CI_0 = 0$
    - $CO_{N-1}$  is carry-out of entire adder
      - $CO_{N-1} = 1 \rightarrow$  "overflow"
- Example: 16-bit ripple carry adder
  - How fast is this?
  - How fast is an N-bit ripple-carry adder?




## Quantifying Adder Delay

- Combinational logic dominated by gate (transistor) delays
  - Array storage dominated by wire delays
  - Longest delay or “critical path” is what matters
- Can implement any combinational function in “2” logic levels
  - 1 level of AND + 1 level of OR (PLA)
  - NOTs are “free”: push to input (DeMorgan’s) or read from latch
  - Example: delay(FullAdder) = 2
    - $d(\text{CarryOut}) = \text{delay}(AB + AC + BC)$
    - $d(\text{Sum}) = d(A \wedge B \wedge C) = d(AB'C' + A'BC' + ABC' + ABC) = 2$
    - Note '^' means Xor (just like in C & Java)
- Caveat: “2” assumes gates have few (<8 ?) inputs

## Fast Addition
 
## Ripple-Carry Adder Delay

- Longest path is to  $CO_{15}$  (or  $S_{15}$ )
  - $d(CO_{15}) = 2 + \text{MAX}(d(A_{15}), d(B_{15}), d(CI_{15}))$ 
    - $d(A_{15}) = d(B_{15}) = 0$ ,  $d(CI_{15}) = d(CO_{14})$
  - $d(CO_{15}) = 2 + d(CO_{14}) = 2 + 2 + d(CO_{13}) \dots$
  - **$d(CO_{15}) = 32$**
- **$D(CO_{N-1}) = 2N$** 
  - **Too slow!**
  - **Linear in number of bits**
- Number of gates is also linear



## Bad idea: a PLA-based Adder?


- If any function can be expressed as two-level logic...
  - ...why not use a PLA for an entire 8-bit adder?
- Not small
  - Approx.  $2^{15}$  AND gates, each with  $2^{16}$  inputs
  - Then,  $2^{16}$  OR gates, each with  $2^{16}$  inputs
  - Number of gates **exponential in bit width!**
- Not that fast, either
  - An AND gate with 65 thousand inputs != 2-input AND gate
    - Many-input gates made a tree of, say, 4-input gates
    - 16-input gates would have at least 8 logic levels
  - So, at least 16 levels of logic for a 16-bit PLA
  - Even so, delay is still **logarithmic in number of bits**
- There are better (faster, smaller) ways

## Theme: Hardware != Software

- Hardware can do things that software fundamentally can't
  - And vice versa (of course)
- In hardware, it's easier to trade **resources** for **latency**
- One example of this: **speculation**
  - Slow computation is waiting for some slow input?
  - Input one of two things?
  - **Compute with both (slow), choose right one later (fast)**
- Does this make sense in software? Not on a uni-processor
- Difference? hardware is parallel, software is sequential

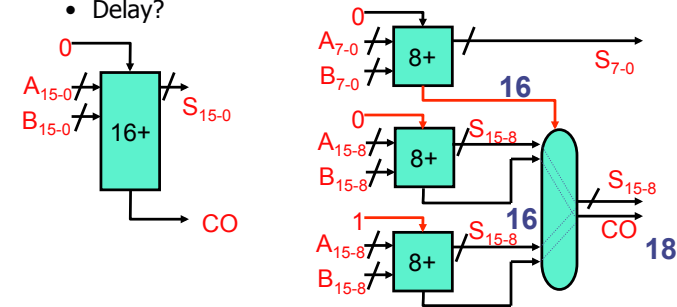
## Carry-Select Adder

- **Carry-select adder**
  - Do  $A_{15-8} + B_{15-8}$  twice, once assuming  $C_8$  ( $CO_7$ ) = 0, once = 1
  - Choose the correct one when  $CO_7$  finally becomes available
  - + Effectively cuts carry chain in half (break critical path)
  - But adds mux
  - Delay?


 
## Multi-Segment Carry-Select Adder

- Multiple segments
  - Example: 5, 5, 6 bit = 16 bit
- Hardware cost
  - Still mostly linear ( $\sim 2x$ )
  - Compute each segment with 0 and 1 carry-in
  - Serial mux chain
- Delay
  - 5-bit adder (10) + Two muxes (4) = 14



## Carry-Select Adder Delay


- What is carry-select adder delay (two segment)?
  - $d(CO_{15}) = \text{MAX}(d(CO_{15-8}), d(CO_{7-0})) + 2$
  - $d(CO_{15}) = \text{MAX}(2*8, 2*8) + 2 = \mathbf{18}$
  - In general:  $\mathbf{2*(N/2) + 2 = N+2}$  (vs  $\mathbf{2N}$  for RCA)
- What if we cut adder into 4 equal pieces?
  - Would it be  $2*(N/4) + 2 = 10$ ? Not quite
  - $d(CO_{15}) = \text{MAX}(d(CO_{15-12}), d(CO_{11-0})) + 2$
  - $d(CO_{15}) = \text{MAX}(2*4, \text{MAX}(d(CO_{11-8}), d(CO_{7-0}))) + 2 + 2$
  - $d(CO_{15}) = \text{MAX}(2*4, \text{MAX}(2*4, \text{MAX}(d(CO_{7-4}), d(CO_{3-0}))) + 2) + 2 + 2$
  - $d(CO_{15}) = \text{MAX}(2*4, \text{MAX}(2*4, \text{MAX}(2*4, 2*4) + 2) + 2) + 2$
  - $d(CO_{15}) = 2*4 + 3*2 = \mathbf{14}$
- N-bit adder in M equal pieces:  $\mathbf{2*(N/M) + (M-1)*2}$ 
  - 16-bit adder in 8 parts:  $2*(16/8) + 7*2 = \mathbf{18}$

## Another Option: Carry Lookahead

- Is carry-select adder as fast as we can go?
  - Nope
- Another approach to using additional resources
  - Instead of redundantly computing sums assuming different carries
  - Use redundancy to compute carries more quickly
    - This approach is called **carry lookahead (CLA)**
 
## Carry Lookahead Adder (CLA)

- Calculate "propagate" and "generate" based on A, B
  - Not based on carry in
- Combine with tree structure
- Prior years: CLA covered in great detail
  - Dozen slides or so
  - Not this year
- Take aways
  - **Tree gives logarithmic delay**
  - Reasonable area



## Adders In Real Processors

- Real processors super-optimize their adders
  - Ten or so different versions of CLA
  - Highly optimized versions of carry-select
  - Other gate techniques: carry-skip, conditional-sum
  - Sub-gate (transistor) techniques: Manchester carry chain
  - Combinations of different techniques
    - Alpha 21264 uses CLA+CSeA+RippleCA
    - Used a different levels
- Even more optimizations for incrementers
  - Why?


 


FIG 10.47 Area vs. delay of synthesized adders
 
## Subtraction: Addition's Tricky Pal

- Sign/magnitude subtraction is mental reverse addition
  - 2C subtraction **is** addition
- How to subtract using an adder?
  - `sub A B = add A -B`
  - Negate B before adding (fast negation trick:  $-B = B' + 1$ )
- Isn't a subtraction then **a negation and two additions**?
  - + No, an adder can implement  $A+B+1$  by setting the carry-in to 1



CIS 371 (Martin): Arithmetic

29

## Shifts & Rotates

CIS 371 (Martin): Arithmetic

30

## Shift and Rotation Instructions

- Left/right shifts are useful...
  - Fast multiplication/division by small constants (next)
  - Bit manipulation: extracting and setting individual bits in words
- Right shifts
  - Can be **logical** (shift in 0s) or **arithmetic** (shift in copies of MSB)
    - `srl 110011, 2 = 001100`
    - `sra 110011, 2 = 111100`
  - Caveat: `sra` is not equal to division by 2 of negative numbers
- Rotations are less useful...
  - But almost "free" if shifter is there
  - MIPS and LC4 have only shifts, x86 has shifts and rotations

CIS 371 (Martin): Arithmetic

31

## Compiler Opt: Strength Reduction

- **Strength reduction**: compilers will do this (sort of)
  - `A * 4 = A << 2`
  - `A * 5 = (A << 2) + A`
  - `A / 8 = A >> 3` (only if A is unsigned)
- Useful for address calculation: all basic data types are  $2^M$  in size
  - `int A[100];`
  - `&A[N] = A+(N*sizeof(int)) = A+N*4 = A+N<<2`




CIS 371 (Martin): Arithmetic

32


   
## A Simple Shifter


- The simplest 16-bit shifter: can only shift left by 1
  - Implement using wires (no logic!)**
- Slightly more complicated: can shift left by 1 or 0
  - Implement using wires and a multiplexor (mux16\_2to1)



## Multiplication
 
## Barrel Shifter

- What about shifting left by any amount 0–15?
  - 16 consecutive “left-shift-by-1-or-0” blocks?
    - Would take too long (how long?)
  - Barrel shifter:** 4 “shift-left-by-X-or-0” blocks (X = 1,2,4,8)
    - What is the delay?



- Similar barrel designs for right shifts and rotations

## 3rd Grade: Decimal Multiplication

$$\begin{array}{r}
 19 \quad // \text{ multiplicand} \\
 * 12 \quad // \text{ multiplier} \\
 \hline
 38 \\
 + 190 \\
 \hline
 228 \quad // \text{ product}
 \end{array}$$

- Start with product 0, repeat steps until no multiplier digits
  - Multiply multiplicand by least significant multiplier digit
  - Add to product
  - Shift multiplicand one digit to the left (multiply by 10)
  - Shift multiplier one digit to the right (divide by 10)
- Product of N-digit, M-digit numbers may have N+M digits

## Binary Multiplication: Same Refrain

```

19 = 010011 // multiplicand
* 12 = 001100 // multiplier
  0 = 000000000000
  0 = 000000000000
 76 = 000001001100
152 = 000010011000
  0 = 000000000000
+  0 = 000000000000
-----
228 = 000011100100 // product
    
```

± Smaller base → more steps, each is simpler

- Multiply multiplicand by **least significant multiplier digit**  
+ 0 or 1 → no actual multiplication, add multiplicand or not
- Add to total: we know how to do that
- Shift multiplicand left, multiplier right by one digit


## Software Multiplication

- Can implement this algorithm in software
- Inputs: `md` (multiplicand) and `mr` (multiplier)

```


int pd = 0; // product
int i = 0;
for (i = 0; i < 16 && mr != 0; i++) {
    if (mr & 1) {
        pd = pd + md;
    }
    md = md << 1; // shift left
    mr = mr >> 1; // shift right
}
    
```

## Hardware Multiply: Iterative

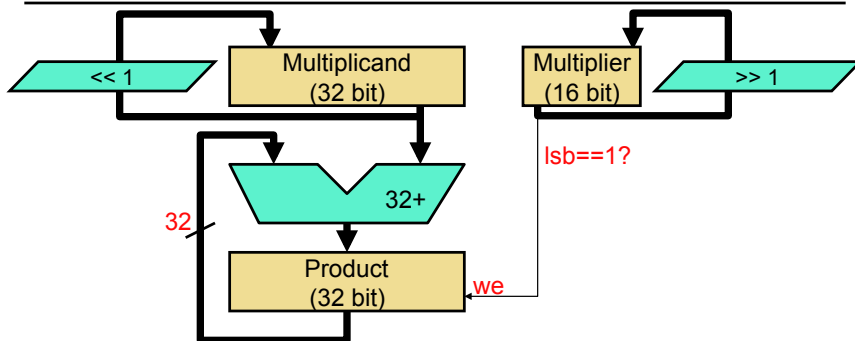


- **Control:** repeat 16 times
  - If least significant bit of multiplier is 1...
    - Then add multiplicand to product
  - Shift multiplicand left by 1
  - Shift multiplier right by 1

## Hardware Multiply: Multiple Adders

 


- Multiply by  $N$  bits at a time using  $N$  adders
  - Example:  $N=5$ , terms ( $P$ =product,  $C$ =multiplicand,  $M$ =multiplier)
  - $P = (M[0] ? (C) : 0) + (M[1] ? (C \ll 1) : 0) + (M[2] ? (C \ll 2) : 0) + (M[3] ? (C \ll 3) : 0) + \dots$
  - Arrange like a tree to reduce gate delay critical path
- Delay?  $N^2$  vs  $N \cdot \log N$ ? Not that simple, depends on adder
  - Approx " $2N$ " versus " $N + \log N$ ", with optimization:  $O(\log N)$

## Consecutive Addition

 

 - 2 N-bit RC adders  
+ 2 + d(add) gate delays
- M N-bit RC adders delay
  - Naïve:  $O(M*N)$
  - Actual:  $O(M+N)$



- M N-bit Carry Select?
  - Delay calculation tricky
- Carry Save Adder (CSA)
  - 3-to-2 CSA tree + adder
  - Delay:  $O(\log M + \log N)$

CIS 371 (Martin): Arithmetic

41

## Hardware != Software: Part Deux

- Recall: hardware is parallel, software is sequential
- Exploit: evaluate independent sub-expressions in parallel
- Example I:  $S = A + B + C + D$ 
  - Software? 3 steps: (1)  $S_1 = A+B$ , (2)  $S_2 = S_1+C$ , (3)  $S = S_2+D$
  - + Hardware? 2 steps: (1)  $S_1 = A+B$ ,  $S_2=C+D$ , (2)  $S = S_1+S_2$
- Example II:  $S = A + B + C$ 
  - Software? 2 steps: (1)  $S_1 = A+B$ , (2)  $S = S_1+C$
  - Hardware? 2 steps: (1)  $S_1 = A+B$  (2)  $S = S_1+C$
  - + Actually hardware can do this in 1.2 steps!
  - Sub-expression parallelism exists below 16-bit addition level

CIS 371 (Martin): Arithmetic

42

## Division

## 4th Grade: Decimal Division

$$\begin{array}{r}
 \underline{9} \\
 3 \mid 29 \\
 \underline{-27} \\
 2
 \end{array}
 \quad
 \begin{array}{l}
 // \text{ quotient} \\
 // \text{ divisor } \mid \text{ dividend} \\
 // \text{ remainder}
 \end{array}$$

- Shift divisor left (multiply by 10) until MSB lines up with dividend's
- Repeat until remaining dividend (remainder) < divisor
  - Find largest single digit q such that  $(q*\text{divisor}) < \text{dividend}$
  - Set LSB of quotient to q
  - Subtract  $(q*\text{divisor})$  from dividend
  - Shift quotient left by one digit (multiply by 10)
  - Shift divisor right by one digit (divide by 10)

CIS 371 (Martin): Arithmetic

43

CIS 371 (Martin): Arithmetic

44

## Binary Division

$$\begin{array}{r}
 \underline{\phantom{3}} \\
 3 \overline{)29} = 0011 \overline{)011101} = 9 \\
 \underline{-24} = \phantom{00} - 011000 \\
 5 = \phantom{00} 000101 \\
 \underline{-3} = \phantom{00} - 000011 \\
 2 = \phantom{00} 000010
 \end{array}$$

## Binary Division Hardware

- Same as decimal division, except (again)
  - More individual steps (base is smaller)
  - + Each step is simpler
- Find largest bit  $q$  such that  $(q * \text{divisor}) < \text{dividend}$ 
  - $q = 0$  or  $1$
- Subtract  $(q * \text{divisor})$  from dividend
  - $q = 0$  or  $1 \rightarrow$  no actual multiplication, subtract divisor or not
- Complication: **largest**  $q$  such that  $(q * \text{divisor}) < \text{dividend}$ 
  - How do you know if  $(1 * \text{divisor}) < \text{dividend}$ ?
  - Human can “eyeball” this
  - Computer does not have eyeballs
    - Subtract and see if result is negative

## Software Divide Algorithm

- Can implement this algorithm in software
- Inputs: dividend and divisor

```

for (int i = 0; i < 32; i++) {
    remainder = (remainder << 1) | (dividend >> 31);
    if (remainder >= divisor) {
        quotient = (quotient << 1) | 1;
        remainder = remainder - divisor;
    } else {
        quotient = (quotient << 1) | 0;
    }
    dividend = dividend << 1;
}

```


## Divide Example

- Input: Divisor = 00011 , Dividend = 11101

Step	Remainder	Quotient	Remainder	Dividend
0	00000	00000	00000	11101
1	00001	00000	00001	11010
2	00011	00001	00000	10100
3	00001	00010	00001	01000
4	00010	00100	00001	10000
5	00101	01001	00010	00000

- Result: Quotient: 1001, Remainder: 10

## Divider Circuit

 

- N cycles for n-bit divide

## Floating Point

## Floating Point (FP) Numbers

- **Floating point numbers:** numbers in scientific notation
  - Two uses
- Use I: real numbers (numbers with non-zero fractions)
  - 3.1415926...
  - 2.1878...
  - $6.62 * 10^{-34}$
- Use II: really big numbers
  - $3.0 * 10^8$
  - $6.02 * 10^{23}$
- Aside: best not used for currency values

## Scientific Notation

- **Scientific notation:**
  - Number  $[S,F,E] = S * F * 2^E$
  - S: **sign**
  - F: **significand** (fraction)
  - E: **exponent**
  - **"Floating point"**: binary (decimal) point has different magnitude
- + "Sliding window" of precision using notion of **significant digits**
  - Small numbers very precise, many places after decimal point
  - Big numbers are much less so, not all integers representable
  - But for those instances you don't really care anyway
- Caveat: all representations are just approximations
  - Sometimes wierdos like 0.9999999 or 1.0000001 come up
  - + But good enough for most purposes

## IEEE 754 Standard Precision/Range

- **Single precision:** `float` in C
  - 32-bit: 1-bit sign + 8-bit exponent + 23-bit significand
  - Range:  $2.0 * 10^{-38} < N < 2.0 * 10^{38}$
  - Precision:  $\sim 7$  significant (decimal) digits
  - Used when exact precision is less important (e.g., 3D games)
- **Double precision:** `double` in C
  - 64-bit: 1-bit sign + 11-bit exponent + 52-bit significand
  - Range:  $2.0 * 10^{-308} < N < 2.0 * 10^{308}$
  - Precision:  $\sim 15$  significant (decimal) digits
  - Used for scientific computations
- Numbers  $> 10^{308}$  don't come up in many calculations
  - $10^{80} \sim$  number of atoms in universe

## Floating Point is Inexact

- Accuracy problems sometimes get bad
  - FP arithmetic not associative:  $(A+B)+C$  not same as  $A+(B+C)$
  - Addition of big and small numbers (summing many small numbers)
  - Subtraction of two big numbers
- Example, what's  $(1*10^{30} + 1*10^0) - 1*10^{30}$ ?
  - Intuitively:  $1*10^0 = 1$
  - But:  $(1*10^{30} + 1*10^0) - 1*10^{30} = (1*10^{30} - 1*10^{30}) = 0$
- Reciprocal math: "x/y" versus "x\*(1/y)"
  - Reciprocal & multiply is faster than divide, but less precise
- Compilers are generally conservative by default
  - GCC flag: `-ffast-math` (allows assoc. opts, reciprocal math)
- **Numerical analysis:** field formed around this problem
  - Re-formulating algorithms in a way that bounds numerical error
- In your code: never test for equality between FP numbers
  - Use something like: `if (abs(a-b) < 0.00001) then ...`

## Pentium FDIV Bug

- Pentium shipped in August 1994
- Intel actually knew about the bug in July
  - But calculated that delaying the project a month would cost  $\sim \$1M$
  - And that in reality only a dozen or so people would encounter it
  - They were right... but one of them took the story to EE times
- By November 1994, firestorm was full on
  - IBM said that typical Excel user would encounter bug every month
    - Assumed 5K divisions per second around the clock
  - People believed the story
  - IBM stopped shipping Pentium PCs
- By December 1994, Intel promises full recall
  - Total cost:  $\sim \$550M$
- Recent example: Intel's chipset (January 2011)

## Arithmetic Latencies


- Latency in cycles of common arithmetic operations
- Source: *Software Optimization Guide for AMD Family 10h Processors, Dec 2007*
  - Intel "Core 2" chips similar

	Int 32	Int 64	Fp 32	Fp 64
Add/Subtract	1	1	4	4
Multiply	3	5	4	4
Divide	14 to 40	23 to 87	16	20

- Divide is **variable latency** based on the size of the dividend
  - Detect number of leading zeros, then divide
- Floating point divide faster than integer divide? Why?

## Summary

---

 

- Integer addition
  - Most timing-critical operation in datapath
  - Hardware != software
    - Exploit sub-addition parallelism
- Fast addition
  - Carry-select: parallelism in sum
- Multiplication
  - Chains and trees of additions
- Division
- Floating point
  
- Next: single-cycle datapath