

CIS 371

Computer Organization and Design

Lab Hints


Based on slides by Prof. Amir Roth & Prof. Milo Martin

Hints & Tips for ALU Lab


```
// Instruction decoder
wire [3:0]    opcode = insn[15:12];
wire        is_branch = (opcode == 4'b0000);
wire        is_arith = (opcode == 4'b0001);
wire        is_add = (is_arith & (insn[5:3] == 3'b000));
wire        is_mul = (is_arith & (insn[5:3] == 3'b001));
...
```

```
// ALU output multiplexer
assign out = is_branch    ? pc_plus_one + sext_imm9 :
            is_add       ? r1data + r2data :
            is_mul       ? r1data * r2data :
            ...
```

LC4 Non-Pipelined Datapath

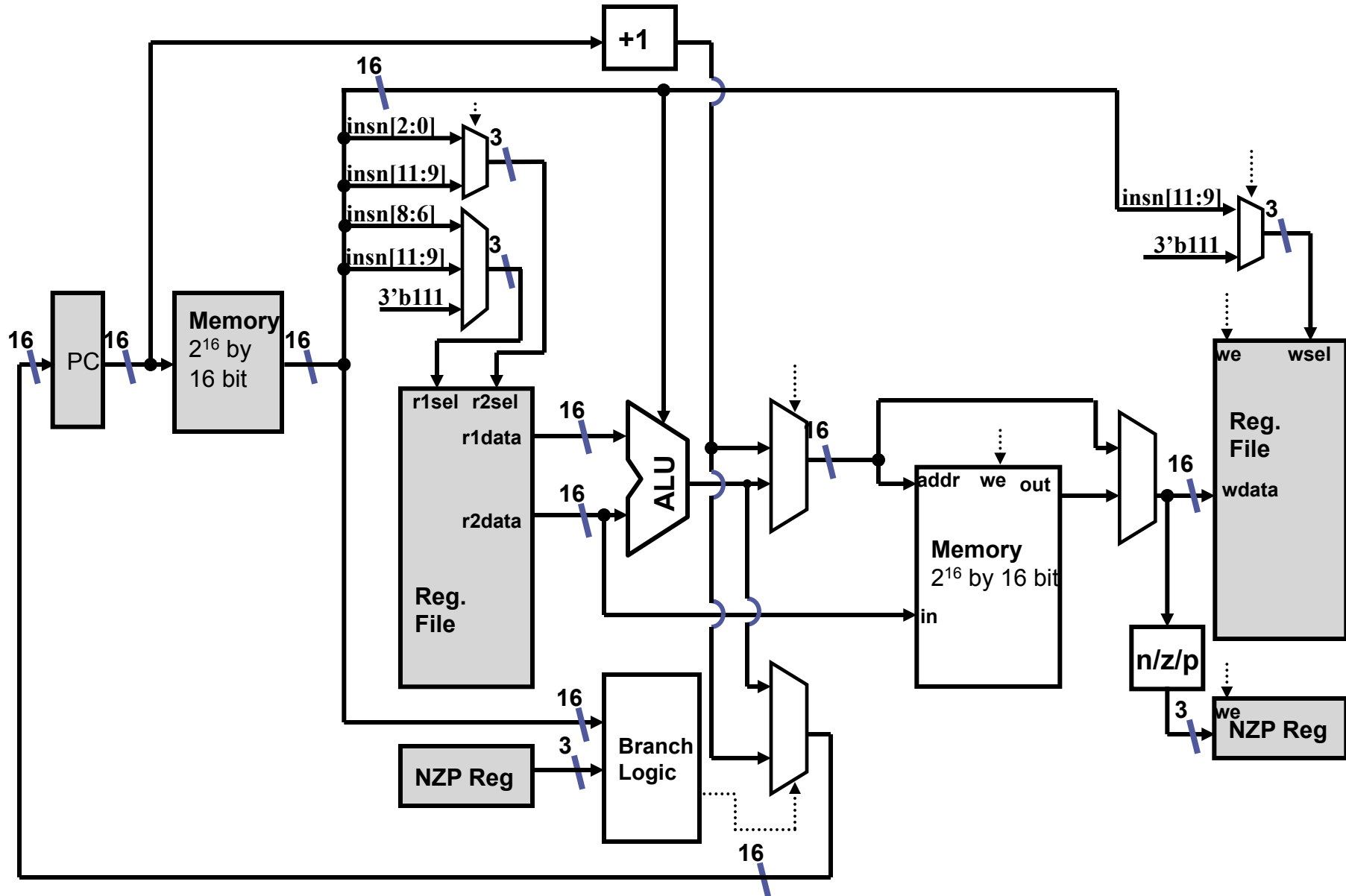

LC4 System Block Diagram

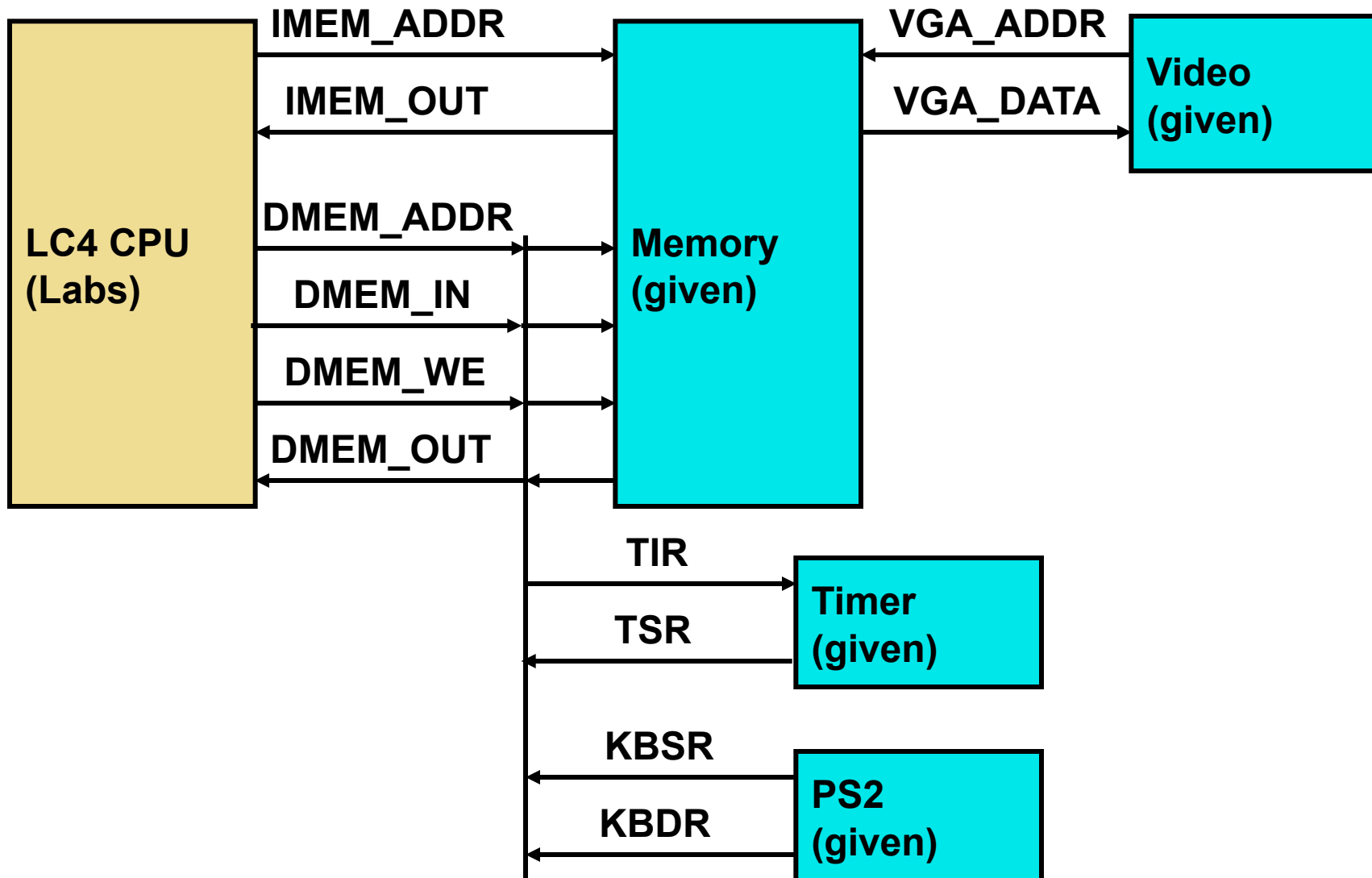

Memory Module

- Processor storage
 - 2^{16} location, each 16-bits
 - Used "Block RAM" on the FPGAs
- Memory mapped I/O
 - Memory mapped display (much like LC-3)
 - Only difference: 128x120 (rather than 128x124)
 - Timer registers
 - Keyboard registers
 - **Read switches**
 - **Set LEDs**
 - **Set 7-segment display**
- Like "register", memory specified using behavioral Verilog

Single-Cycle or Multi-Cycle?

- Xilinx block RAMs (memory) only read on a clock edge
 - How do you do a single-cycle datapath?
 - How can you fetch instructions and load data in same cycle?
- Hack solution: use two clocks
 - “Big-clock” for registers (slow)
 - “Little-clock” for memory (fast)
 - 1 big-clock period = 4 little-clock periods
 - Fetch on big-clock + 1 little-clock
 - Data load on big-clock + 3 little-clock
 - Data store on big-clock
 - Implemented using “global write enable” (gwe) on registers
 - Same system used to implement single-stepping

Recall: Verilog Register

- How do we specify state-holding constructs in Verilog?

```
module register (out, in, wen, rst, clk);  
    parameter n = 1;                wen = write enable  
    output [n-1:0] out;             rst = reset  
    input [n-1:0] in;               clk = clock  
    input wen, rst, clk;
```

```
    reg [n-1:0] out;  
    always @(posedge clk)  
        begin  
            if (rst)  
                out = 0;  
            else if (wen)  
                out = in;  
        end
```

```
endmodule
```

- **reg**: interface-less storage bit
- **always @ ()**: synthesizable behavioral sequential Verilog
 - Tricky: hard to know exactly what it will synthesize to
 - **We will give this to you, don't write your own**
 - "Creativity is a poor substitute for knowing what you're doing"


New "Register" Module

```
module register(out, in, we, gwe, rst, clk);
    parameter n = 1;
    parameter reset_value = 0;

    output [n-1:0] out;
    input [n-1:0] in;
    input          clk, we, gwe, rst;
    reg [n-1:0] state;
    assign #(1) out = state;
    always @(posedge clk)
        begin
            if (rst)
                state = reset_value;
            else if (gwe & we)
                state = in;
        end
endmodule
```


371 Design Rule

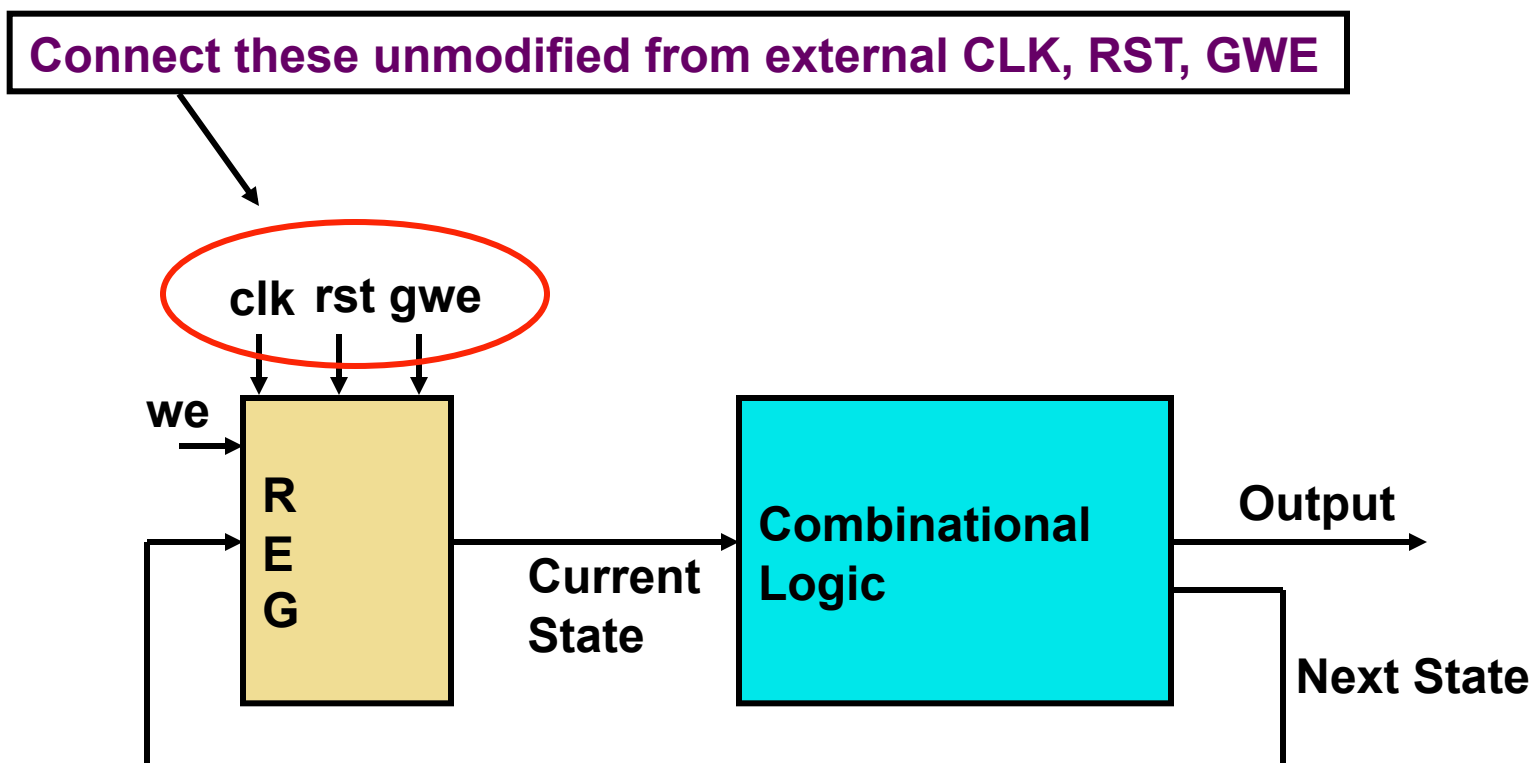- Separate combinational logic from sequential state
 - Not enforced by Verilog, but a very good idea



Clock

- The clock signals are **not** normal signals
 - Travel on dedicated “clock” wires
 - Reach all parts of the FPGA
 - Special “low-skew” routing
- Messing with the clock can cause a errors
 - Often can only be found using timing simulation
- Never do logic operations on the clocks
 - Always pass them unmodified

LC4 DATAPATH SKELETON (LC4_SINGLE.V)

LC4 Datapath Skeleton (lc4_single.v)

```
module lc4_processor(...);

    input          clk;          // main clock
    input          rst;          // global reset
    input          gwe;          // global we for single-step clock

    output [15:0] imem_addr;     // Address to read from instruction memory
    input  [15:0] imem_out;      // Output of instruction memory
    output [15:0] dmem_addr;     // Address to read/write from/to data memory
    input  [15:0] dmem_out;      // Output of data memory
    output          dmem_we;     // Data memory write enable
    output [15:0] dmem_in;      // Value to write to data memory
endmodule
```

- Clock/Reset/Gwe
- Signals to talk to/from memory

LC4 Datapath Skeleton (lc4_single.v)

```
module lc4_processor(...);
    ...
    output [1:0] test_stall; // Testbench: is this is stall cycle?
    output [15:0] test_pc; // Testbench: program counter
    output [15:0] test_insn; // Testbench: instruction bits
    output test_regfile_we; // Testbench: register file write enable
    output [2:0] test_regfile_reg; // Testbench: which register to write in RegFile
    output [15:0] test_regfile_in; // Testbench: value to write into the register file
    output test_nzp_we; // Testbench: NZP condition codes write enable
    output [2:0] test_nzp_in; // Testbench: value to write to NZP bits
    output test_dmem_we; // Testbench: data memory write enable
    output [15:0] test_dmem_addr; // Testbench: address to read/write memory
    output [15:0] test_dmem_value; // Testbench: value read/written from/to memory
endmodule
```

- Hook to our testbench
 - “test_stall” will be used for pipeline
 - Why 2bits? Pipeline will specify source of stall

LC4 Datapath Skeleton (lc4_single.v)

```
module lc4_processor(...);
    ...
    input [7:0]    switch_data;
    output [15:0] seven_segment_data;
    output [7:0]  led_data;

    // PC
    wire [15:0]   pc;
    wire [15:0]   next_pc;

    Nbit_reg #(16, 16'h8200) pc_reg
    (.in(next_pc), .out(pc), .clk(clk), .we(1'b1), .gwe(gwe), .rst(rst));

    /*** YOUR CODE HERE ***/
    assign test_stall = 2'b0; // No stalling for single-cycle design
endmodule
```

- Switches & LEDs (below)
- PC register
 - Notice initialization to 0x8200

LC4 Datapath Skeleton (lc4_single.v)

```
module lc4_processor(...);  
    ...  
  
    `define DEBUG  
    `ifdef DEBUG  
        always @(posedge gwe) begin  
            $display("%d %h %b %h", $time, pc, insn, alu_out);  
        end  
    `endif
```

LC4 Datapath Skeleton (lc4_single.v)

```
module lc4_processor(...);
    ...

    // For on-board debugging, the LEDs and segment-segment display can
    // be configured to display useful information. The below code
    // assigns the four hex digits of the seven-segment display to either
    // the PC or instruction, based on how the switches are set.

    assign seven_segment_data = (switch_data[6:0] == 7'd0) ? pc :
                                (switch_data[6:0] == 7'd1) ? imem_out :
                                (switch_data[6:0] == 7'd2) ? dmem_addr :
                                (switch_data[6:0] == 7'd3) ? dmem_out :
                                (switch_data[6:0] == 7'd4) ? dmem_in :
                                /*else*/ 16'hDEAD;


    assign led_data = switch_data;

endmodule
```

Other Verilog & Lab Hints

Control Logic in Verilog

```
wire [31:0] insn;  
wire [5:0] func = insn[5:0]  
wire [5:0] opcode = insn[31:26];  
wire is_add = ((opcode == 6'h00) & (func == 6'h20));  
wire is_addi = (opcode == 6'h0F);  
wire is_lw = (opcode == 6'h23);  
wire is_sw = (opcode == 6'h2A);  
wire ALUinB = is_addi | is_lw | is_sw;  
wire Rwe = is_add | is_addi | is_lw;  
wire Rwd = is_lw;  
wire Rdst = ~is_add;  
wire DMwe = is_sw;
```

 

Aside: Non-binary Hardware Values

- A hardware signal can have any of four values: 0, 1, ...
 - **x**: don't know, don't care
 - **z**: high-impedance (no current flowing)
- For us in CIS371, both are "bad"
 - Have actual uses (they exist for a reason)
 - For us, any occurrence of "x" or "z" is almost certainly an error
 - Should not be ignored; cause subtle and non-deterministic bugs
- Real-world uses of "x": tells synthesis tool you don't care
 - Synthesis tool makes the most convenient circuit (fast, small)
- Real-world uses of "z": no assigned value
 - Many "tri-state" devices can drive same wire, all but 1 must be "z"

Testing & Testbenches

Testing The Entire Processor

- We give you a testbench module to test the processor
- Instantiates your processor and memory
- Uses a “.trace” file of execution
 - Uses the “test_” signals to compare to the trace entries

Testing The Entire Processor

- Need a little bit more to test the entire processor
 - First thing you need is a program to test
 - Open file `include/bram.v` (memory module)
 - You will see this line at the top

```
`define MEMORY_IMAGE_FILE "code/wireframe.hex"
```

- And these lines inside the memory module

```
reg[15:0] RAM [65535:0];
```

```
initial begin
```

```
    $readmemh(`MEMORY_IMAGE_FILE, RAM, 0, 65535);
```

```
end
```

- The first line is how you define a memory in verilog
- The second is how you define its initial contents
 - Xilinx embeds this into the `.bit` programming file
- Change `MEMORY_IMAGE_FILE` to test different programs

Creating Test Programs

- We will give you a memory image for (modified) mc
 - You can use PennSim to create images of smaller programs
 - First: write a small program in LC4 assembly
 - Second: assemble using PennSim `as` command
 - Third: load into PennSim memory using `ld` command
 - Fourth: create memory image using PennSim `dump` command
 - Example using file `test1.asm`

```
as test1 test1
```

```
ld test1
```

```
dump -readmemh 0 xFFFF test1.hex
```

- Make sure you use the most recent PennSim.jar
 - Linked from labs

Thoughts on Testing

- You shouldn't need to modify the testbench
- But feel free to modify it you wish
- However, realize that the sort of "testbench" Verilog is not synthesizable